

Circuit Elements and Kirchhoff's laws.

* Resistance:- The property of material to ~~resist~~ ^{oppose} the flow of electrons is called resistance and denoted by 'R' (Ω).

* Units:- The unit of resistance is ohm (Ω) according to ohms law $I = \frac{V}{R}$ (A) $i = \frac{v}{R}$.

$$\therefore V = R \cdot \frac{dq}{dt}; i = \frac{V}{R} = G I G.$$

* The power absorbed by resistor is given by

$$P = Vi = (iR)i = i^2 R.$$

* Energy lost in resistance in time 't' is given by $W = \int P dt = Pt = i^2 R t = \frac{V^2}{R} t$.

* Inductance Parameter:- If current is made to pass through an inductor, an electro magnetic field is formed. A change in the magnitude of current changes the electro magnetic field increase in current expands the fields and decrease in current reduces the fields therefore the change in current produces change in electro magnetic field which induces a voltage across the coil. According to Faraday's law of electro magnetic induction.

$$V = L \frac{di}{dt}$$

Power absorbed by the inductor.

$$P = Vi = Li \frac{di}{dt}$$

Energy stored in an inductor

$$W = \int P dt = \int L i \frac{di}{dt} dt = \frac{1}{2} L i^2$$

- I:- The induced voltage across an inductor is zero if the current through it is constant. That means an inductor acts as short circuit to DC.
- II:- In a fixed inductor the current can not change abruptly.
- III:- Pure inductor never dissipates energy, only stores energy.

Capacitors Parameters:- Any two conducting surfaces separated by an insulating medium exhibit property of a capacitor. The conducting surface are called electrodes and insulating medium is called dielectric. A capacitor stores energy in the form of an electric field.

$$C = \frac{Q}{V} \quad (Q = CV)$$

$$C = \frac{dQ}{dt} \cdot P = V_i \cdot C = V \cdot \frac{dQ}{dt}$$

Energy stored in a capacitor


$$W = \int P dt = \int V \cdot C \cdot \frac{dV}{dt} dt = \frac{1}{2} CV^2$$

- * The capacitor acts as open circuit to DC
- * In a fixed capacitor the voltage can not change abruptly.
- * The capacitors can store finite amount of energy even if the current through it is zero.
- * A pure capacitor never dissipates energy but only stores it.


Energy Sources:-

* According to their terminal voltage - Current characteristics electrical energy sources are characterised into ideal voltage sources and ideal current sources. Further they can be divided into independent and dependent sources.

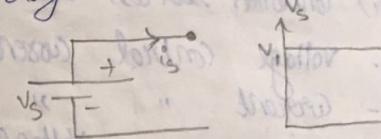
* An ideal voltage source is a two terminal element in which the voltage V_s is completely independent of the current i_s through its terminals.



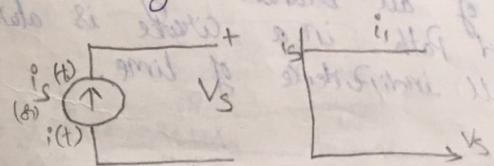
* An ideal constant current source is two terminal elements in which current i_s is completely independent of the voltage V_s across its terminals.



Practical current sources:-

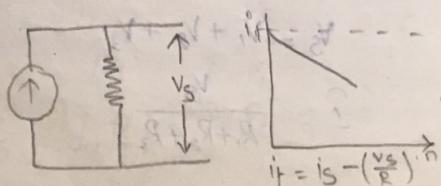

Practical Voltage Sources:-

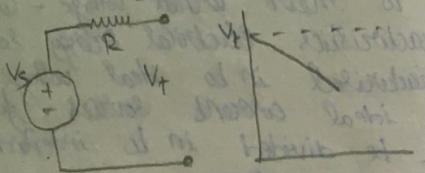


Dependent Sources:- Source voltage or current is not fixed it is dependent on the voltage or current existing at some other location in the circuit.

Dependent (or) Controlled sources are of the following

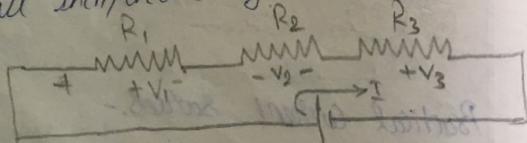- 1) VCCS :- voltage control current sources.
- 2) CCCS :- current " " " voltage "
- 3) CCVS :- " " " current "
- 4) VCVS :- voltage " " "

Krichhoff's law:- It states that algebraic sum of all branch voltages around any closed path in a circuit is always zero in all instants of time.



$$V_s = V_1 + V_2 + V_3$$


$$I = \frac{V_s}{R_1 + R_2 + R_3}$$

The total power supplied by the source in any series resistive circuit is equal to the sum of power in each resistor in series.


$$P_s = P_1 + P_2 + P_3 + \dots + P_n$$

$$P_s = V_s I = I^2 R_s = \frac{V_s^2}{R_s}$$

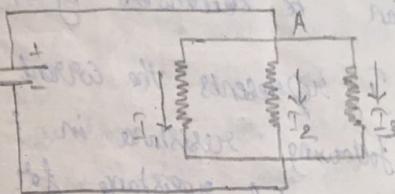Krichhoff's current law:- It states that sum of currents entering in to the node is equal to the sum of currents leaving node.



Date: 22/9/06

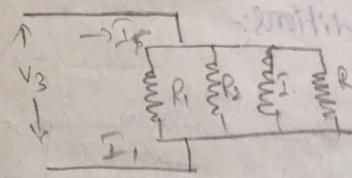

$$I_1 = I_T \frac{R_2}{R_1 + R_2}$$

$$I_2 = I_T = \frac{R_1}{R_1 + R_2}$$

$$V_s = I_1 R_1 = I_2 R_2$$


$$I_T = I_1 + I_2$$

$$I_T = \frac{V_S}{R_T} = \frac{V_S}{R_1 R_2} (R_1 + R_2) = ?$$

In general if the circuit consists of 'n' branches the current in any branch can be determined by $I_i = \frac{R_i}{R_i + R_T} \cdot I_T$

I_i represents the current in the branch following resistance in i connection. R_T is the total resistance for total ^{the} and R_i is the " " " ~~Branch~~ Branch

Initial conditions:-

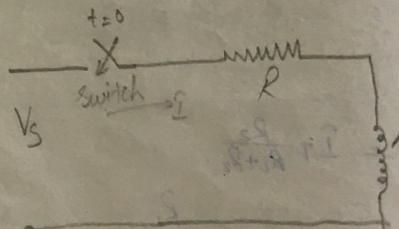

Initial conditions in networks:- Initial & final conditions must be known to evaluate the arbitrary constants that show up in the general solution of differential eq we can have the knowledge of the behavior of the elements at the instants of switching.

At the references time $t=0$ one (81) more switches operate assume that switches act in a zero time. To differentiate b/w the time immediately before and immediately after the operation of ~~spec~~ switch we will use '-' and '+' thus conditions existing just before the switch is operated will be designated as $i(0-)$, $v(0-)$, $i(0+)$, $v(0+)$ etc;

Initial conditions and elements:-

1) The Resistor:- in the ideal resistor $V = IR$ If a step input of voltage applied to a resistor network the current will have same uniform alter by the scale factor $1/R$ the current through a resistor will change instantaneously


If the voltage changes instantaneously and
rise versa.

Inductor: The current can not change instantaneously in a system of constant inductance consequently, closing a switch connect a inductor to a source of energy will not cause current to flow at initial instant. at the initial instance the inductor acts as if it were open circuit integrated as independent at the voltage at terminal. If the current of value I_0 close the inductor at the instant switching takes place the current will continue to flow. But the incident for initial for conductor can be taught as current source as a I_0 .




Capacitor: Voltage can not change instantaneously in a capacitor. with an uncharged capacitor is connected to an energy source a current will

flow instantaneously, the capacitor being equivalent to short circuit with an initial charge in the system the capacitor is equivalent to a voltage source of value $V_0 = \frac{Q_0}{C}$ where Q_0 is initial charge.


Element

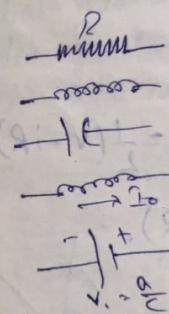







Eq Ckt at $t=0^+$

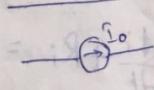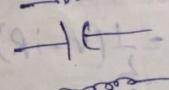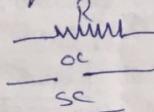

Element

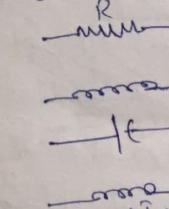


Eq Ckt at $t=0^-$

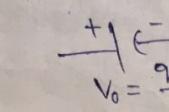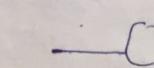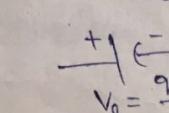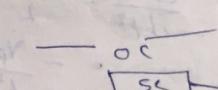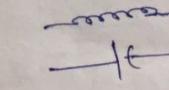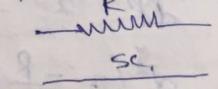

$$V_0 = \frac{Q_0}{C}$$

Geometrical Interpretation

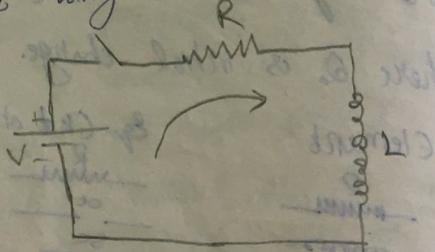Consider the differential eq that describes an RL circuit connected to a constant voltage source.



$$L \frac{di}{dt} + Ri = V \Rightarrow \frac{di}{dt} = \frac{1}{L}(V - iR)$$

$$\frac{di}{dt} = \frac{1}{L}(V - iR).$$


$$\frac{d^2i}{dt^2} = -\frac{R}{L}i(t) \leq \frac{1}{L}(V - iR)$$

$$\frac{d^2i}{dt^2} = -\frac{R}{L} \frac{di}{dt}$$

$$= -\frac{V_R}{L^2}$$

At $t = 0^+$

The procedure for evaluating initial conditions we usually solve first for the initial values of the variables currents, voltages, charges and derivatives for derivatives and the first step is by drawing an equivalent circuit for $t = 0^+$ based on the equivalent element representations in solving for initial values of derivatives the details and order of manipulation will be different for each different network.

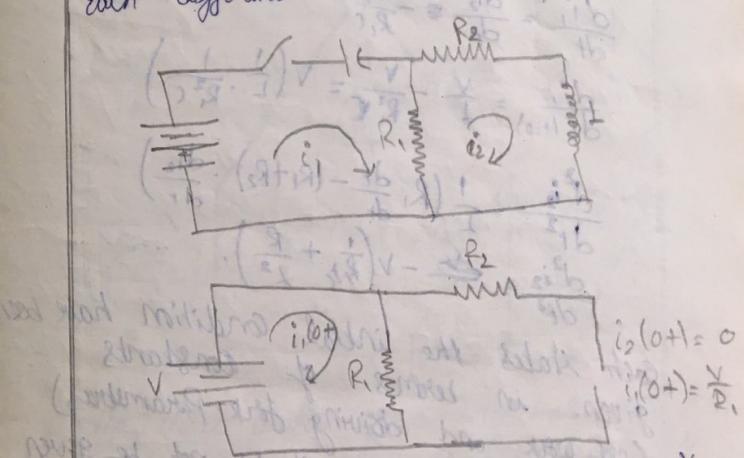

By inspection initial value $i_1(0^+) = \frac{V}{R}$, $i_2(0^+) = 0$.

The first step in solving initial values of derivatives is to write the differential

Eq from Kirchhoff's law in to either a loop
or node which gives the required
quantities more directly.

$$\frac{1}{C} \int i_1 dt + R_1(i_1 - i_2) = V \Rightarrow \frac{i_1}{C} + R_1 \frac{di_1}{dt} - R_1 \frac{di_2}{dt} = 0$$

$$R_1(i_2 - i_1) + R_2 i_2 + L \cdot \frac{di_2}{dt} = 0$$

$$R_1(i_2 - i_1) + R_2 i_2 + L \cdot \frac{di_2}{dt} = 0$$

$$\frac{di_2}{dt} = \frac{1}{L} (R_1 i_1 - (R_1 i_1 + R_2) i_2)$$

$$\frac{di_2}{dt} = \frac{1}{L} R_1 i_1 - \frac{1}{L} (R_1 + R_2) i_2$$

$$\frac{di_1}{dt} = \frac{1}{C} - \frac{V}{R_1 C} = V \left(\frac{1}{L} - \frac{1}{R_1 C} \right)$$

$$\frac{d^2 i_1}{dt^2} = \frac{1}{C} (R_1 \frac{di_1}{dt} - (R_1 + R_2) \cdot \frac{di_2}{dt})$$


$$\frac{d^2 i_2}{dt^2} = -V \left(\frac{1}{R_1 C} + \frac{R_2}{L^2} \right).$$

Each states the initial condition have been given. in terms of constants
(Net work and driving force Parameters)
Solutions to problems should not be given in terms of derivative or integral expression


Methods of analysing circuits:-

In N.R all the elements in a network must satisfy Kirchhoff's laws beside their own characteristics based on this laws, we can form a graph of these eq can be easily written by converting the network in to a graph.

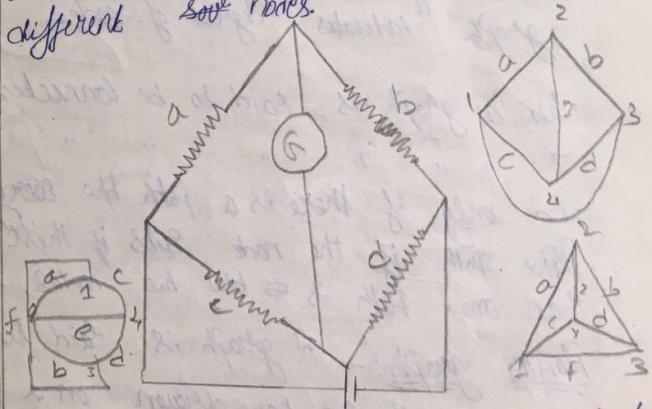Net work:- It is a interconnection of elements in various branches of different nodes.



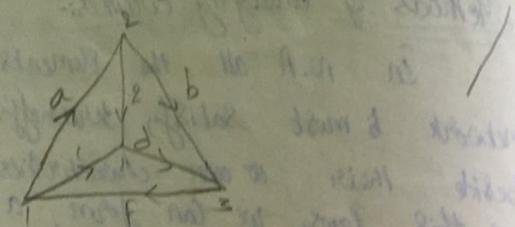The three graphs of 6 branches and four nodes. These are called as undirected if every branch of a graph have a direction then graph is called as directed graph also called as oriented graph.




A node and branch at incident to the node is a terminal of a branch. the nodes if the node can be incident.

The no:- of branches incident at a node of a graph indicates degree of node.


when a graph is said to be connected

* " " " " " if and only if there is a path b/w every pair of nodes if the node gets if there is more than one path is b/w two nodes.

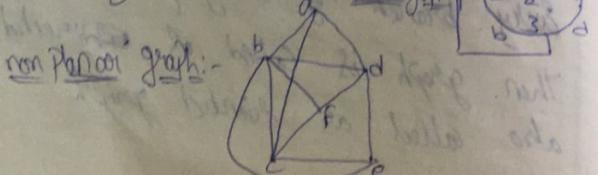Planar graph:- A graph is said to be " if it can be drawn on a plane surface such that draw two branches draw together.



Planar graph

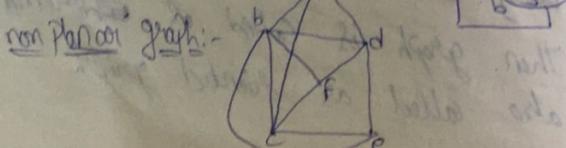


non planar graph

There will be branches which are not in same plane as tell abt other it is called non-planar graph.

Tree & Co-tree

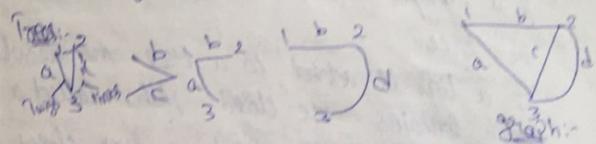* A tree is connected sub graph of net work which consists of all nodes, but not closed path.



* The no of nodes in a graph = no of nodes in a tree

* The " branches " needs \times branch in a graph


* A graph is a tree if there is a unique path b/w any pair of nodes.

$$\{a, c\} = \text{tree}; \{b\} \text{ is co-tree}$$

Links (a) link branches in forming a tree for a given graph and certain branches (a) removed or opened the branches thus opened as called links (a) link branches.

* The set of all links of a given tree is called the co-tree of a graph. thus link branches and tree branches combine to form a graph of entire net work.

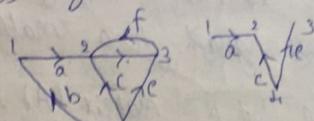Twigs:- The branches of a tree are called its twigs.



for a net work with 'b' branches and 'n' nodes
the no of twigs for selected tree is $(n-1)$ and
no of links is $b - (n-1) =$
the no of twigs $(n-1)$ is known as tree value
of a graph it is also called as rank of
the tree.

If a link is added to a tree the resulting
graph contains one closed path, called a loop
Loops which contain at least one link closed is called
closed loop

Loops which are contain one link are independent
are called basic loops:

Incident Matrix:-

Node	a	b	c	d	e	f
1	1	0	1	0	0	1
2	-1	-1	0	-1	0	0
3	0	1	0	0	1	-1
4	0	0	-1	1	-1	0



Def:- The incidence of elements, to nodes in a
connected graph is shown by element node
incident matrix (A)

* Arrow in a graph are the indication for
current flow (or) voltage in net work.

* It is possible to have an analytical diagram
of an oriented graph in a matrix form.

* The dimensions of a matrix (A) is $n \times b$ where 'n' is no of nodes and

'b' is no of branches.

* An entry a_{ij} has the following values

$a_{ij} = 1$ if j^{th} branch is incident to
and oriented away from i^{th} node

$a_{ij} = -1$ if j^{th} branch incident to and
oriented towards the i^{th} node

$a_{ij} = 0$ if j^{th} branch is not incident to the
 i^{th} node.

* Reduce incident matrix:-

If one row of 'a' is deleted the resulting
 $(n-1) \times b$ matrix is called the reduced incidence
matrix A,

given A, 'a' is easily obtained in which each
column representing a branch contains two
non-zero entries +1 and -1 and rest being
zero.

$$\begin{array}{ccccc} & a & b & c & \\ \xrightarrow{-1} & 1 & 2 & 3 & \\ & 1 & 2 & 3 & \\ \xrightarrow{+1} & 2 & 3 & 1 & \\ & 3 & 1 & 2 & \\ \xrightarrow{+1} & 1 & 3 & 2 & \\ & 2 & 1 & 3 & \end{array}$$



$$\begin{bmatrix} -1 & 0 & 0 & 1 & 0 & 0 \\ 0 & -1 & 0 & -1 & 0 & 0 \\ 0 & 0 & 1 & 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} = 0$$

$$A_1 I_6 = 0$$


* Here I_B represent a call matrix or vector
of a branch currents.

* Main currents and direct matrix:-

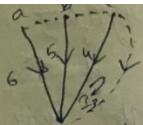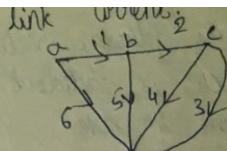for given tree of a graph addition of
tree b/w two nodes form a tree called
a fundamental loop. In a loop there exists a closed
path and circulating current which is called




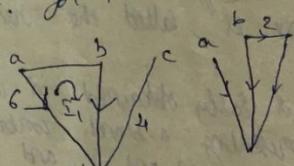The current in any branch of a graph can be formed by two link currents the fundamental loop formed by 'i' link as a unit unique path of the tree joining two nodes of loop. These rates are called fundamental loops. For the same



The link currents 6-insides with branch current direction.

Bi-set matrix:

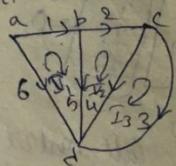

Kirchhoff's voltage law can be applied to the fundamental loops to get set of linearly independent eq. if $v_1, v_2, v_3, v_4, v_5, v_6$ are independent voltages the KVL eq. for the three fundamental loops can be written as.

$$v_1 + v_5 - v_6 = 0$$

$$v_2 + v_4 - v_5 = 0$$

$$v_3 - v_4 = 0$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

where 'V' is an 3×6 matrix called Bi-set matrix (or) fundamental loop matrix and V_B is a cross product column matrix of branch matrix.

$\text{Bi-set matrix and branch currents:}$

If I_B and I_L represents a branch current matrix and loop current matrix respectively and 'T' is the Bi-set matrix then

$$[I_B] = [B^T] [I_L] \rightarrow ①$$

The eq ① is known as link current transformation.

Q. consider a Bi-set matrix for a graph.

$$B = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 \end{bmatrix}; B^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$


$$I_B = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \rightarrow \text{from } ①$$

$$i_1 = I_1; i_2 = I_2; i_3 = I_3; i_4 = I_2 - I_3; i_5 = I_1 - I_2; i_6 = -I_1$$

Cut-set and tree branch voltages:-

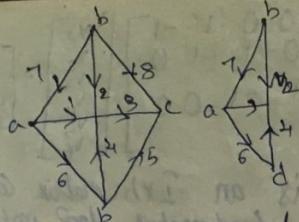A cut-set is a minimal set of branches of a connected graph such that the removal of this branches causes the graph to be cut in to exactly two parts.




The important property of cut-set is that by restoring any one of the branches of the ~~head~~ cut-set, the graph should become connected. A cut-set consists of one, and only one branch of the net work tree, together with any links which must be cut to divide the net work in to 2-paths.

* The set formed by branches 3, 5, 8 is called the cut-set of the connected graph.


Cut-set orientation:-

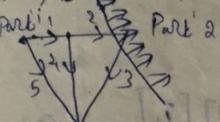We may take the orientation either from Path 1 to Path 2 (or) from Path 2 to Path 1.




The orientation of some branches of the cut-set may be inside with the orientation of cut-set while some branch of cut-set may not be inside.

Cut-set matrix and KCL for cut-set:-

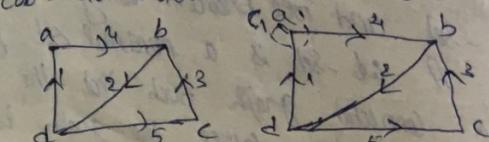

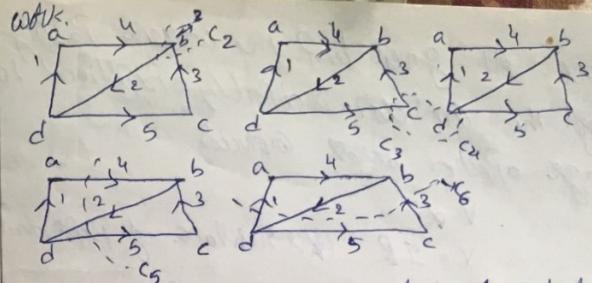KCL is also applicable to a cut-set of a net



Apply for any augmented electrical network the algebraic sum of all cut-set branch currents is equal to zero.
Applying KCL for each cut-set, we obtain the following &

Sol:- Let i_1, i_2, \dots be branch currents.

$$\begin{aligned} C_1 &= i_1 - i_4 = 0 & C_2 &= i_3 + i_4 - i_2 = 0 \\ C_3 &= -i_3 + i_5 = 0 & C_4 &= i_2 + i_5 - i_1 = 0 \\ C_5 &= -i_2 + i_4 + i_5 = 0 & C_6 &= i_1 + i_2 + i_3 = 0. \\ Q \cdot I_6 &= 0 \end{aligned}$$


$$\left[\begin{array}{cccccc} 1 & 0 & 0 & -1 & 0 & 0 \\ 0 & 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 0 & 1 & 0 \\ -1 & 1 & 0 & 0 & -1 & 0 \\ 0 & -1 & 0 & 1 & 1 & 0 \\ 1 & -1 & 1 & 0 & 0 & 0 \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{array} \right] = 0$$

where ' Q ' is called the augmented cut-set matrix of the graph (or) all cut-set matrix of the graph. The matrix I_B is the branch current matrix of the graph.

Ohm's:- At given temp the current passing through the conductor is directly proportional to the voltage applied across conductor.

$$V \propto I$$
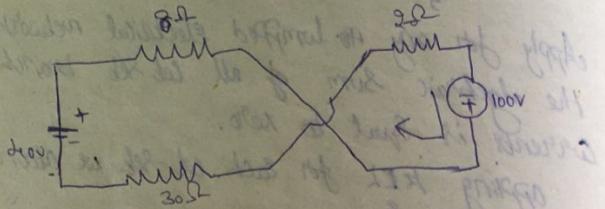
$$V = IR \quad (\text{R is resistance of proportionality})$$



$$V = IR$$

$$I = \frac{V}{R} = \frac{100}{30+2+2} = 2.55A$$


$$100 = 8i + 20 + 2i$$

$$60 = 10i$$

$$i = 6A$$

$$R = \frac{V}{i} = \frac{100}{6} = 16.67\Omega$$


Incident matrix:

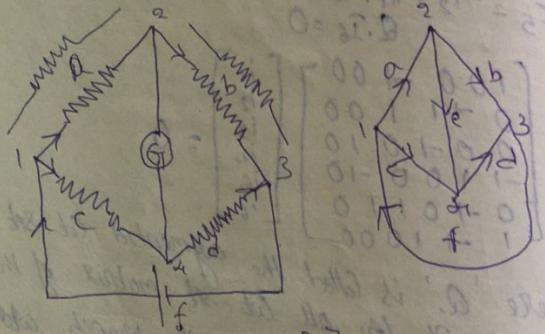



	a	b	c	d	e	f
1	1	0	1	0	0	-1
2	-1	1	0	0	1	0
3	0	-1	0	-1	0	1
4	0	0	-1	1	-1	0

Reduced incident matrix
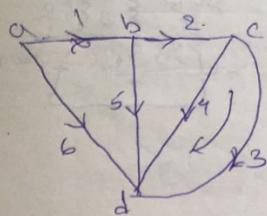
$$\begin{bmatrix} 1 & 0 & b & c & d \\ 2 & -1 & 0 & 1 & 0 \\ 3 & -1 & 0 & 1 & 0 \end{bmatrix}$$



Fundamental cut set: - If the Cut Set can be defined as independent linear variable in the set of variables then the tree is selected and a back edge tree is selected promoting this tree in to the separate tree in to two parts all the twigs which go from 1 part disjointly to the other together with that twig of selected tree will constitute a cut set. This cut set is known fundamental cut set. This fundamental cut set of graph with respect to tree is a cut set found by twig and lead to set of kys unique set of lines is.

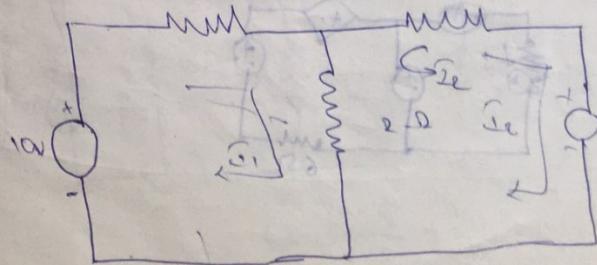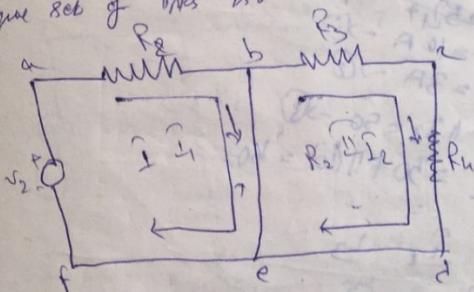


$$5\bar{I}_1 + 2(\bar{I}_1 - \bar{I}_2) = 10$$

$$2(\bar{I}_2 - \bar{I}_1) + 10\bar{I}_2 = 50$$

$$2(\bar{I}_1 + 3(\bar{I}_1 - \bar{I}_2)) + 40 + 80 = 6$$
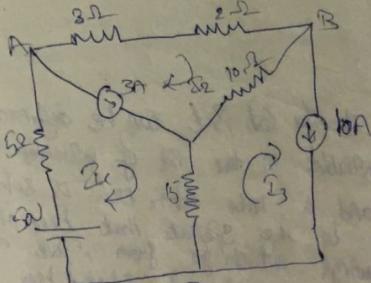
$$3(\bar{I}_2 - \bar{I}_1) + 4\bar{I}_2 + 100 - 40 = 0 \dots$$



$$I_1 - I_2 = 3A \rightarrow ①$$

$$I_2 = 10A \rightarrow ②$$

$$50 = 6 + 3I_1 + 3I_2 + 2I_3 + 10(I_2 - I_3) + (I_1 - I_3) \rightarrow ③$$

$$50 = 6 + 3I_1 \rightarrow ④$$

$$I_3 = 10A \rightarrow ⑤$$

$$I_1 - I_2 = 3A \rightarrow ⑥$$

$$6I_1 + 15I_2 - 1I_3 = 50 \rightarrow ⑦$$

$$6I_1 + 15I_2 = 30 + 11(10) = 160.$$

$$I_1 = 2A$$

$$I_2 = 5A$$


$$I_3 = 10A$$

$$V_{AB} = 6V$$




$$V_{BC} = 45V$$

$$V_{CD} = 30V$$

$$V_{DA} = 6V$$

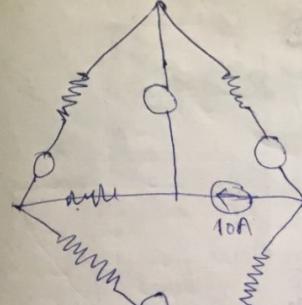

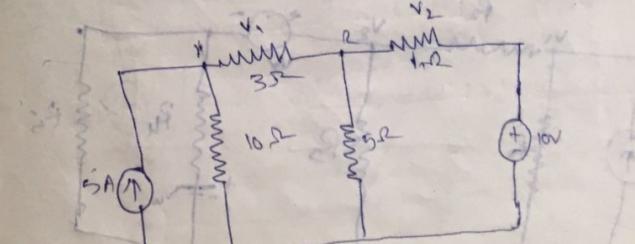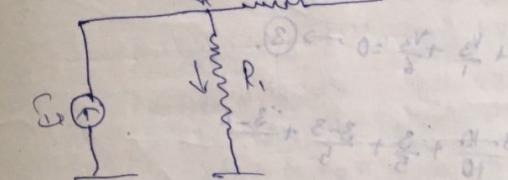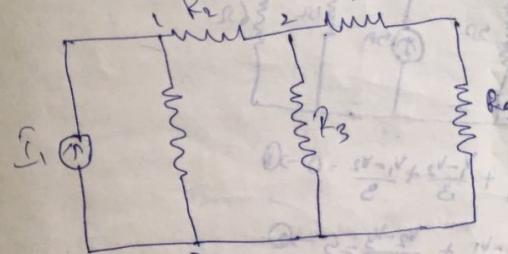In an n -node circuit if one of the node is




$$S = \frac{V_1 - V_2}{3} + \frac{V_1}{10} \rightarrow ①$$

$$\frac{V_2 - V_1}{3} + \frac{V_2}{5} + \frac{V_2 - 10}{1} = 0 \rightarrow ①$$

$$S = \frac{3-1}{3} + \frac{3}{10} = 0$$

$$S = \frac{2}{3} + \frac{3}{10} = 0$$

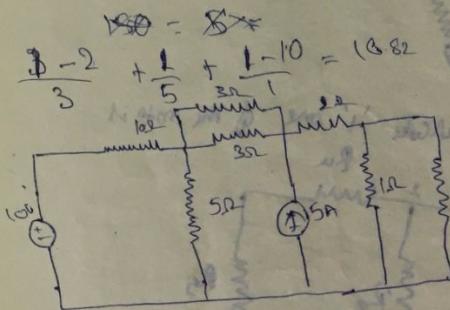


$$\frac{V_1 - 10}{10} + \frac{V_1}{5} + \frac{V_1 - V_2 + V_1 - V_2}{3} = 0 \rightarrow ①$$

$$\frac{V_2 - V_1}{3} + \frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{2} = 0 \rightarrow ②$$

$$\frac{V_3 - V_2}{2} + \frac{V_3}{1} + \frac{V_3 - V_2}{6} = 0 \rightarrow ③.$$

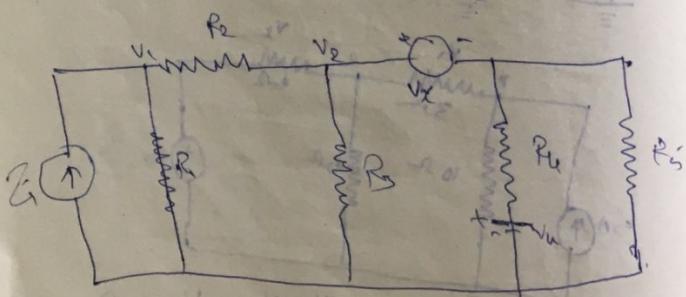
$$10 = \frac{3-10}{10} + \frac{3}{5} + \frac{3-3}{5} + \frac{3-2}{1}$$



$$I = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} \rightarrow ①$$

$$V_2 - V_3 = 8 \rightarrow ②. \quad \text{③} = \frac{V_2 - V_3}{R_2}$$
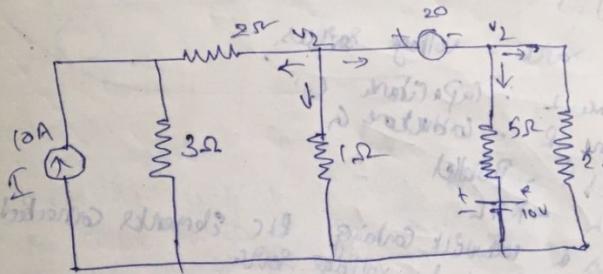
$$0 = \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_3 - V_2}{R_4} + \frac{V_3}{R_5} \rightarrow ④$$




$$10 = \frac{V_1}{3} + \frac{V_1 - V_2}{2} \rightarrow ①$$

$$V_2 + V_3 = 20 \rightarrow ②$$

$$5V_2 - 5V_1 + 10V_2 + 2V_3 - V_4 + V_2 \\ = 20V_2 - 20 - 5V_1 + 2V_3 = (V_2 - V_3)^2$$

$$12V_1 + 7V_3 = 80$$

$$7V_1 - 7V_3 = 120.$$

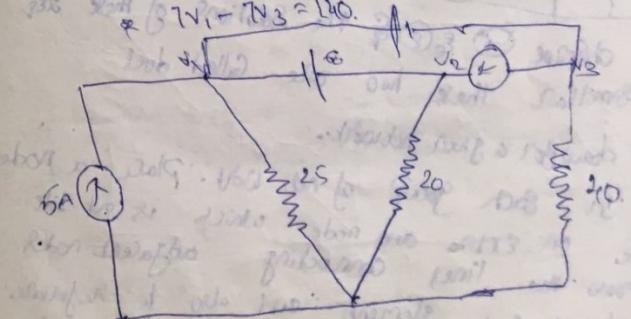

In an electrical circuit there are new circuits which can be interconnected to get new circuits. Such pair of given form are given below.

Current Source = Voltage Sources.


Inductance \leftarrow Capacitance C

Resistance R \leftarrow Inductor G

Series \leftarrow Parallel

$KCL \leftarrow KVL$

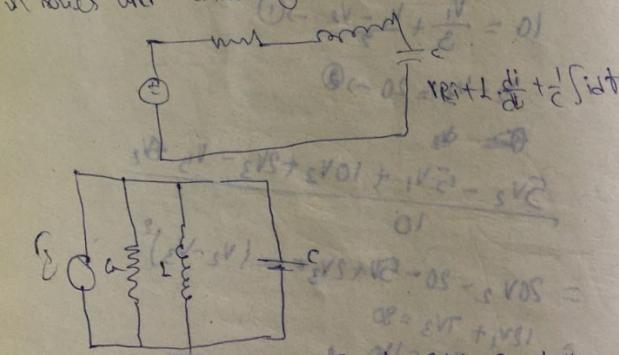
Consider a network containing RLC elements connected in series and excited by voltage source



If we observe ① & ② & the solutions of these 2 eq will be similar these two are called dual.


Procedure to draw for a given network:-

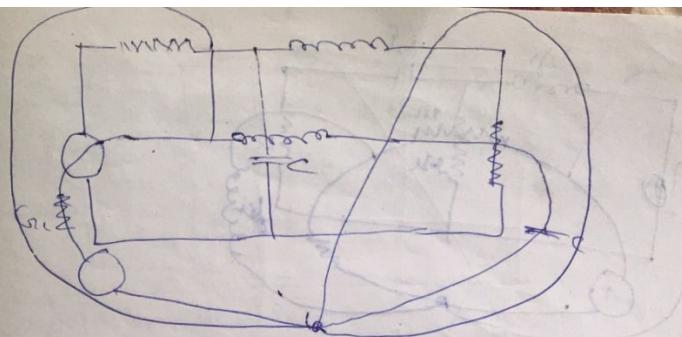In each group of net work place a node and place an extra one node which is outside. Then draw the lines connecting adjacent nodes passing through each element and also to reference node by placing dot of each element in the line passing through original elements.






Show that the work produced by this flux leaves the circuit the to of the current flowing through the circuit. one changes with circuit time the flux will also change.

$$M = \frac{N\Phi}{2}$$

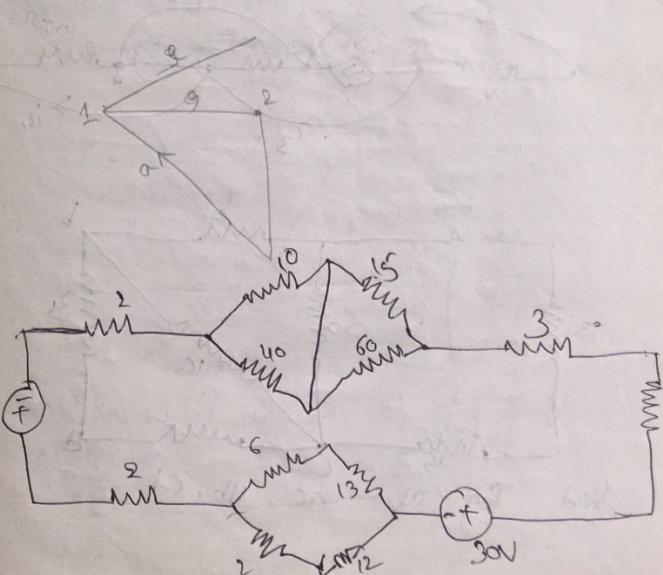


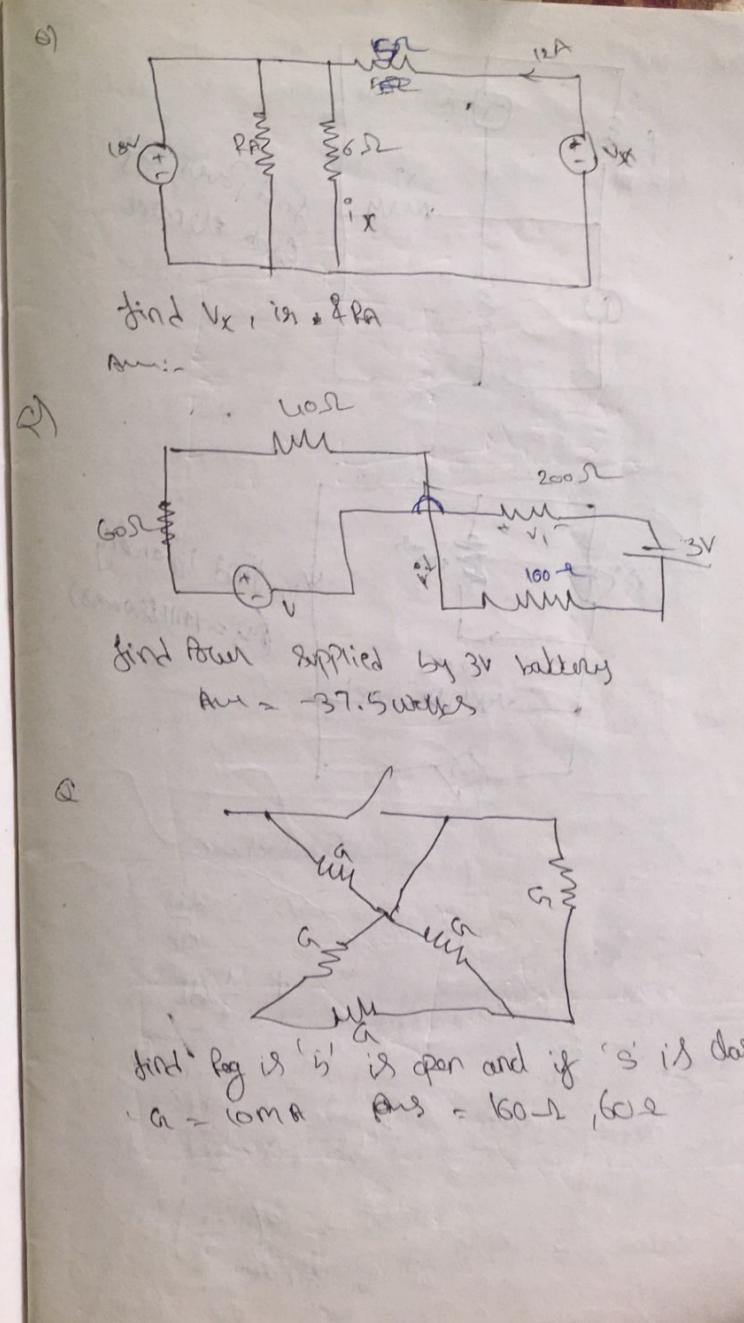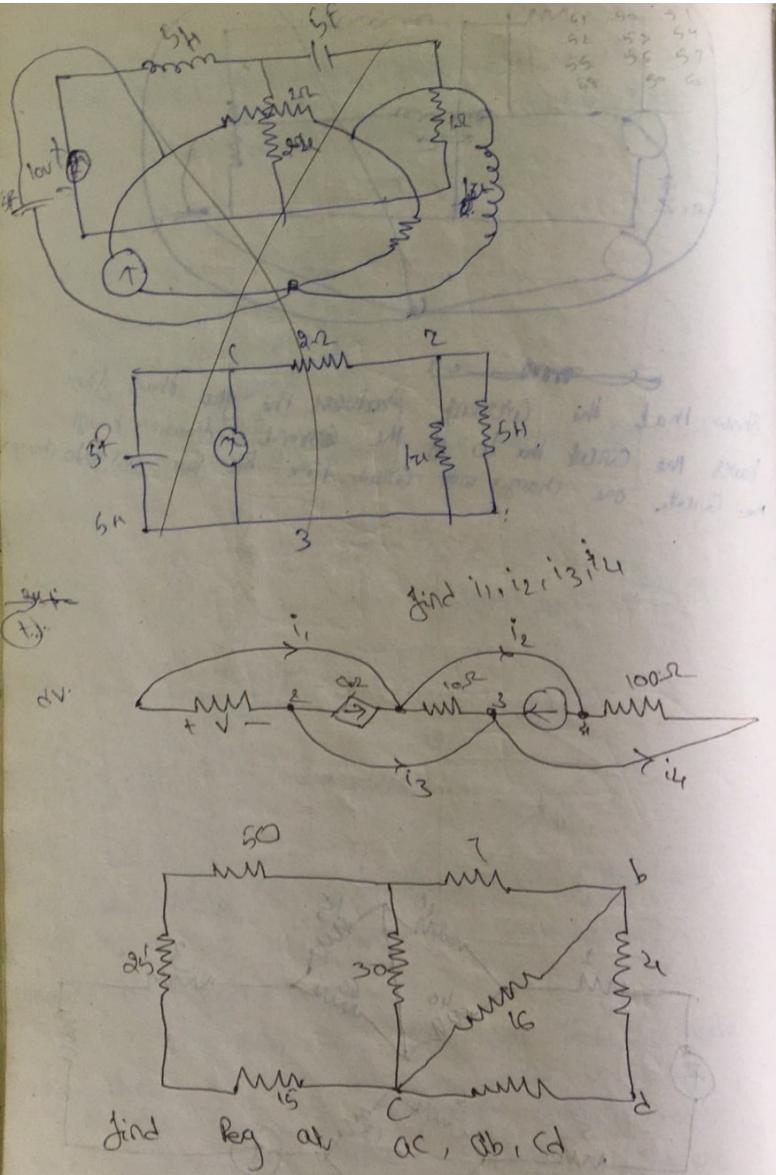Find Power Supply on source and also find current in circuit.



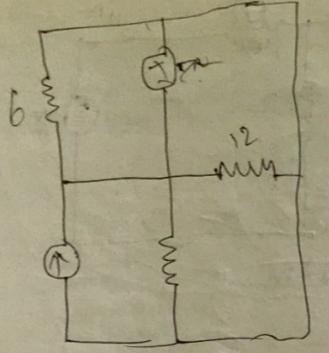

Find Power by
Each Element

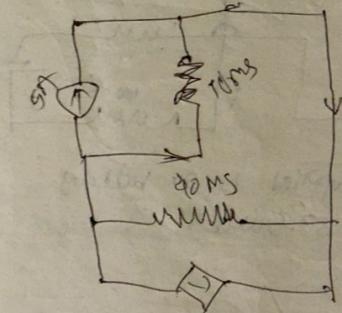

find in and by
fungi & milliseas

Resista

$\frac{d}{dx} \sin x$

octane

$$V = \frac{dV}{dt} \cdot R$$

$$dI = \frac{1}{t} k dI$$


$$d_2 = \frac{1}{\lambda} \cdot \ln R$$

$$i(t) - i(0) = \frac{1}{t} \int_0^t v \cdot dt$$

$$P = VI = \rho \left(L \frac{di}{dE} \right)^2$$

$$W = \frac{1}{2} L^2$$
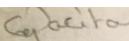
$$W = \frac{24}{5} \left(\frac{1}{2} \Delta E \right)$$



$$c = \rho, \quad \varrho = \frac{\rho}{c}$$

$\frac{2}{2}$

$$\int_a^b dv = \int_a^b l db$$

$$E = \frac{1}{2} C_r^2$$

$\angle = 150^\circ$


$$I = \frac{V}{R_1 + R_2 + R_3}$$

Current:- $V_{in} = 10 \times 10^{-3}$ & 30Ω

$$\frac{1}{c} + \frac{1}{2} = \frac{1+3}{6} = \frac{x^2}{8}$$

$$0.166 + 0.5$$
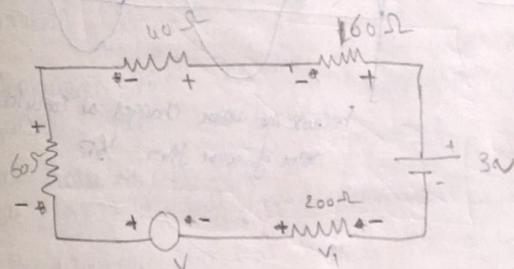
$$I = 10 \left(\frac{5}{8} + \frac{1}{2} \right) = 10 \left(\frac{9}{8} \right) = \frac{90}{8}$$



$$V_{\text{out}} = \frac{V_S}{R_1 + R_2 + R_3}$$

V_{Bm}

$$3V = 160 + 40 + 60 + V + 200$$

$$3V = 3450 \quad 460 + V \quad \Rightarrow \quad V = 460 \Rightarrow 230 \text{ V}$$

4- Chapter:-

Periodic wave forms:-

A function $f(x)$ is said to be Periodic when $f(x) = f(x + T)$


$f(x) = f(x + nT)$ where T = Time Period of function $f(x)$

Non Periodic:- If a function $f(x)$ is said to be non


Periodic when $f(x) \neq f(x + nT)$

where 'n' is integer.

For periodic wave form:-

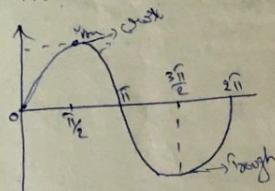

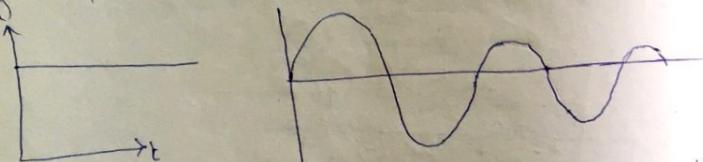The time period for non periodic wave form is



because the value changes at every interval
value of wave form $\frac{1}{2}\pi$.

Amplitude:-


Frequency:- The frequency of a wave is defined as the no. of cycles that wave completes in 1 sec.

Angular relation of Sin wave:-

A sin wave can be expressed in terms of angular measurement i.e. either degrees or radians.

Radian:- A radian is the angular distance measured along the circumference of circle which is equal to radius of circle. The sin wave completes a half cycle in 180° of π radians when completed full circle with 360° are 2π .

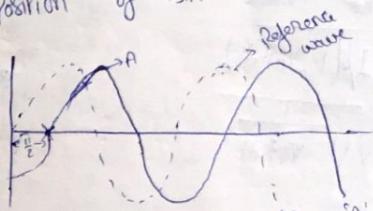Phase of a sin wave:- It is an angular measurement that specifies position of sin wave related to the reference.



The phase shift of the wave form 'A' is $\frac{\pi}{2}$ with respect to reference wave form indicated by dotted lines.

Logging wave form is 'A'

If $f(x) = \sin x$ then for the reference wave form and there is a phase shift with R. ϕ for a wave form 'A' with function $f(x) = \sin(x + \phi)$

Instantaneous value:- The value of sin wave is defined at different points along the wave form.

Peak values:- The max value during the positive half cycle (A) -ve half cycle

The difference b/w max value of +ve half cycle and max value of -ve half cycle.

Avg value:- The avg value of any function $f(t)$ with period 'T' is given by $f(t)_{avg} = \frac{1}{T} \int_0^T f(t) dt$.

P.Rajesh

If the function $V(t) = V_m \sin(\omega t)$

$$\text{avg value} = V(t) = \frac{2V_m}{\pi}$$

$$\text{avg value of sinusoid} = 0.637$$

Root mean square value " " of sin wave is a measure of heating effect of the wave

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \cdot \frac{2\pi}{(2\pi - 0)}$$

If the function consists of no. of sinusoidal terms i.e.

$$V(t) = V_0 + V_1 \cos(\omega t) + V_2 \cos(2\omega t) + \dots + V_S \sin(\omega t) + V_S \sin(2\omega t)$$


$$V(t)$$

$$\text{the effective value } V_{rms} = \sqrt{V_0^2 + \frac{1}{2}(V_1^2 + V_2^2 + \dots) + \frac{V_S^2}{2}(V_1^2 + V_2^2 + \dots)}$$

Peak factor :- It is the ratio of peak value to rms value.

$$\text{peak value} = \sqrt{2} \times V_{rms}$$

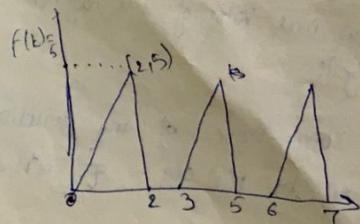Form factor :- It is the ratio of rms value to avg value



$$t = 3$$

$$\text{time per sec} = \frac{1}{3} \int_0^3 f(t) dt$$


$$= \frac{1}{3} [at^3]_0^3 = 10.$$

$$\frac{x_1 - x_1}{x_2 - x_1} = \frac{x - x_1}{x_2 - x_1}$$

$$\therefore \boxed{\int_a^b f(x) dx = \int_a^b f(t) dt}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T (f(t))^2 dt}$$
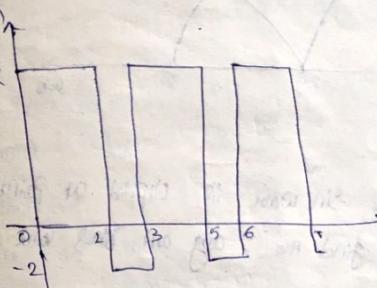
$$= \sqrt{\frac{1}{3} \int_0^3 (2t)^2 dt} = \sqrt{\frac{1}{3} \cdot 27} = 3\sqrt{3}$$



$$\int_0^b f(t) dt = f(t) = 4 \quad (0, 3); b = 3$$

$$\int_0^b f(t) dt = \int_0^3 f(t) dt = \frac{3}{2} \cdot 4 = 6.$$


$$V_{rms} = \sqrt{6}$$

$$\text{avg value} = V(t) = \frac{2 \times V_m}{\pi} = \frac{2 \times 4}{\pi} = 2,$$

$$\text{avg } V_{rms} = \sqrt{\frac{1}{T} \int_0^T (f(t))^2 dt} = \sqrt{\frac{1}{2} \int_0^2 (2t)^2 dt}$$


$$V_{rms} = \sqrt{\frac{1}{2} \times 4 \times 2} = 2\sqrt{3},$$
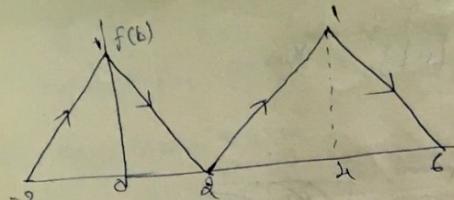
$$V_{\text{avg}} = \frac{V_m}{\sqrt{2}} = 2.63 \text{ V}$$



$$T=2; \quad \frac{y_2 - y_1}{x_2 - x_1} = \frac{1-0}{0-(-2)} = \frac{1}{2}$$
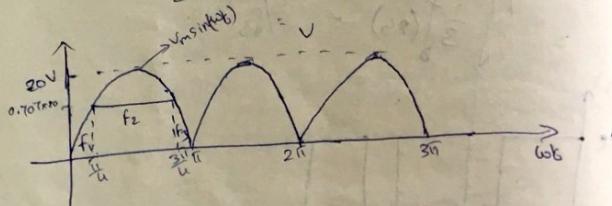
$$f(0) = \frac{1}{2}(0+2) = -2 \text{ to } 0 \\ = -\frac{1}{2}(2-0) = -\frac{1}{2}(2-2)$$



A full wave rectified sin wave is clipped at point PSS as shown in figure find the avg and rms value of the function

$$f_2 = 12.13 \text{ V}; f_3 = V_m \sin \omega t$$

$$\frac{1}{T} \int_0^T f_2(t) dt = \int_0^{\frac{\pi}{2}} 12.13 dt$$

$$= \int_0^{\frac{\pi}{2}} 12.13 \sin(\omega t) dt = 8 \text{ V}$$

$$8 \left[\cos(\omega t) \right]_0^{\frac{\pi}{2}}$$

$$\cos\left(\frac{\pi}{2}\right) - \cos(0) = 0.999 - 0.2496 \\ = 0.75,$$

$$\int_0^{\pi} \sin(\omega t) dt = \left[-\frac{1}{\omega} \cos(\omega t) \right]_0^{\pi} \\ = -\frac{1}{\omega} \cos(\pi) + \frac{1}{\omega} \cos(0) \\ = -\frac{1}{\omega} (-1) + \frac{1}{\omega} (1) \\ = \frac{2}{\omega} = 0.99 - 0.99 = 0.$$

Determine the rms value of the voltage defined by

$$v = 5 + 5 \sin(314t) + \frac{1}{2} \cos(628t)$$

find rms value of function $v = 20 \times (1 - e^{-0.001t})$ where t lies between 0 to 0.1 and $v = 20 e^{-50} \times (t^2 - 0.1)$ where t lies between 0.1 to 0.2

series Resonance :-

occurs when total reactance is zero

$$\text{angular frequency} : \omega = \frac{1}{\sqrt{LC}}$$

$$\text{Resonance frequency} : f_R = \frac{1}{2\pi\sqrt{LC}}$$

Q:- Consider an RLC circuit as shown in figure the total impedance of RLC " " is given as $Z = R + j(X_L - X_C)$

resonance is a phenomenon in an electrical circuit where the total reactance in the circuit become zero at some frequency

$\therefore Z = R$ in the above circuit $X_L - X_C = 0$ total reactance occurred which should becomes zero at resonance

$$X_L - X_C = 0 \Rightarrow X_L = X_C \Rightarrow X_{RL} = \frac{1}{\omega C}$$

$$\Rightarrow \omega^2 = \frac{1}{LC}$$

$$Z = R$$

$$\omega = 2\pi f$$

$$2\pi f_R = \frac{1}{\sqrt{LC}}$$

so the above eq represents the resonance frequency in an RLC circuit $f_R = \frac{1}{2\pi\sqrt{LC}}$

Resistor $R = 50\Omega$; $X_L = 50\Omega$; Capacitive reactance $= -jX_C$


Determine the value of capacitive reactance and impedance at resonance. Draw out resonance graph.

$$L = R \Rightarrow X = 50, X_C = 50$$

$$f_R = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{50 \times 10^{-9}}} = 10 \text{ Hz}$$

Find resonance frequency in RCL when $R = 10\Omega$; $L = 0.5 \text{ mH}$ and capacitance $C = 10 \text{ nF}$.
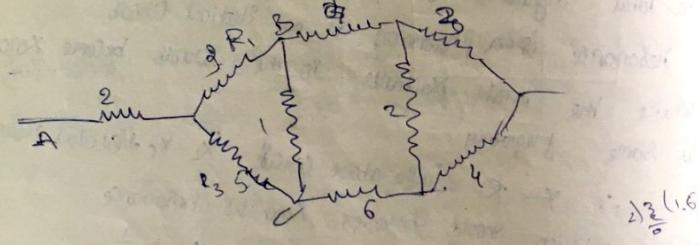
$$f_R = \frac{1}{2\pi\sqrt{0.5 \times 10^{-9}}} = \frac{1}{2\pi\sqrt{5}} = \frac{1}{2\pi} = 0.25 \text{ Hz}$$



$$R_A = \frac{R_1 R_3}{R_1 + R_2 + R_3} = \frac{3 \times 5}{3 + 2 + 5} = \frac{15}{10} = 1.5$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2 + R_3} = \frac{3 \times 1}{4 + 1 + 3} = \frac{3}{8} = 0.375$$

$$I_C = \frac{L \times 1}{L + 1 + 5} = \frac{1}{6} = 0.166$$

$$R_D = \frac{3 \times 2}{3 + 2 + 4} = \frac{6}{9} = \frac{2}{3} = 0.66$$


$$Z_E = \frac{4 \times 2}{4 + 2 + 6} = \frac{8}{12} = 0.666$$

3) $\omega = 0.166$

Theorems:- Net Work :-

Superposition theorem:-

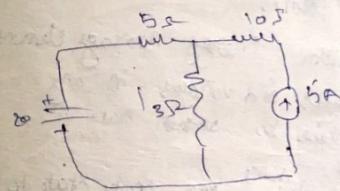In any linear network containing 2 or more sources the response in any element is equal to the algebraic sum of the responses caused by individual sources acting alone while other sources are non-operative.



$$\frac{1}{R_{AB}} = \frac{1}{5} + \frac{1}{10} = \frac{3}{10}$$

$$R_{AB} = \frac{10}{3} \Omega$$

$$R_{AB} = \frac{1}{3} \Omega$$


$$R_{AB} = \frac{1}{3} \Omega$$


$$R_{AB} = \frac{1}{3} \Omega$$

$$R_{AB} = \frac{1}{3} \Omega$$

Find Current flowing through 3Ω resistor using Superposition theorem.

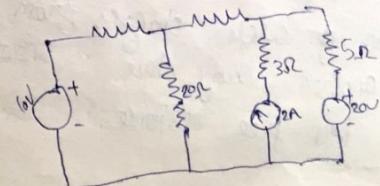Find Voltage across 9Ω resistor by using super position theorem.



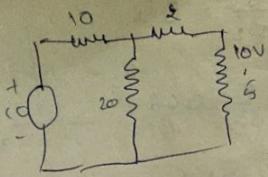

$$\frac{V-10}{10} + \frac{V}{20} + \frac{V}{5} = 0$$

$$V\left(\frac{1}{10} + \frac{1}{20} + \frac{1}{5}\right) = 0$$

$$V = \frac{10+70+20}{140}$$

$$= \frac{230}{140}$$

$$= 1.643$$

$$= 3.14$$

A circuit having constant sources, is said to be in steady state if the currents and voltages do not change with time.

Circuits with currents and voltages having constant amplitude and constant frequency sinusoidal functions are also considered to be in a steady state.

Transient State :- Circuits with energy storage elements

change in excitation, the currents and voltages in any element may change from one state to another state.

This is known as transient state. The time taken for circuit to change from one steady state to another steady state is called transient time.


Natural response (a) Steady state response :-

The response of the circuit depends upon the nature of the elements in the circuit, is known as natural response.

Forced response :-

The response of circuit changes from one steady state to another steady state is known as transient response. (a) free response.

DC response of an RL circuit:-

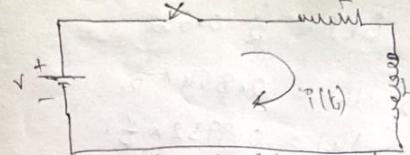

Consider a circuit consisting of an inductor and an inductor as shown in figure apply KVL

$$V = i(t) \cdot R + L \cdot \frac{di(t)}{dt}$$

dividing B.S on L

$$\frac{V}{L} = \frac{i(t) \cdot R}{L} + \frac{di(t)}{dt}$$

$$\frac{di}{dt} + R \frac{di}{dt} = \frac{V}{L}$$

$$y = \frac{V}{L}$$

$$I.F. = e^{\int \frac{R}{L} dt}$$

$$I.F. = e^{\frac{R}{L} t}$$

$$e^{\frac{R}{L} t} \cdot \frac{dy}{dt} = \int e^{\frac{R}{L} t} \cdot \frac{di(t)}{dt} dt + C$$

$$e^{\frac{R}{L} t} \cdot i(t) = \frac{V}{R} e^{\frac{R}{L} t} + C$$

$$i(t) = \frac{V}{R} + C \cdot e^{-\frac{R}{L} t} \quad \rightarrow (1)$$


$$\text{At } t=0; \frac{dy}{dt} = 0$$

$$0 = \frac{V}{R} + C \cdot e^0$$

$$C = -\frac{V}{R}$$

$$\text{Substituting in (1)}$$
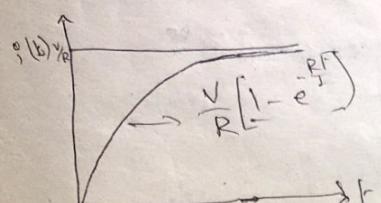
$$i(t) = \frac{V}{R} \left[1 - e^{-\frac{R}{L} t} \right]$$



Time constant $\tau = \frac{RC}{R}$


$$At t=0 \Rightarrow i(0) = \frac{V}{R} \times 0.632$$

$$t=\infty \Rightarrow i(\infty) = 0.864 \times \frac{V}{R}$$

$$t=5\tau \Rightarrow i(5\tau) = 0.9932 \times \frac{V}{R}$$

$$\text{Transient time} = 5\tau = 5 \times \frac{R}{C}$$

DC response of an RC net work:-

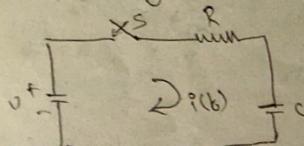

$$V = i(t)R + \frac{1}{C} \int i(t)dt \rightarrow ①$$

$$0 = R \frac{di(t)}{dt} + \frac{i(t)}{C}$$

$$\Rightarrow 0 = \frac{d(i(t))}{dt} + \frac{i(t)}{RC} \rightarrow ②$$

$$0 = \left(D + \frac{1}{RC} \right)$$

$$D + \frac{1}{RC} = 0$$

$$D = -\frac{1}{RC}$$


$$\therefore i(t) = C \cdot e^{-HRC}$$

$$i(0) = C \cdot e^0 = C$$

$$\Rightarrow \frac{C}{R} = C$$


$$i(0) = \frac{C}{R} \text{ when } t=0$$

$$i(t) = \frac{C}{R} \cdot e^{-HRC}$$

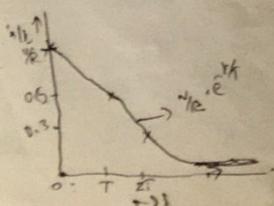

Time constant $\tau = \frac{RC}{R}$

DC

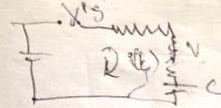

$$V = i(t) \cdot R + L \cdot \frac{di(t)}{dt} \rightarrow ③$$


$$0 = R \cdot i(t) + L \cdot \frac{di(t)}{dt} + i(t)$$

$$\Rightarrow D = \frac{1}{L}$$

$$0 = \left[D^2 - \frac{1}{L} - \frac{1}{R^2} \right] i(t)$$

$$A.C. \rightarrow R^2$$

Sinusoidal response of RL circuit:-

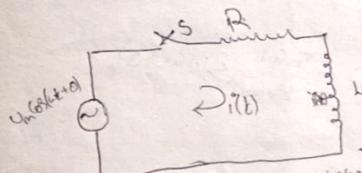

$$V_m \cos(wt + \theta) = i(t)R + L \cdot \frac{di(t)}{dt} \rightarrow ④$$

$$\frac{V_m}{L} \cdot \cos(wt + \theta) = i(t) \left(\frac{R}{L} + j \right)$$

$$D + \frac{R}{L} = 0$$

$$\Rightarrow D = -\frac{R}{L}$$

$$i_1(t) = C_1 \cdot e^{-\frac{R}{L}t}$$

$$i_p = k_1 \cos(wt + \theta) + k_2 \sin(wt + \theta)$$

$$i_p = -k_1 w \sin(wt + \theta) + k_2 w \cos(wt + \theta)$$

Substituting in ④

$$V_m \cos(wt + \theta) = [k_1 \cos(wt + \theta) + k_2 \sin(wt + \theta)]R + L \left[-k_1 w \sin(wt + \theta) + k_2 w \cos(wt + \theta) \right] - \sin(wt + \theta) [k_2 R - L k_1 w] + (w \cos(wt + \theta)) [k_1 R + k_2 w]$$

$$V_m = K_1 R + K_2 \omega L \rightarrow ①$$

$$0 = K_2 R - K_1 \omega L \rightarrow ②$$

Solving above ① and ② by method

$$V_m = K_1 R + K_2 \omega L$$

$$0 = K_2 R - K_1 \omega L$$

$$\frac{V_m}{R} = K_1 - K_2 \omega L$$

$$V_m = R(K_1 - K_2 \omega L)$$

$$i_1 = \frac{V_m R}{R^2 + (\omega L)^2}$$

$$i_1 = \frac{V_m R}{R^2 + (\omega L)^2} \cos(\omega t + \phi) + \frac{V_m \omega L}{R^2 + (\omega L)^2} \sin(\omega t + \phi)$$

$$i(t) = i_1 + i_2$$

$$= C_1 e^{-\omega L t}$$

$$\text{At } t=0, i(0)=0$$


$$C_1 = - \left[\frac{V_m R}{R^2 + (\omega L)^2} \cos \phi + \frac{V_m \omega L}{R^2 + (\omega L)^2} \sin \phi \right]$$

$$i(t) = - \left[\frac{V_m R}{R^2 + (\omega L)^2} \cos \phi + \frac{V_m \omega L}{R^2 + (\omega L)^2} \sin \phi \right] e^{-\omega L t} + \frac{V_m \omega L}{R^2 + (\omega L)^2} \sin(\omega t + \phi)$$

$$V_m \cos(\omega t + \phi) = i(t) R + \frac{1}{C} \int i(t) dt$$

$$\Rightarrow -V_m \sin(\omega t + \phi) = R \cdot \frac{di(t)}{dt} + \frac{i(t)}{C}$$
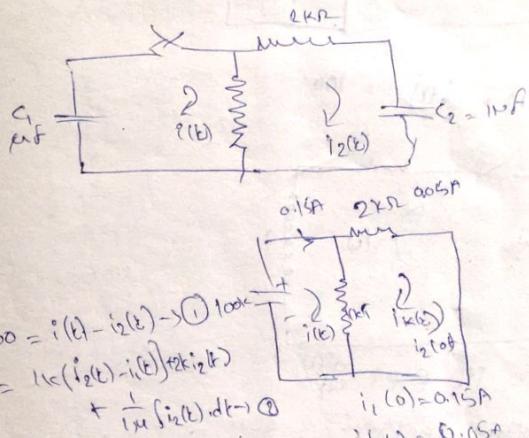
$$\Rightarrow V_m \sin(\omega t + \phi) = R \cdot \frac{di(t)}{dt} + \frac{i(t)}{C}$$



$$i(t) = i_1(t) - i_2(t) \rightarrow ①$$

$$100 = i_1(t) - i_2(t)$$

$$0 = 1k(i_2(t) - i_1(t)) + 2k i_2(t)$$

$$+ \frac{1}{100} \int i_2(t) dt \rightarrow ③$$

$$i_1(0) = 0.15A$$

$$i_2(0) = 0.05A$$

$$100 = i_1(t) - i_2(t) \rightarrow ①$$

$$0 = 1k(i_2(t) - i_1(t)) + 2k i_2(t) + \frac{1}{100} \int i_2(t) dt \rightarrow ②$$

$$0 = 1k(100) + 2k i_2(t) + \frac{1}{100} \int i_2(t) dt$$

$$0 = 100k + 2k i_2(t) + \frac{1}{100} \int i_2(t) dt$$

$$0 = \frac{2k i_2(t) + 100k}{100} + \frac{1}{2k} \int i_2(t) dt$$

$$= 2k D + 10^6 = 0$$


$$D = -\frac{10^6}{2k} = 0.5 \times 10^3$$

$$i_2(t) = C_1 e^{-0.5 \times 10^3 t}$$


$$i_2(t) \approx 0.05e$$

$$100 = i_1(t) - 0.05e \Rightarrow 100 + 0.05 = i_1(t) = 100.05e$$

$$i_{00} = i_1(t) - 0.05e^k$$

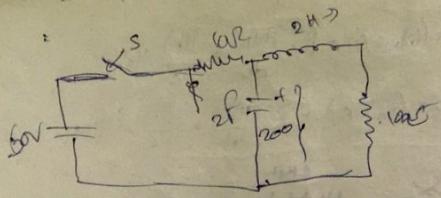

$$i_1(t) \times i_0(t) = 100$$

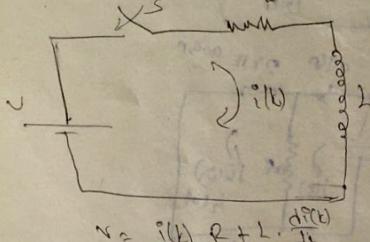

$$v = i_1(t) R + L \cdot \frac{di_1(t)}{dt}$$

Apply Laplace transform

$$\Rightarrow \frac{V}{S} = 2(SR + L \cdot \frac{dI_1}{dt}) [SIB] - i_0(t)$$

$$I(s) = \left\{ R \frac{dV}{ds} \right\} = \frac{N}{S}$$


$$\Rightarrow Z(s) = \frac{V}{S(R+Ls)}$$

$$\Rightarrow Z(s) = \frac{V}{S} \cdot \frac{1}{(SR_1)s + R_0} = 0$$

Applying inverse Laplace.

$$I(s) = \frac{V}{L} \left[\frac{1}{RS} - \frac{1}{R} \cdot \frac{1}{(S+R_1)} \right]$$
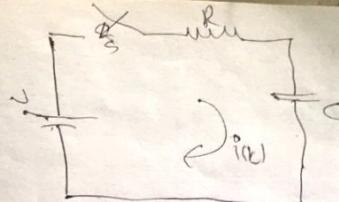
$$i(t) = \frac{V}{R} \times \frac{1}{R} = \frac{V}{R} \cdot \frac{1}{R}$$




$$v = i_1(t) R + L \cdot \frac{di_1(t)}{dt}$$


~~i(t)~~
Apply Laplace.

$$\frac{V}{S} =$$

* Parameters:-

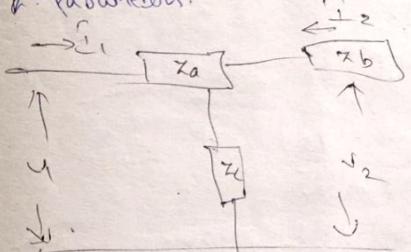

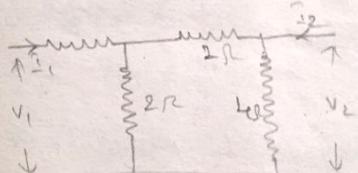Two Port Network (Open Circuit of Z-Parameters)




W.R.T Z-Parameter Eq are

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

When $I_2 = 0$ then V_1 & I_1 is given by

$$V_1 = Z_{11} I_1 \\ \Rightarrow Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

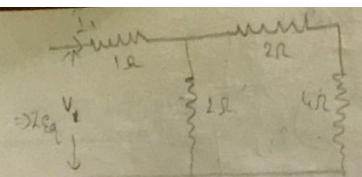


here 2Ω and 4Ω resistors are in series w.r.t V_2
then another 2Ω and 6Ω in parallel with 6Ω

$$Z_{eq} = \frac{4}{1 + \frac{6 \times 2}{6+2}} = 1 + \frac{24}{8} = 2.5 \Omega$$

$$V_1 = I_1, Z_{21} = I_1, 2.5$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 2.5 \Omega$$

now - $Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$

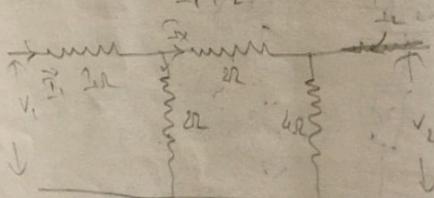

$$V_2 = Z_{21} I_1$$

$$V_2 = 2 I_1$$

$$\therefore Z_{21} = 2 \Omega$$


when port of $Z_2 = 0$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$V_2 = Z_{22} I_2$$

$$V_2 = 6 I_2$$

$$Z_{22} = 6 \Omega$$

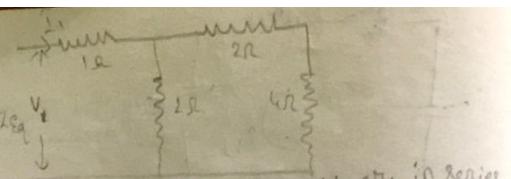

here 2Ω and 4Ω resistors are in series w.r.t V_2
then another 2Ω and 6Ω in parallel with 6Ω


$$Z_{eq} = \frac{4}{1 + \frac{6 \times 2}{6+2}} = 1 + \frac{24}{8} = 2.5 \Omega$$

$$V_1 = I_1, Z_{21} = I_1, 2.5$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 2.5 \Omega$$

now - $Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$

→ Parameter

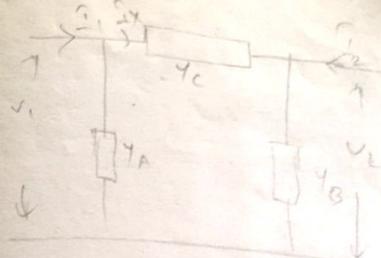

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$Z_{11} \rightarrow$ independent voltage
 $Z_{11} \rightarrow$ calculation

$Z_{21} =$ impedance of Y_B
through I_1

$Z_{22} =$ impedance of Y_A
through I_2

now - $I_2 = 0$

$$V_1 = Z_{11} I_1 \Rightarrow Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{11} = V_1 = I_1 \left(\frac{Y_A + (Y_B + Y_C)}{Y_A + Y_B + Y_C} \right)$$

$$Z_{11} = \frac{Y_A + (Y_B + Y_C)}{Y_A + Y_B + Y_C}$$

$$Z_{21} V_2 = Z_{21} I_1$$

$$Z_{21} = \frac{V_2}{I_1}$$

$$Z_{21} = \frac{Y_C}{Y_A + Y_B + Y_C}$$

$$V_2 = I_1 \times Y_B$$


$$Z_{21} = \frac{Y_C}{Y_A + Y_B + Y_C} \times Y_B$$

when port at $I_2 = 0$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$V_2 = Z_{22} I_2$$
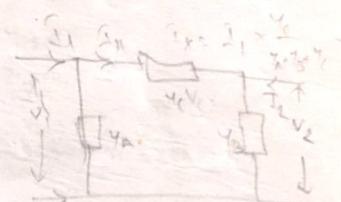
$$V_2 = Y_C \times Y_A \times I_2 \Rightarrow Z_{22} = Y_A + Y_C$$



$$Y_{12} \quad V_1 = I_{12} \cdot Z_2$$

$$Z_{12} = \frac{V_1}{I_{12}} \Big|_{I_{12}=0}$$

$$Z_{12} = \frac{I_1}{Y_A} = \frac{I_2}{Y_B}$$

$$\begin{aligned} V_1 &= Y_A I_1 = I_2 \\ &= Y_A \times \frac{I_2}{Y_B} = I_2 \end{aligned}$$

$$V_1 = I_2$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{V_1}{I_1} = Z_2$$

$$V_1 = Z_{12} I_1$$

The voltage impedance at Y_A is

$$Z_y = Z_2 \times \frac{Y_C}{Y_A + Y_B + Y_C}$$

$$V_2 = Z_y \times Y_A = \frac{Y_C}{Y_A + Y_B + Y_C} \times Y_A$$


$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_2=0} = \frac{Y_C}{Y_A + Y_B + Y_C} \times Y_A$$

Y - PARAMETERS:-

$$Eq \quad Y_{eq} = \frac{V_1}{I_2}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

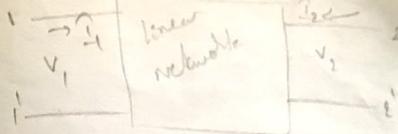

Let V_2 be short circuit

$$I_1 = Y_{11} V_1 \Rightarrow Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$


$$I_2 = Y_{22} V_2 \Rightarrow Y_{22} = \frac{I_2}{V_2} \Big|_{V_2=0}$$

when $V_1 = 0$ we get

$$I_1 = Y_{12} V_2 \Rightarrow Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$I_2 = Y_{21} V_1 \Rightarrow Y_{21} = \frac{I_2}{V_1} \Big|_{V_1=0}$$

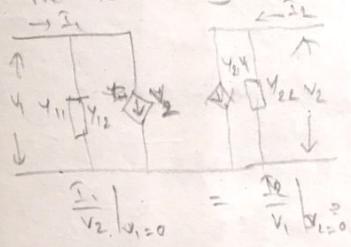
when the circuit of equivalent of two ports



$$\frac{I_1}{V_2} \Big|_{V_1=0} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = Y_{21}$$

P)

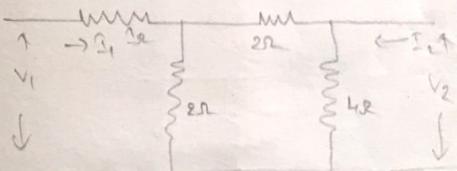


$$The \quad Eq \quad I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

when $V_2 = 0$ we get

$$I_1 = Y_{11} V_1 \Rightarrow Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

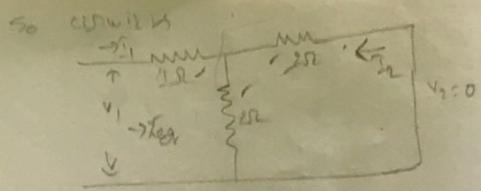

$$\text{Using KVL } V_1 = \frac{1}{2} V_2 + 2I_2$$

$$Z_{\text{eq}} = 2 + 2 + \frac{2V_2}{2+2} = 4 + \frac{V_2}{2} = 2I_2$$

$$V_1 = I_1 \times 2 \Rightarrow I_1 = \frac{V_1}{2}$$

$$\therefore Y_1 = \frac{I_1}{V_1} = \frac{I_1}{2I_2} = \frac{1}{2} \Omega$$

$$\text{Now: } Y_{21} = \frac{I_2}{V_1} \Big|_{V_1=0}$$

Impedance through 2 ohm


$$Y_2 = \frac{1}{2} \times \frac{1}{2} = \frac{1}{4} \Omega \quad (\because I_1 \text{ is zero})$$

$$-I_2 = V_2 \times \frac{1}{2} \quad (\because I_1 = \frac{V_1}{2})$$

$$-I_2 = \frac{V_1}{2} \times \frac{1}{2} = \frac{V_1}{4}$$

$$Y_{21} = -\frac{1}{4} \Omega$$

When $V_1 = 0$

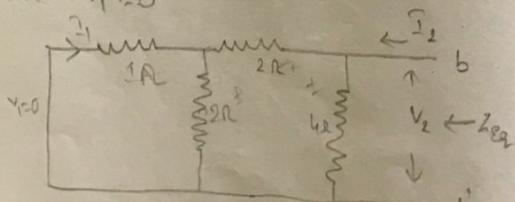

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

$$V_2 = I_2 \cdot Z_{\text{eq}}$$

$$V_2 = -I_2 \times \frac{(4+6)}{4+6} = -I_2 \times \frac{10}{10} = -I_2$$

$$Z_{\text{eq}} = \frac{(2+2+6)}{(1+2+2)} = \frac{8}{5} \Omega$$

$$V_2 = I_2 \times \frac{8}{5}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{8}{5} \Omega$$

$$\text{when ab' shorted} \quad -I_1 = \frac{2}{5} I_2$$

$$I_2 = \frac{5}{8} \times V_2$$


$$-I_1 = \frac{2}{5} \times \frac{5}{8} \times V_2$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{1}{6} \Omega$$


$$\therefore \text{The } \delta_V \text{ is } \delta_V = 0.5 V_1 - 0.25 V_2$$

$$I_2 = -0.25 V_1 + 0.625 V_2$$

b) Given Problem - Circuit

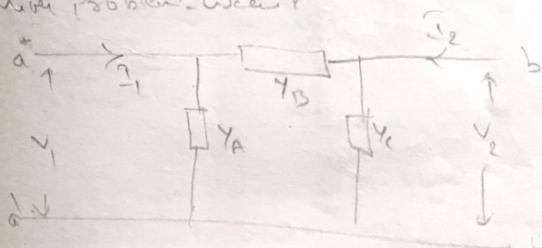

When $b'b'$ is shorted then

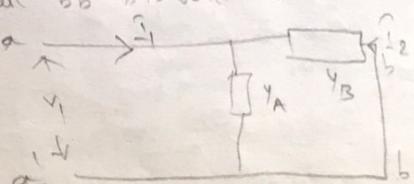

No eq of Y-parameter

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

where $V_2 = 0$ then

$$I_1 = Y_{11} V_1 \Rightarrow Y_{11} = \frac{V_1}{I_1}$$

$$\therefore V_1 = I_1 \cdot Z_{eq}$$

$$V_1 = I_1 \times \frac{Y_A + Y_B}{Y_A \cdot Y_B}$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{Y_A(Y_A + Y_B)}{Y_A \cdot Y_B} = \left(\frac{Y_A + Y_B}{Y_A \cdot Y_B} \right)$$

$$I_2 = Y_{21} V_1$$

$$Y_{21} = \frac{I_2}{V_1} =$$


$$V_1 = -I_2 = I_1 \times \frac{Y_B}{Y_A + Y_B}$$


$$-I_2 = \left(\frac{Y_A + Y_B}{Y_A \cdot Y_B} \right) \times \left(\frac{Y_B}{Y_A + Y_B} \right)$$

$$-I_2 = \frac{Y_B}{Y_A \cdot Y_B} = \frac{1}{Y_A}$$


$$I_2 = -\frac{1}{Y_A}$$
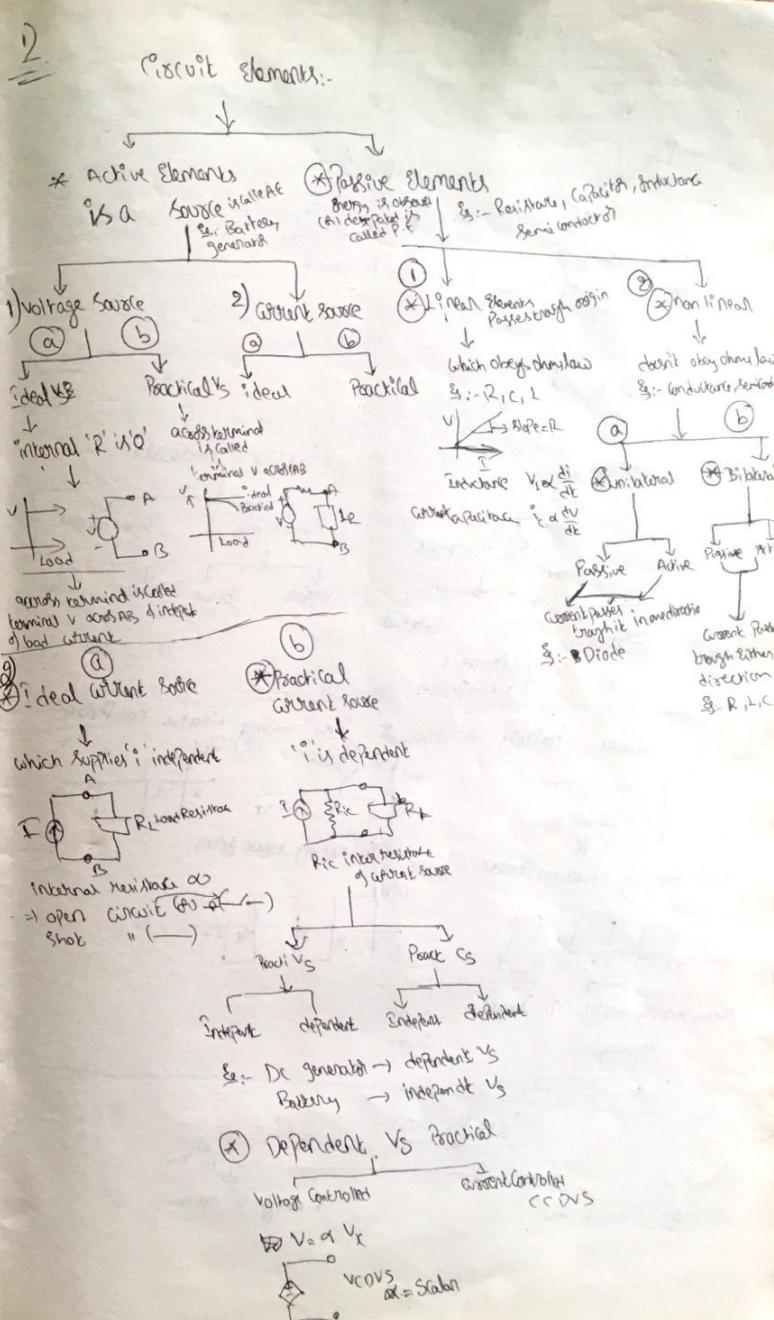
$$Y_{21} = \frac{I_2}{V_1} = -\frac{1}{Y_A}$$




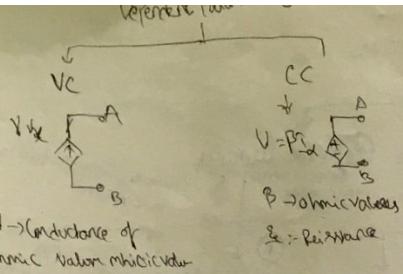


CCDS:-

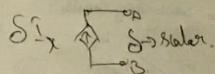


Active Elements

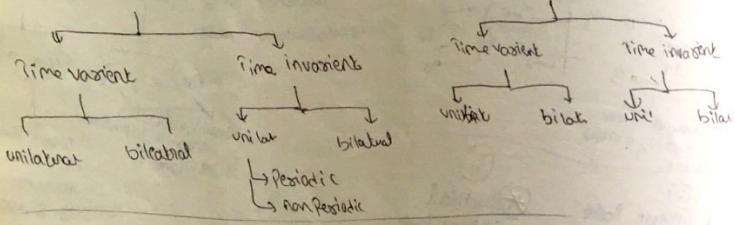

e.g. Time varying: battery

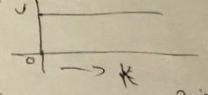

time varying unilateral periodic

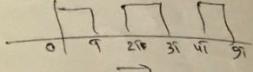

time varying unilateral non-periodic




Kirchoff's law:-


$\sum I = 0$

Kirchoff's current law


Pассивные элементы

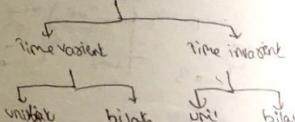

e.g. Time varying bilateral non-periodic

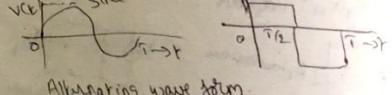

Alternating wave form

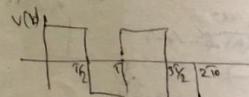

Kirchoff's voltage law

i) Kirchoff's Current law:- Any electrical net consisting of linear, bilinear, passive, active elements. the algebraic sum of the currents through the elements meeting at a particular junction at node is zero


$$i_1 + i_2 + i_3 - i_4 = 0$$

Sum of currents entering a node = Sum of currents leaving a node

Sign convention:- Current entering is +ve and
" leaving " -ve



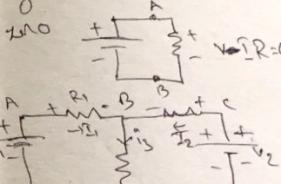ii) Law:- (Same as up to active elements from above KCL) The algebraic sum of source potential drop across the elements in any closed loop is zero



(around triangle ABC)

Sign convention:- In any branch, where one encounter -ve to +ve, it is taken as voltage raise & sign is taken as +ve. If +ve to -ve it is taken as voltage fall & sign is taken as -ve

$$V_1 - i_1 R_1 - i_3 R_3 = 0$$

$$i_3 R_3 + i_2 R_2 - V_2 = 0$$

$$DABC: V_1 - i_1 R_1 + i_2 R_2 - V_2 = 0$$

Dc - Circuit Analysis

Net Work

Analyses:-

Formulae:-

Chapter 1:-

Voltage:-

$$V = \frac{W}{Q} \quad (\text{SI})$$

Current:-

$$I = \frac{Q}{t} \quad (\text{SI})$$

Power:-

$$P = \frac{W}{t} \quad (\text{SI})$$

Energy:-

$$P = \frac{dW}{dt} = \frac{dW}{dt} \times \frac{dq}{dt} = V \cdot I \cdot W$$

Resistance:-

$$I = \frac{V}{R} \Rightarrow V = IR \quad (\text{SI})$$

Power observed:-

$$P = Vi = (IR)I = I^2 R$$

Energy lost:-

$$W = \int P dt = \int I^2 R dt = \frac{V^2}{R} t$$

Inductance:-

$$V = L \cdot \frac{di}{dt} \Rightarrow di = \frac{1}{L} \cdot V dt$$

on integrating we get

$$i(t) = \frac{1}{L} \int_0^t V dt + i(0)$$

Power observed:- $P = Vi \Rightarrow L i \cdot \frac{di}{dt}$

Energy stored:- $W = \int_0^t L i \cdot \frac{di}{dt} dt = \frac{L i^2}{2}$

Capacitance

Parameter:-

$$C = \frac{Q}{V}; \quad C = \frac{Q}{V}$$

$$i = C \cdot \frac{dv}{dt}; \quad dv = \frac{1}{C} \cdot idt$$

on integrating:-

$$v(t) = \int_0^t idt + v(0)$$

Power observed:- $P = Vi \Rightarrow Vc \cdot \frac{dv}{dt}$

$$\text{energy stored}:- W = \frac{1}{2} CV^2$$

Kirchhoff's Voltage Law:-

$$V_{\text{GE}} = V_1 + V_2 + V_3$$

$$I = \frac{V}{R_1 + R_2 + R_3}$$

Kirchhoff's Current Law:-

$$I_1 + I_2 + I_3 = I_T$$

Parallel Resistance:-


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_m}$$

Current division:-


$$I_i = \frac{R_T}{R_1 + R_T} I_T$$

Star delta transformation:-

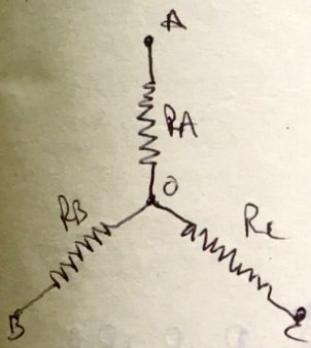It is useful for solving complex networks. Basically, any circuit elements i.e. resistive, inductive (L) capacitive may be connected in two different ways. One way of connecting these elements is called the star connection or Y-connection. The other way of connecting these elements is called delta (Δ) connection. These connections are said to be Star connection.



Star circuit

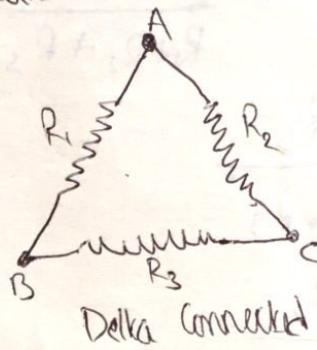

Delta connected

In " " the resistance from terminals AB, BC and AC are respectively.

$$R_{AB} (Y) = R_A + R_B$$

$$R_{BC} (Y) = R_B + R_C$$

$$R_{CA} (Y) = R_C + R_A$$

seen from terminals
AB, BC, and CA respectively are

$$R_{(AB)} \Delta = R_1 \parallel (R_2 + R_3) = \frac{R_1 \times (R_2 + R_3)}{R_1 + R_2 + R_3}$$

$$R_{(BC)} \Delta = R_3 \parallel (R_1 + R_2) = \frac{R_3 \times (R_1 + R_2)}{R_1 + R_2 + R_3}$$

$$R_{(CA)} \Delta = R_2 \parallel (R_1 + R_3) = \frac{R_2 \times (R_1 + R_3)}{R_1 + R_2 + R_3}$$

R_(CA)

Net work analysis:-

(a) Resistance: -

in terms of current $i = \frac{v}{R}$
in terms of voltage $v = R \frac{di}{dt}$

$$i = \frac{v}{R} \quad (\because i = \frac{dq}{dt})$$

Power observed through resistor $P = vi = (ir)i = i^2 R$

most. Energy lost in resistance in time 't' is
 $W = \int_0^t P dt = \int_0^t i^2 R dt = \frac{v^2 t}{R}$

(b) Inductor: -

in terms of voltage $v = L \cdot \frac{di}{dt}$

$$di = \frac{1}{L} \cdot v \cdot dt$$

by integrating on B.S.

$$\int_0^t di = \int_0^t \frac{1}{L} \cdot v \cdot dt$$

$$(i(t)) - (i(0)) = \frac{1}{L} \int_0^t v \cdot dt$$

$$i(t) = \frac{1}{L} \int_0^t v \cdot dt + i(0)$$

Power observed by inductor is

$$P = vi = L \cdot \frac{di}{dt} \text{ work.}$$

Energy stored by inductor is

$$W = \int_0^t P dt = \int_0^t L \cdot \frac{di}{dt} dt = \frac{L i^2}{2} t.$$

Capacitance :-

$$\therefore C = \frac{Q}{V} \quad i \cdot C = \frac{q}{V}$$

in terms of current $i = \frac{C}{V} \frac{dv}{dt}$

" " " voltage $dv = \frac{1}{C} \cdot i dt$

Integrating B.S. we have


$$\int_0^t dv = \frac{1}{C} \int_0^t i \cdot dt$$

$$v(t) - v(0) = \frac{1}{C} \int_0^t idt$$




$$v(t) = \frac{1}{C} \int_0^t idt + v(0)$$

The Power observed by capacitor is given by $P = vi = V C \frac{dv}{dt}$
The energy stored by capacitor is $W = \int_0^t P dt = \int_0^t V C \frac{dv}{dt} dt$

$$W = \frac{1}{2} CV^2$$

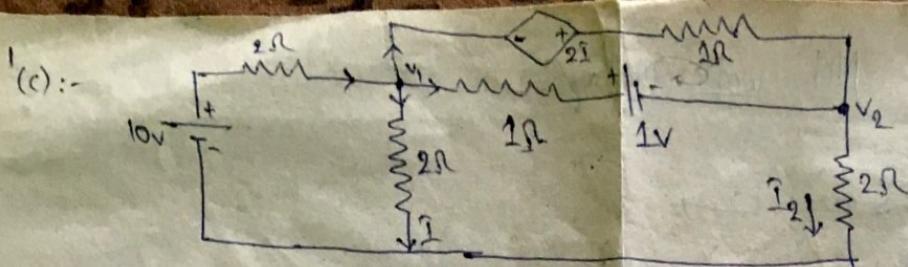
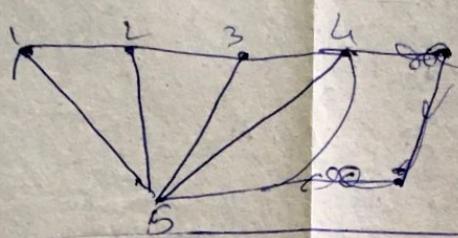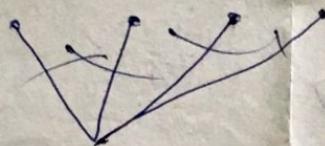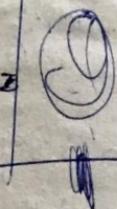
$$\frac{V_1 - 10}{2} + \frac{V_1}{2} + 2I + \frac{V_1 - 0}{1} + \frac{V_1}{1} - 2I = \frac{V_1 - 1}{2}$$



KVL find out:-

first write the given Ckt 'Eq'.
and then both write in matrix form. as

$$A \begin{Bmatrix} I \\ I_1 \\ I_2 \\ I_3 \end{Bmatrix} = B \quad \text{currents going out.}$$

$$A = \begin{bmatrix} 1 & 2 & 3 \\ 0 & 5 & 6 \\ 2 & 8 & 9 \end{bmatrix} \begin{Bmatrix} I_1 \\ I_2 \\ I_3 \end{Bmatrix} = \begin{Bmatrix} 1 \\ 2 \\ 3 \end{Bmatrix}$$

ob A = 'A'

now from Grammer's rule

$$A_1 = \begin{Bmatrix} 0 & 2 & 3 \\ 1 & 5 & 6 \\ 2 & 8 & 9 \end{Bmatrix}; \quad A_2 = \begin{Bmatrix} 1 & 3 \\ 4 & 6 \\ 7 & 9 \end{Bmatrix}; \quad A_3 = \begin{Bmatrix} 1 & 2 \\ 9 & 5 \\ 7 & 8 \end{Bmatrix}$$

$$\therefore i_1 = \frac{A_1}{A}; \quad i_2 = \frac{A_2}{A}; \quad i_3 = \frac{A_3}{A}.$$

KCL find out:-

let write given Ckt and currents 'I' flowing in it
with given voltage

$$\therefore I_1 = \frac{V}{R} = \frac{V}{2}; \quad I_2 = \frac{V}{3} \quad ; \quad \text{given current.}$$

$$\therefore I = I_1 + I_2 + I_3$$

$$I = \frac{V}{2} + \frac{V}{3} + \dots$$

$$10 = \frac{V}{2} + \frac{V}{3} + \dots \text{ solve we get } V$$

Well:-

While the $i_1 = \dots ; v_1 = \dots ; R$

$$P_1 = i_1 v_1 ; \quad (\because v = iR)$$

$$P = i^2 R ; \quad P = \frac{V^2}{R} ; \quad P_2$$

find out above relation from given C.R and then

and total Power :- $P = P_1 + P_2 + P_3$


$$P = (i_1 v_1) + (i_2 v_2) + \dots$$

Chapter:-


Tree:-

A tree do not consist a closed loop

Ex:- Given:-

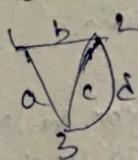

we can draw a tree in no. of ways

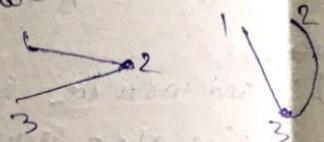

1

2

3

'tree' contains 'n' nodes

$$\text{branches} = n - 1$$


in above C.R there are
3 nodes

$$3 - 1 = 2 \text{ branches}$$


\therefore branches =

Wings & Links:-

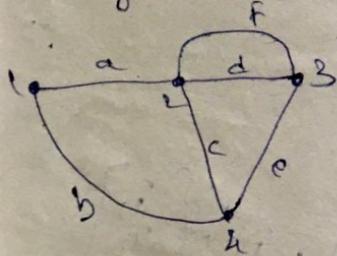
Wings :- Branches of tree are known as wings




Wings are

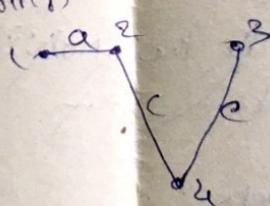

Links in f

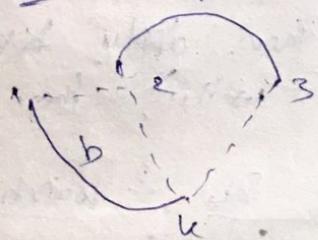


Index matrix:-

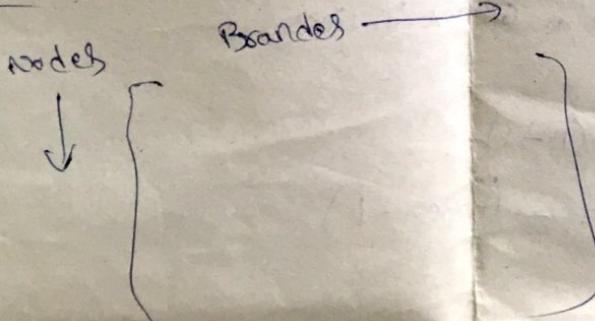



moving both in same direction
means +ve
opposite means -ve
in a loop

Graphical Representation:-

Given Ckt as

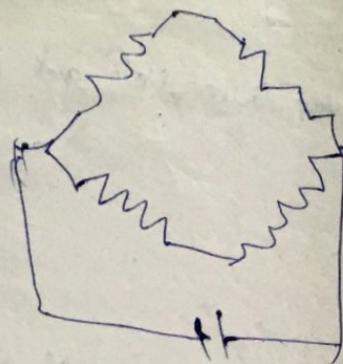

We can draw in

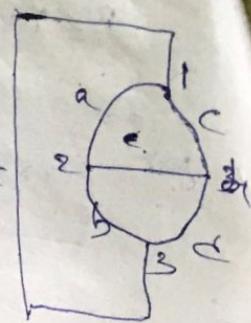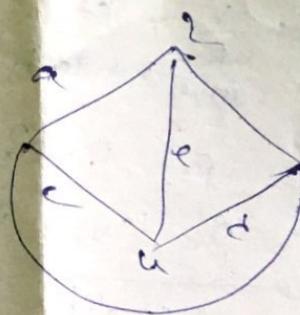

tie - cut matrix:-

First Draw the given Ckt in the graph form.

Locate the nodes & branches

Take them in matrix form using above erwike in matrix form
nodes Branches →

$$BV_b = 0$$

$$\begin{bmatrix} \dots \\ \dots \\ \dots \end{bmatrix}$$

Then take one-one loop and indicate the directions by Current flowing through it

If both i and direction are in same then 'i'

• Opposite '-'

Then apply KV L to the Matrix by striking the equation going

Tie - cut & branch currents:-

$$\text{Find } I_b \rightarrow I_b = B^T I_L$$

Current in Branches = ^{Branch} Matrix \times Current in Links


$$I_b = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}; I_L = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

No of Link Branch $I_L = b - (n - 1)$

$$I_L = \text{branch} - (\text{nodes} - 1)$$

Q.L.S.E.

Ex:-

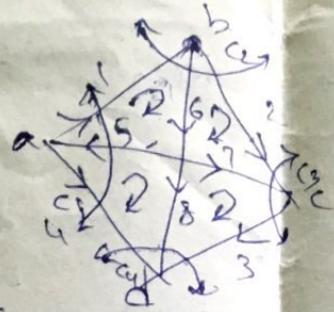

If $c_1 = \{1, 4, 5\}$ are cutted



Colour moving

$$c_2 = \{1, 6, 2\} \quad " \quad "$$

$$c_3 = \{2, 3, 7\} \quad " \quad "$$

$$c_4 = \{4, 5, 8\} \quad " \quad "$$

now apply KCL eq to above by moving the direction form

$$c_1 = i_1 - i_5 - i_4 = 0$$

$$c_2 = i_2 - i_6 + i_1 = 0$$

$$c_3 = \text{Same way}$$

Then write in matrix

$$\begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ c_1 & 1 & 0 & 0 & 0 & -1 & -1 & 0 & 0 \end{matrix}$$

$$\begin{cases} c_2 \\ c_3 \\ c_4 \end{cases} = \begin{cases} 1 \\ 1 \\ 1 \end{cases}$$

$$Q \leftarrow b = 0$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Mesh analysis:-

Draw Given K_C
Adding i_1, i_2, i_3, i_4 ... current from loop equation

Super mesh

finding, i_1, i_2 , currents using loop eqn.


Nodal Analysis:

Draw the circuit at any point.
Locate the node

Write eqn as

$$\text{Eqn: } -6 + \frac{v_1 - 0}{12} + \frac{v_1 - 0}{8} + \frac{v_1 - 0}{3} = 0$$

Super nodal Analysis:

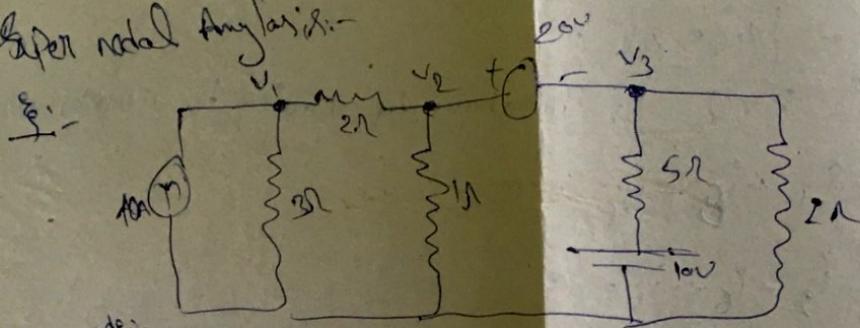

Sink node:

$$\frac{v_1}{3} + \frac{v_1 - v_2}{2} = 10$$

$$v_1 \left[\frac{1}{3} + \left(1 - \frac{1}{2} \right) \right] = 10$$

$$0.83v_1 + 0.5v_1 - 0.5v_2 = 10$$

$$1.33v_1 - 0.5v_2 = 10$$

2nd node:

$$\frac{v_2 - v_1}{2} + \frac{v_2}{1} + \frac{v_3 - 10}{5} + \frac{v_3}{2} = 0$$

$$v_3 - v_2 = 20V$$

$$0.5v_2 - 0.5v_1 + v_2 + 0.2v_3 - 2 + 0.5v_3 = 0$$

$$1.5v_2 + 0.7v_3 - 0.5v_1 - 2 = 0$$

Dual & duality:

(R) Resistance - Conductance (G)

(L) Inductance - Capacitance (C)

Voltage source - Current source


(V) Voltage - Current (I)

Open - Short

Series - Parallel

k_{VL} - ICC

Thevenin - Norton

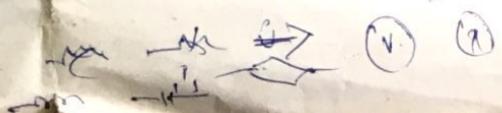

UNIT - II:

Magnetic Circuits:-

Flux density :- (B)

$$B = \frac{\Phi}{A} \text{ wb/m}^2 \text{ (SI) tesla}$$

Dot Conventions:- → Ensuring '+' when writing 'eg' we

should write opposite current in metal induces

$$\text{Q:- } V_1 = L_1 \frac{di}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di}{dt} + M \frac{di_1}{dt}$$

Coefficient of coupling:- $k = \frac{M}{\sqrt{L_1 L_2}}$

Maximum mutual inductance

$$M = k \sqrt{L_1 L_2}$$

Ideal Transformer.

Series Connection of Coupled Circuits

$$L = L_1 + L_2 + 2M \text{ both giving '+}'$$

Parallel :-



$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

Flux :- (Φ) wb

$$\text{Flux density :- } B = \frac{\Phi}{A} \text{ wb/m}^2 \text{ (SI) } B = M \cdot H = 4\pi \times 10^{-7} \times H$$

magnetic motive force:- $MMF = NI$

magnetic field :- $H = \frac{MMF}{l}$

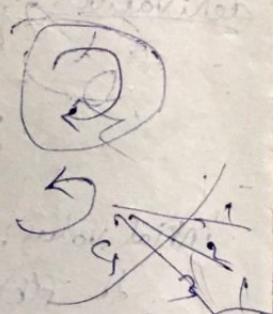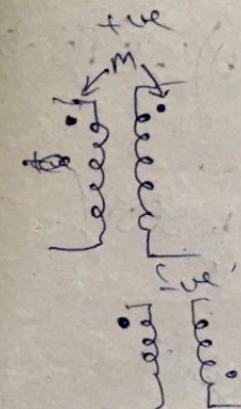

$$C_2 = \{1, 2, 3\} \text{ as } C_2 \{ \}$$

The total energy stored in system t=0' is

$$W(t) = \frac{1}{2} L_1 [i_1(t)]^2 + \frac{1}{2} L_2 [i_2(t)]^2 - M [i_1(t) \cdot i_2(t)]$$

Unit - 18

c) DC Response of RL circuit

$$i = \frac{V}{R} \left(1 - \exp\left(-\frac{R}{L}t\right) \right)$$

Laplace transform :-

$$\text{Current} : - \frac{e^t f e^{-st}}{2}, \text{ & source} = \frac{e^t - e^{-st}}{2i}$$

1.1 Periodic functions

$$L\{f(t)\} = \frac{1}{1 - e^{-st}} \int_0^T f(t) \cdot e^{st} dt$$

derivatives :-

$$L\{f'(t)\} = Sf(s) - s f(0)$$
$$L\{f''(t)\} = S^2 f(s) - Sf(0) - sf'(0)$$

Atrial value :-

$$\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} Sf(s)$$

final value

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} Sf(s)$$

Chapter: 53'

Theorem:-

Superposition

current - open circ \rightarrow I

voltage - short it

If current is opened then find out currents of load current by
case (i) doing equivalent resistance

Case (i):-

Thévenin's :-

first make open ckt
find shortcircuit path and where the 'i' is to be find in resistor
find $V_{th} = i_2 \times R$

Then make the ckt short the voltage and find R_{th}

$$R_{th} =$$

Then replace the ckt from the voltage, current, and removed resistor
then find 'i' at removed resistor using voltage division rule

points:-

find place shortcircuit
same above procedure

$$\text{frequency } f = \frac{1}{T}$$

$$V(t) = V_m \sin \omega t$$

$$\text{Time } T = \frac{1}{f}$$

$$\therefore V(t) = V_m \sin(\omega t + \phi) \text{ when left side}$$

$$\text{Avg value : } V_{av} = \frac{1}{T} \int_0^T V(t) dt$$

$$\uparrow V(t) = V_m \sin(\omega t - \phi) \text{ Right side}$$

$$\text{Rms value } V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt} \quad (\text{or}) \quad V_{rms} = \frac{V_p}{\sqrt{2}}$$

$$\text{Peak factor : } = \frac{V_p}{V_{rms}} = \frac{V_p}{V_p/\sqrt{2}}$$

$$\text{Form factor : } = \frac{V_{rms}}{V_{av}}$$

Phase relation in pure resistance:-


$$V(t) = i(t)R$$

$$i(t) = i_m \sin \omega t$$

$$V_m = I_m R$$

$$\text{Impedance : } Z = \frac{V_m 2^\circ}{I_m 2^\circ} = R$$

Superposition Th:-

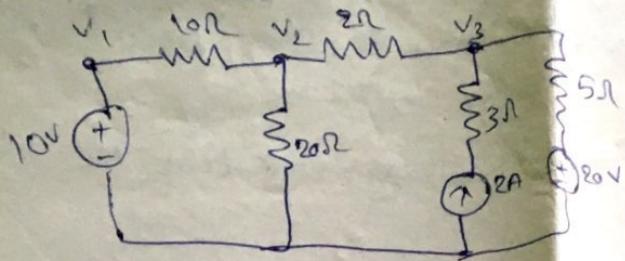

Node V_1 :

$$\frac{V_1}{10} + \frac{V_1 - V_2}{10} = 0$$


$$2V_1 - V_2 = 0$$

$$2V_1 = V_2$$

Node V_2 :

$$\frac{V_2 - V_1}{10} + \frac{V_2}{20} + \frac{V_2 - V_3}{5} = 0$$
~~$$10V_2 - 10V_1 + 5V_2 + 50V_2 - 50V_3 = 0$$~~
~~$$10V_2 - 10V_1 + 10V_2 + 100V_1 - 50V_3 = 0$$~~
~~$$100V_1 + 50V_3 + 10V_2 = 0$$~~
~~$$100V_1 + 10V_2 - 50V_3 = 0$$~~
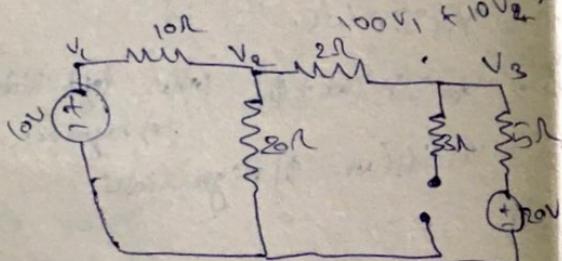
$$\left\{ \begin{array}{l} 10, 20, 2 \\ 5, 10, 1 \end{array} \right.$$



$$\frac{V_1}{10} + \frac{V_1 - V_2}{10} = 0$$

$$2V_1 = V_2$$

$$\frac{V_2 - V_1}{10} + \frac{V_2}{20} + \frac{V_2 - 20}{5} = 0$$

$$\left\{ \begin{array}{l} 5, 10, 20 \\ 1, 2, 4 \end{array} \right.$$

$$\frac{2V_2 - 4V_1 + 2V_2 + 8V_2 - 160}{40} = 0$$

$$6V_2 - 4V_1 = 160$$

$$28V_1 - 4V_1 = 160$$

$$24V_1 = 160$$

$$V_1 = \frac{160}{24} = 6.66$$

phase relation in RLC circuit

Chapter - 5

$$V(L) = L \cdot \frac{di}{dt}$$

$$V_m = WLIm$$

$$= X_L Im$$

Capacitive reactance $X_C = \frac{1}{2\pi f C} \quad (\because \omega = 2\pi f)$

$$X_C = \frac{1}{\omega C}$$

$$X_L = \omega L$$

Series RL circuit find $X_L = \omega L = 2\pi f L$

Total impedance formula $Z = R + j\omega L$

$$\Rightarrow Z = \sqrt{R^2 + X_L^2} \quad X_L = \omega L$$

$$\text{Current } I = V_s/Z$$

$$\text{Phase angle } \theta = \tan^{-1}\left(\frac{X_L}{R}\right)$$

Polar form total impedance $Z = ZL^\circ$

Series RC circuit :-

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

Total impedance $Z = R + j\omega L$

$$Z = \sqrt{R^2 + X_C^2}$$

$$\text{Current } I = \frac{V_s}{Z}$$

$$\theta = \tan^{-1}\left(\frac{X_C}{R}\right)$$

Polar \Rightarrow

Series RLC circuit :-

$$X_C ; X_L$$

Total impedance :- $Z = (R + jX_L - jX_C)$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta = \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$

$$V_s \quad I = \frac{V_s}{Z} - \text{flowing voltage in phasor } Z$$

$$V_R = IR =$$

$$IX_C =$$

$$IX_L =$$

then CR circuit

RC Circuit :-

$$X_C = \frac{1}{2\pi f C}$$

$$I_R = \frac{V_s}{R} \quad , \quad I_C = \frac{V_s}{X_C}$$

$$\text{Total current. } (I_R + I_C) * =$$

$$Z = \frac{V_s}{I_R} =$$

RL circuit

$$I_R = \frac{V_s}{R} \quad , \quad I_L = \frac{V_s}{X_L}$$

$$I_T = I_R + I_L$$

$$Z = \frac{V_s}{I_T}$$

Compound circuit :-

$$Z_T = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3}$$