

## Circuit Elements and Kirchhoff's laws:-

1.1 Voltage:- A certain amount of energy (work) is required to overcome the force and move the charges through a specific distance.

$$V = \frac{W}{Q} \quad (\text{or}) \quad V = \frac{dW}{dq}$$



Problem:- If 10 Joule of energy is available for 30 Coulombs of charge what is voltage

$$V = \frac{W}{Q} = \frac{10}{30} = 2.33V$$

### 1.2:- Current:-

$$I = \frac{Q}{t} \quad (\text{or}) \quad i = \frac{dq}{dt}$$

Problem:- 5 Coulomb of charge flow past a given point in a wire in 2 seconds how many amperes of current flowing.

$$I = \frac{Q}{t} = \frac{5}{2} = 2.5A.$$

### 1.3:- Power & Energy:-

Power is the rate of change of energy if certain amount of energy is used over a certain length of time

$$\text{Power (P)} = \frac{\text{Energy}}{\text{Time}} = \frac{W}{t}; P = \frac{dW}{dt}$$

We can also write:  $P = \frac{dw}{dt} = \frac{dw}{dq} \times \frac{dq}{dt}$

Problem:- what is the power in watts if energy

equal to 50J is used in 2.5s?

$$P = \frac{\text{Energy}}{\text{Time}} = \frac{50}{2.5} = 20 \text{ W.}$$

1.5:- Resistance Parameter:- (R): The property of a material to restrict the flow of electron is called resistance, denoted by R.

$$I = \frac{V}{R}; i = \frac{V}{R}$$

$$V = R \cdot \frac{dq}{dt} \quad (\because i = \frac{dq}{dt})$$

$$i = \frac{V}{R} = GV$$

Units:-

Resistance :- ohms ( $\Omega$ )

Conductance :- mho ( $\sigma$ )

Power dissipated by the resistor is

Energy lost by resistance in time  $t$  is given by

$$W = \int P dt = Pt = i^2 R t = \frac{V^2}{R} t.$$

Problem:- A  $10\Omega$  resistor is connected across a battery how much current flows through the resistor

$$V = IR$$

$$I = \frac{V}{R} = \frac{12}{10} = 1.2A.$$

Inductance Parameter:- back side of the book

Problem:- The current in a  $2H$  inductor varies at a rate of  $2A/s$ . Find the voltage across the inductor and energy stored in magnetic field after  $2s$

$$V = L \frac{di}{dt} = 2 \times 4 = 8V$$


$$W = \frac{1}{2} L i^2 = \frac{1}{2} \times 2 \times (2)^2 = 16J.$$

Capacitance Parameter:- BS-0-B

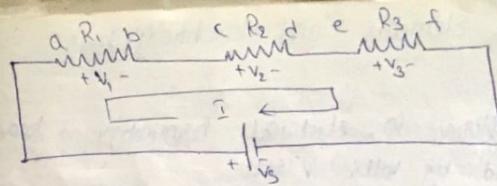Problem:- A capacitor having a capacitance  $2\text{MF}$  is charged to a voltage of  $1000V$ . Calculate stored energy in Joules.


$$W = \frac{1}{2} C V^2 = \frac{1}{2} \times 2 \times 10^{-6} \times (1000)^2 = 1\text{Joule}$$

Kirchhoff's Voltage Law (KVL):- The algebraic sum of all branch voltages around any closed path in a circuit is always zero at all instants of time



$$Vs = V_1 + V_2 + V_3$$

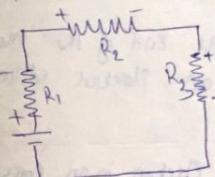Assume the reference current direction and to indicate the polarities for different elements.



By using Ohm's law, voltage across each resistor as follows

$$V_{R1} = IR_1, V_{R2} = IR_2, V_{R3} = IR_3$$

where  $V_{R1}$ ,  $V_{R2}$  and  $V_{R3}$  are the voltages across  $R_1$ ,  $R_2$  &  $R_3$  respectively. Finally by applying Kirchhoff's law's we can form the

$$V = V_{R1} + V_{R2} + V_{R3}$$

$$V = IR_1 + IR_2 + IR_3$$

from the above eq the current delivered by both is given by

$$I = \frac{V}{R_1 + R_2 + R_3}$$

Problem:- In last book

Voltage division:- The voltage dropped across any resistor in a series circuit is equal to the ratio of that resistance value to the total resistance, multiplied by the total voltage

$$V_m = \frac{V_s(R_m)}{R_1 + R_2 + \dots + R_m}$$

## Circuit elements and kirchhoff's laws.

### Voltage:-

Potential difference in electrical terminology is known as voltage. Denoted by volts V (V)

It is expressed in terms of energy (W) per unit charge (q)

$$V = \frac{W}{Q} ; \text{ or } V = \frac{dw}{dq}$$

### Current:-

Movement of electrons from one end of the material to the other end constitutes an electric current denoted by I (A)

It is defined as rate of flow of electron in an conductivity measured by no. of electrons that flow past a point in unit time.

$$I = \frac{Q}{t} \quad (\text{or}) \quad i = \frac{dq}{dt}$$

Resistance:- The property of material to resist the flow of electrons through the conductor is called as a resistance.

It is denoted 'R' (Ω)

Units:- ohms (Ω)

$$\text{Ohm's law} \quad I = \frac{V}{R} \quad (\text{or}) \quad i = \frac{v}{R}$$

$$\text{Power dissipated} \quad P = IR \quad (\text{or}) \quad V^2 = iR$$

~~Energy~~ in resistance for time t is

$$\therefore P = V^2 = i(iR) = i^2 R$$

By ~~integating~~ in time t, it is

$$W = \int P dt = i^2 R t = i^2 R t = \frac{V^2}{R} t$$

### Power and Energy:-

Energy:- Energy is the capacity for doing work, and it is nothing but stored work. It may exist in many forms such as mechanical, chemical, electrical and so on.

Energy measured in Joules (J).

Power:- It is a rate of change of energy and denoted by Power P (W)  $\neq$  P. If certain amount of energy is used over a certain length of time then

$$\text{Power (P)} = \frac{\text{Energy}}{\text{Time}} = \frac{W}{t}$$

$$P = \frac{dw}{dt}$$

where dw is change in energy and dt is change in time

$$P = \frac{dw}{dt} = \frac{dw}{dq} \times \frac{dq}{dt}$$

$$= V \times i$$

$$P = Vi \cdot W$$

over time in seconds (S) Power in watts (W).

### Inductance Parameter:-

A wire of certain length, when twisted in to a coil becomes a basic inductor. If the current is made to pass through an inductor ~~then~~ the electro magnetic field is formed. A change in magnitude of current changes electro magnetic field. Increase in current expands and decrease in current reduces the electro magnetic field. Therefore change in current produces the change in electro magnetic field which induces the voltage across the coil according to faraday's law of electromagnetic induction.

$$V = L \cdot \frac{di}{dt}$$

$$di = \frac{1}{L} \cdot V \cdot dt$$

Integrating on R-S

$$\int_0^t i \, dt = \int_0^t \frac{1}{2} V \, dt$$

$$i(t) - i(0) = \frac{1}{2} \int_0^t V \, dt$$

$$i(t) = \frac{1}{2} \int_0^t V \, dt + i(0)$$

$$i(t) = \frac{1}{2} \int_0^t V \, dt$$

The Power absorbed by inductor is

$$P = Vi = L \frac{di}{dt}$$

The energy stored by inductor is

$$W = \int_0^t P \, dt$$

$$= \frac{1}{2} \int_0^t L \frac{di}{dt} \, dt = \frac{1}{2} i^2$$

### Chapter 1:

Voltage: Current ( $i$ ) - measured in Amperes (A)

$$V = \frac{W}{Q} \quad (i) \quad W = \frac{dQ}{dt}$$

$W$  is energy in Joules (J) charge ( $Q$ ) in Coulombs (C)

Given 70J of energy =  $W$

30 C of charge =  $Q$

$$\therefore V = \frac{W}{Q} = \frac{70}{30} = 2.33V$$

Given current 3A energy  $W = 500J$

Time ( $t$ ) = 12sec

$$V = \frac{W}{Q} \text{ where } Q = It$$

$$Q = 3 \times 12 = 36C$$

$$V = \frac{500}{36} = 13.88V$$

Given  $Q = 75C$   $t = 18$  find  $I$

$$\text{Ans? } Q = It \\ I = \frac{Q}{t} = \frac{75}{18} = 7.5 \text{ Amp}$$

Given  $Q = 10C$ ;  $t = 0.58$  find  $I$

$$Q = It \Rightarrow I = \frac{Q}{t} = \frac{10}{0.58} = 0.2 \text{ Amp}$$

Given  $Q = 5C$  intab find  $t$

$$Q = It \\ \Rightarrow I = \frac{Q}{t} = \frac{5}{2} = 2.5 \text{ Amp}$$

(P) Given  $Q = 10C$ ;  $I = 5A$  find  $t$

$$Q = It \Rightarrow t = \frac{Q}{I} = \frac{10}{5} = 2 \text{ sec}$$

objective: Given  $W = 100J$ ,  $Q = 25C$

$$V = \frac{W}{Q} = \frac{100}{25} = 4V$$

Given  $W = 800J$ ,  $Q = 40C$

$$V = \frac{800}{40} = 20V$$

Given  $Q = 10C$   $t = 0.58sec$

$$Q = It \Rightarrow I = \frac{Q}{t} = \frac{10}{0.58} = 20A$$

1 Coulomb of charge is  $6.25 \times 10^{19}$  electrons.

Power = ~~Work Energy~~  $\frac{Work}{Time} = \frac{Energy}{Time} = \frac{P}{dt}$

$$P = \frac{dQ}{dt} \times \frac{dv}{dt}$$

$$P = V \times i$$

Given  $P = \frac{\text{Energy}}{\text{Time}} = \frac{50J}{2.5} = 20W$

Given  $R = 5\Omega$  here  $R$  is resistive in ohms  $\Omega$

$$V = 100V$$

$$W \propto I^2 = P = I \times V \therefore I = V/R$$

$$\Rightarrow P = \frac{V}{R} \times V$$

$$= \frac{100}{5} \times 100 = 2000W = 2kW$$

1.3.2.2

Given  $I = 2A$ ;  $W = 1000J$ ;  $t = 5sec$

Find 'V' across resistor:-

$$W \propto I^2 R \quad P = \frac{W}{t} = \frac{1000}{5} = 200W$$

$$P = I \times V \quad I = \frac{Q}{t}$$
$$\therefore P = 200 = 2 \times V \quad Q = 2 \times 5 = 10C$$
$$V = 100V$$

$$R = \frac{V}{I} = \frac{100}{2} = 50\Omega$$

$$R = \frac{100}{200} = 0.5\Omega$$

Objectives

$$R = 5.5V; I = 3mA; t = 8.33sec$$

Find 'P'.

$$P = I \times V \quad \text{when } I = \frac{V}{R} \Rightarrow P = \frac{V^2}{R}$$

$$P = 16.5 \times 3$$

$$P = 49.5W$$

units of conductance are mho ( $\Omega^{-1}$ )

Resistance:-

units are ohms ( $\Omega$ )

$$V = IR$$

$$I = \frac{V}{R}$$

$$\text{Given } R = 10\Omega; V = 12$$

$$I = \frac{12}{10} = 1.2A$$

Given:  $V = 180V; I = 0.8A; R = ?$

$$I = \frac{V}{R} \Rightarrow 0.8 = \frac{180}{R}$$

$$R = \frac{180}{0.8} = 225\Omega$$

Inductance Parameter:-

units of inductance is henry ( $H$ )

$$V = L \frac{di}{dt}$$

Given Inductance  $L = 2H; \frac{di}{dt} = 2A/s \times 2sec$

and Energy stored in magnetic field in  $J$

Power absorbed by inductor is

$$P = V \cdot i = \frac{di}{dt} \cdot \frac{V}{L}$$

Energy stored by inductor is

$$W = \int_0^t P \cdot dt = \int_0^t \frac{di}{dt} \cdot \frac{V}{L} dt = \frac{1}{2} L i^2$$

work in Joules (J)

$$V = 2 \times 2 = 8V$$

$$W = \frac{1}{2} L i^2 = \frac{1}{2} \times 2 \times (2)^2 = 16J$$

1.5:

$I = ?$  Current increases at  $0.2A$ .

$$V = 15V$$

$$V = L \cdot \frac{di}{dt} \quad \text{current in } 1S = \frac{0.2}{0.3} = 0.66A$$

Gross charge at rate of  $0.66A/s$

$$I = \frac{V}{(\frac{di}{dt})} = \frac{15}{0.66} = 22.737A$$

1.7 Capacitance Parameter:-

unit are Farad's. (F)

$$C = \frac{Q}{V} \quad (a) \quad C = \frac{q}{\varphi}$$

$$W = \frac{1}{2} CV^2$$

$$C = 2 \mu F$$

$$UF = 10^{-6}$$


$$V = 1000$$

$$W = \frac{1}{2} CV^2 = \frac{1}{2} \times 2 \times 10^{-6} \times (1000)^2 = 1 J.$$


Energy Sources:-

AC to their terminal voltage wrt

electrical energy stores

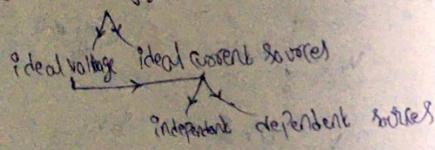

Krichhoff's law voltage law:

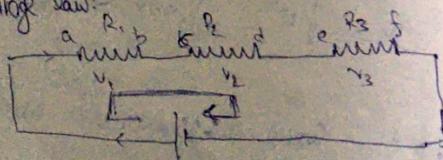

$$V = IR_1 + IR_2 + IR_3$$

$$I = \frac{V}{R_1 + R_2 + R_3}$$

By using ohm law voltage across resistor

$$V_{R1} = IR_1; V_{R2} = IR_2; V_{R3} = IR_3$$

1. 0.3 V

2. 2.5 V

3.  $V_1 = V_2$

4. 0.682 V

5. 1.602

6. 0.7A

7. -4V

8. -1.73V

9. -1.3V

10. -0.7V

11. -0.3V

12. -0.1V

13. -0.05V

14. -0.025V

15. -0.0125V

16. -0.00625V

17. -0.003125V

18. -0.0015625V

19. -0.00078125V

20. -0.000390625V

21. -0.0001953125V

22. -0.00009765625V

23. -0.000048828125V

24. -0.0000244140625V

25. -0.00001220703125V

26. -0.000006103515625V

27. -0.0000030517578125V

28. -0.00000152587890625V

29. -0.000000762939453125V

30. -0.0000003814697265625V

31. -0.00000019073486328125V

32. -0.000000095367431640625V

33. -0.0000000476837158203125V

34. -0.00000002384185791015625V

35. -0.000000012020928955078125V

36. -0.0000000060104644775390625V

37. -0.00000000300523223876953125V

38. -0.000000001502616119384765625V

39. -0.00000000075130805969238125V

40. -0.000000000375654029846190625V

41. -0.0000000001878270149230953125V

42. -0.00000000009391350746154765625V

43. -0.0000000000469567537307738125V

44. -0.00000000002347837686538690625V

45. -0.000000000011739188432693453125V

46. -0.000000000005869594216346725125V

47. -0.0000000000029347971081733625125V

48. -0.00000000000146739855408668125125V

49. -0.000000000000733699277043340625125V

50. -0.0000000000003668496385216703125125V

voltage division

draw duality of circuit in (graph)

chapter 1:-

1) Voltage :-  $V = \frac{W}{Q}$  (a)  $V = \frac{W}{q}$

2) Current:-

$$I = \frac{Q}{t} \quad (a) \quad i = \frac{dq}{dt}$$

3) Power and Energy:-


$$P = \frac{\text{energy by time}}{\text{time}} = \frac{W}{t} \quad (a) \quad P = \frac{dW}{dt}$$

$$P = \frac{dW}{dt} = \frac{dW}{dt} \times \frac{dt}{dt} = V \times i = Vi \text{ W.}$$

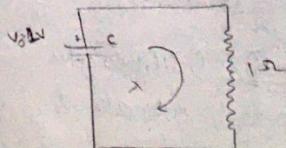4)

Imp :- Chapter - 1:- Spectrom-

30 Given that:- A capacitor charged 1 volt at  $t=0$  resistor  $1-2$  is connected across terminals. The current in the form  $i(t) = e^t \text{ Amp.} \rightarrow ①$  At particular time current drops:- 0.37 Amp



$$i(t) = e^t \text{ Amp.} \quad R = 1 \Omega$$

The current  $i(t)$  is given by

$$i(t) = i(0) \cdot e^{t/R} \rightarrow ②$$

Comparing Eq ② with ① we get

$$i(0) = 1 \text{ & } RC = 1 \Rightarrow C = \frac{1}{R} = \frac{1}{1} = 1 \text{ F}$$

(i)  $i(t) = e^t$

Given  $i(0) = 0.37 \text{ A}$

when  $i(t) = e^t$  so

$$e^t = 0.37 \text{ A}$$

Applying log on both sides

$$\log e^t = \log 0.37$$

$$-t \cdot \log e = \log 0.37$$

$$-t(1) = \log 0.37$$

$$-t = -0.9942$$

$$t = 0.9942 \text{ sec}$$

∴ rate of change of voltage across capacitor is given by

$$\frac{dV(t)}{dt} = \frac{i(t)}{C} = \frac{0.37}{1} = 0.37 \text{ V/sec}$$

(ii) charge on capacitor.

$$Q = CV = 1 \times \frac{i(t)}{R} = 1 \times \frac{0.37}{1} = 0.37 \text{ Coulombs}$$

3) voltage across capacitor:-

$$V_C(t) = e^t = 0.37 \text{ (volt)}$$

4) Energy stored in a capacitor.

$$W_C = \frac{1}{2} CV^2 = \frac{1}{2} \times 1 \times (0.37)^2$$

$$= 0.06845 \text{ Joules}$$

5) voltage across resistor as  $t = 0.9942 \text{ sec}$  is


$$V_R = i(t) \times R = e^t \times 1 = e^t = 0.37 \text{ V}$$

- 2) what are Active, Passive elements? Explain Voltage current relation  
3) Passive elements with Eq:-

A) Active Elements:- The elements which are capable of Providing energy to the devices or networks which are connected across them is called as active elements. Basically there are two kinds


- 1) Independent voltage source
- 2) " Current "

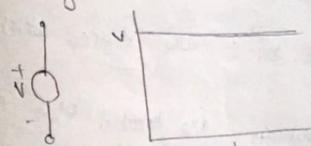1) An independent voltage source is a source in which the voltage across the terminals is independent of current passing through it




v-i characteristic of an ideal source

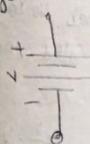The voltage source is formed as a DC voltage source. The voltage source is represented if it has a constant voltage and its




v-i characteristic of practical voltage

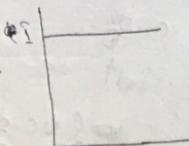2) An independent current source is a source which can deliver a constant current independent of the voltage across its terminals.



v-i of ideal current source

Practically the voltage and current

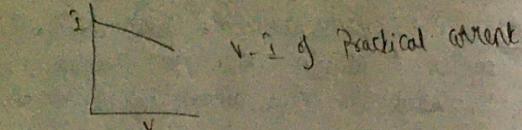


### Passive elements:-

The elements which can not deliver power and can only receive the power are known as passive elements.


There are 3 types of passive elements.

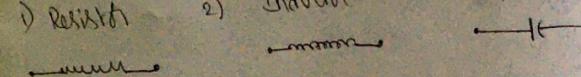- 1) Resistors
- 2) Inductors
- 3) Capacitors




\* The passive elements R, L, C are defined which current and voltage related.

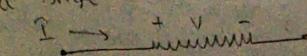(i) If the current I and voltage V are related by a constant for a single element, then element is 'R'.



$$\text{Voltage } V = \frac{P}{I} \Rightarrow I = \frac{V}{R}, \text{ Power } \Rightarrow P = VI = I^2 R$$

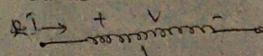(ii) If the current and voltage are related such that voltage is the time derivative of current, then the element is called inductor.



$$V = L \cdot \frac{dI}{dt} \Rightarrow I = \frac{1}{L} \cdot V \cdot dt; \text{ Power } \Rightarrow P = VI = \frac{1}{L} \cdot V^2$$

(iii) If the voltage and current are related such that the current is such that current is the time derivative of voltage. Then it is called capacitor.



$$\text{Current } I = C \cdot \frac{dv}{dt}$$

$$\text{Voltage } V = \frac{1}{C} \cdot \int I dt$$

$$\text{Power } P = VI = VC \cdot \frac{dv}{dt}$$

Ques) A heater element takes 8W of power when connected to mains. The element is cut down such that the length is doubled.

Given:- Let  $P_1$  = Power observed by original R,

$$P_1 = 8W = \frac{V^2}{R_1}$$

$l_1$  = length of heating element

$A_1$  = Area of cross section of heating element

$$P = \frac{l_1}{A_1}$$

$V_1$  = volume of heating element

$$V_1 = l_1 \times A_1$$

Case 2:-

When length is doubled the area will be ~~double~~ halved

$$l_2 = 2l_1$$

$$A_2 = \frac{A_1}{2}$$

$$R_2 = P \cdot \frac{l_2}{A_2}$$

$$R_2 = P \cdot \frac{2l_1}{\frac{A_1}{2}} = P \cdot \frac{4l_1}{A_1} = 4 \cdot R_1$$

Power observed by new element

$$P_2 = \frac{V^2}{R_2} = \frac{V^2}{4R_1}$$


Voltage applied.

$$P_2 = \left( \frac{V^2}{R_1} \right) \times \frac{1}{4} = \frac{8V^2}{4R_1} = 2W.$$

## Net Work Theory:-

### Chapter-2:-

#### 1) field theory:-

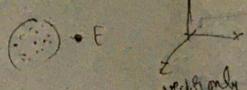

nowadays  
field theory is expand


#### Circuit theory:-

1 MHz 1000 kg 1000

F 1 MHz

(10.001 - 10)  
It will not be expand because it may  
be used in small circuits.

#### 2) Voltage:-

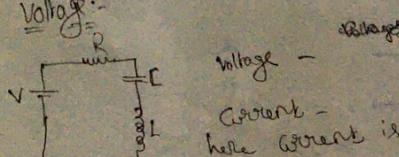

voltage -  
Current -  
here current is constant

#### 3) Current:-

here voltage is constant.

Resistor:  $\frac{V}{R}$

Capacitor:  $\frac{Q}{C}$

Inductor:  $\frac{V}{L}$

$$5 \times 10^8 \text{ c/s}$$

$$5 \times 6 \times 10^{18} \text{ c/s}$$

$$30 \times 10^{18} \text{ c/s}$$

Resistor:  $R$

$\frac{V}{R}$

Power  $P = VI$


$$P = R^2 I^2 = \frac{V^2}{R}$$

$$(or) P = \frac{V^2}{R}$$

$$V = RI \quad \text{Ohm's law}$$

$$I = \frac{V}{R}$$


#### Series:-

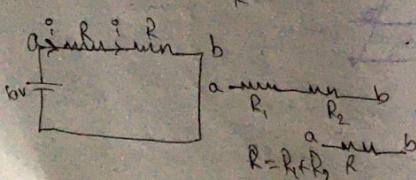

$$R = R_1 + R_2$$

(joined)

## Parallel:-


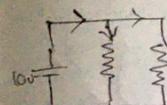


$$R = \frac{R_1 R_2}{R_1 + R_2}$$

(joined)

Current division:- opposite resistance

voltage " :- that "

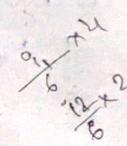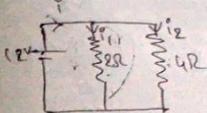


$$i = \frac{V}{R} = \frac{12}{12} = 1A \quad ; \quad i = \frac{12}{36} = 0.33A$$

$$i_1 = i_2 + i_3 \\ i_1 = \frac{V}{R_1 + R_2} \\ = 6 + 3 = 9A$$

$$\text{then } \frac{R_1 R_2}{R_1 + R_2}$$

Current division:-

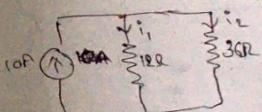

Total current  $\frac{10}{12+36}$  at  $i_1$  &  $i_2$  at  $i_3$


$$R_1 = 12 \Omega, R_2 = 36 \Omega$$

$$R_{eq} = \frac{12 \times 36}{12+36} = \frac{432}{48} = 9 \Omega$$

$$i_1 = \frac{10}{28} \times 36 = \frac{360}{48} = 7.5A$$

$$i_2 = \frac{10}{48} \times 12 = 2.5A$$

Voltage division:-

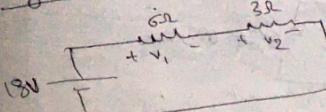


Total voltage  $\frac{18}{6+3}$  at  $v_1$  &  $v_2$

$$\frac{6}{9} \times 6 = 4V$$

$$2 \times 3 = 6V$$


$$R = R_1 + R_2 \\ = 6 + 3 = 9\Omega$$
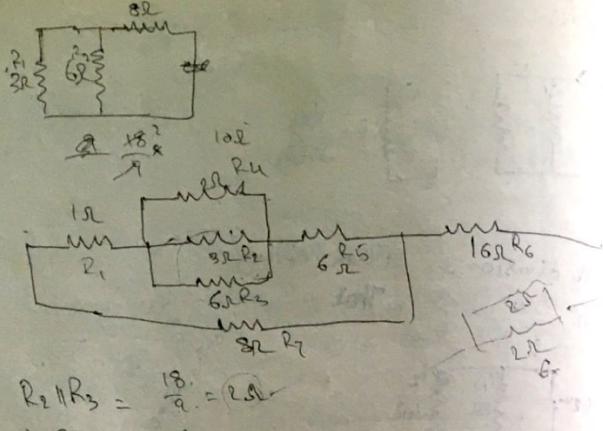
$$I = \frac{18}{9} = 2A \quad ; \quad i_1 = \frac{18}{6} = 3A \quad ; \quad i_2 = 6A \quad ; \quad i_3 = 3A$$




$$R_2 \parallel R_3 = \frac{18}{9} = 2\Omega$$


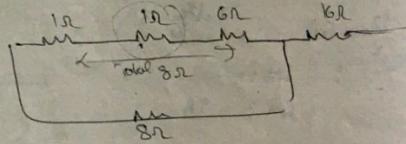
$$(R_2 \parallel R_3) \parallel R_4 = \frac{2 \times 2}{2+2} = 1$$




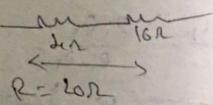
$$\frac{8 \times 8}{8+8} = \frac{64}{16} = 4\Omega$$



$$R = 20\Omega$$

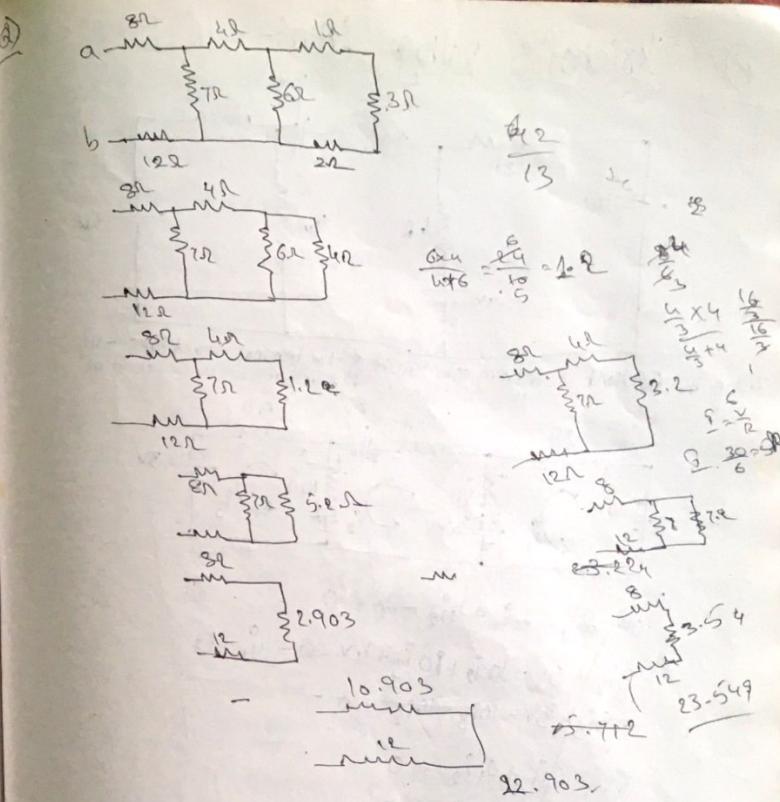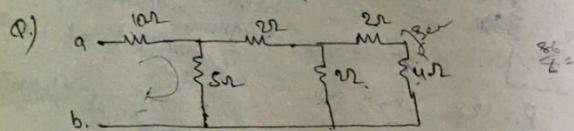

A voltage division:-

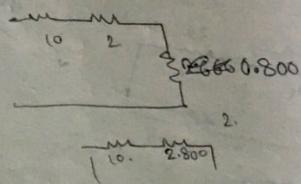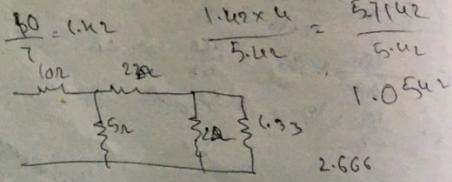



$$1.0 \times 0.8 = 0.800$$

$$2.0 \times 0.8 = 1.600$$


$$10 + 2 = 12$$

$$12 \times 0.8 = 9.600$$

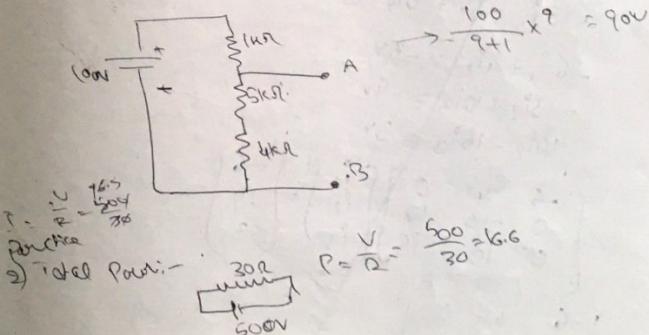

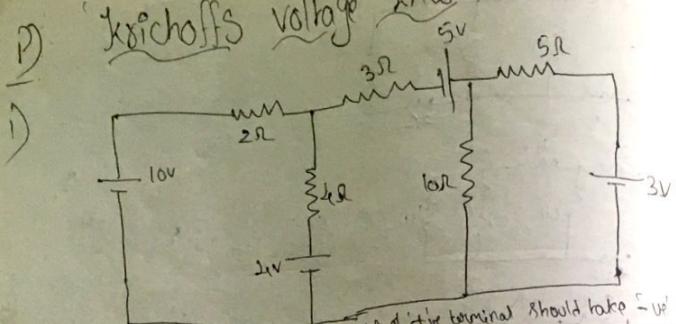

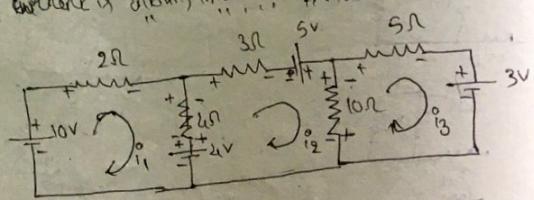When the current is entering into terminal of the terminal " +ve " " " " " +ve " " -ve " " " " " -ve "



$$10V - 2i_1 - 4i_1 - 4V + 4i_2 = 0$$

$$-3i_2 + 5V - 10i_2 + 10i_3 + 4V - 2i_1 - 4i_1 = 0$$

$$-5i_3 - 3V - 10i_3 + 10i_2 = 0$$

$$6V - 6i_1 + 4i_2 = 0$$

~~$$-13i_2 + 9V + 10i_3 = 0$$~~

$$-15i_3 - 3V + 10i_2 = 0$$

$$-6i_1 + 4i_2 = -6V$$

$$-13i_2 + 10i_3 = -9V$$

$$10i_2 - 15i_3 = 3V$$

$$\begin{vmatrix} -6 & 4 & 0 \\ 0 & -13 & 10 \\ 0 & 10 & -15 \end{vmatrix} \begin{Bmatrix} i_1 \\ i_2 \\ i_3 \end{Bmatrix} = \begin{Bmatrix} -6 \\ -9 \\ 3 \end{Bmatrix}$$

$$\Delta = \begin{vmatrix} -6 & 4 & 0 \\ 0 & -13 & 10 \\ 0 & 10 & -15 \end{vmatrix} =$$

$$10V - 2i_1 - 4i_1 - 4V + 4i_2 = 0$$

$$2V - 4i_2 + 4i_1 - 3i_2 + 5V - 10i_2 + 10i_3 = 0$$

$$-10i_3 + 10i_2 - 5i_3 - 3V = 0$$

$$-6i_1 + 6V + 4i_2 = 0$$

$$9V - 17i_2 + 4i_1 + 10i_3 = 0$$

$$-10i_3 + 5i_2 - 3V = 0$$

$$\Rightarrow -6i_1 + 2i_2 = -6V$$

$$2i_1 - 17i_2 + 10i_3 = -9V$$

$$5i_2 - 10i_3 = 3V$$

$$\begin{vmatrix} -6 & 4 & 0 \\ 2 & -17 & 10 \\ 0 & 10 & -15 \end{vmatrix} \begin{Bmatrix} i_1 \\ i_2 \\ i_3 \end{Bmatrix} = \begin{Bmatrix} -6 \\ -9 \\ 3 \end{Bmatrix}$$

$$\Delta = \begin{vmatrix} -6 & 4 & 0 \\ 2 & -17 & 10 \\ 0 & 10 & -15 \end{vmatrix} = -560$$

$$\Delta_1 = \begin{vmatrix} -6 & 4 & 0 \\ -9 & -17 & 10 \\ 3 & 5 & -10 \end{vmatrix} = -960$$

$$\Delta_2 = \begin{vmatrix} -6 & -6 & 0 \\ 4 & -9 & 10 \\ 0 & 3 & -10 \end{vmatrix} = -600$$


$$\Delta_3 = \begin{vmatrix} -6 & 4 & -6 \\ 4 & -17 & -9 \\ 0 & 5 & 3 \end{vmatrix} = -132$$

$$\Delta \times i_1 = \frac{\Delta_1}{\Delta} = \frac{-960}{-560} = 1.714$$


$$i_2 = \frac{\Delta_2}{\Delta} = \frac{-600}{-560} = 1.0714$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{-132}{-560} = 0.235$$


P) 2)

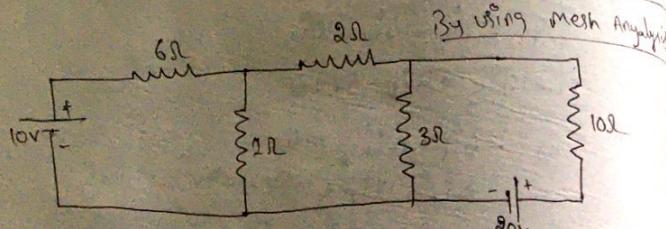


P) 3)

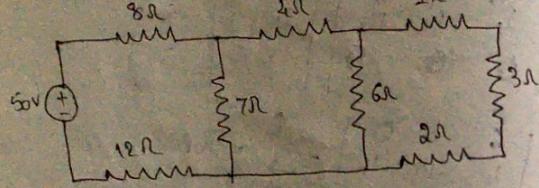


P) 4)

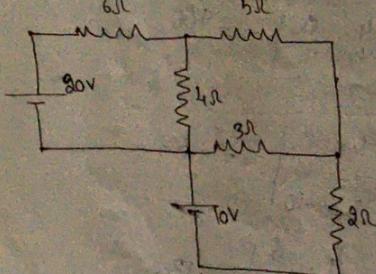

P) 5)

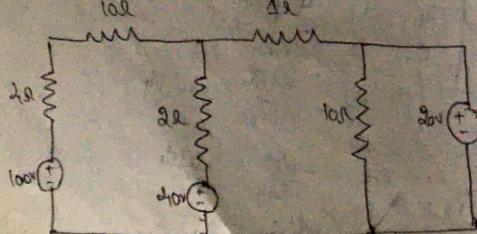


P)  
6)

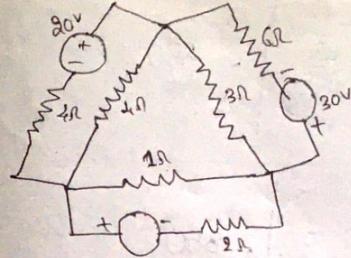

$$\begin{aligned} P &= V^2 / R \\ &= U^2 / R \\ &= I^2 R \end{aligned}$$

P)  
2 Ans)

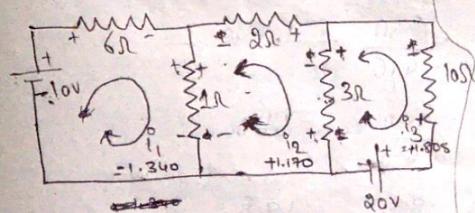

$$P_{av} = 10 \times 1.340 = 13.4 \text{ W}$$

(derived)

$$P_{av} = (1.340)^2 \times 6 =$$

$$\begin{aligned} P_R &= 9.2R + 9.2^2 R \\ &= (1.340)^2 \times 6 + (1.340)^2 \times 1 \\ P_{av} &= 20 \times 1.808 \approx \text{del-m} \end{aligned}$$

$$\begin{aligned} &+ 10 - 6i_1 - i_1 + i_2 = 0 \quad \text{Ans +ve 2} \\ &- i_2 + i_1 - 2i_2 - 3i_2 + 3i_3 = 0 \quad \text{Ans -ve 3} \\ &- 20 - 3i_3 + 3i_2 - 10i_3 = 0 \end{aligned}$$

$$-7i_1 + i_2 = 10$$

$$i_1 - 6i_2 + 3i_3 = 0$$

$$3i_2 - 13i_3 = 20$$

$$\Delta = \begin{vmatrix} -7 & 1 & 0 \\ 1 & -6 & 3 \\ 0 & 3 & -13 \end{vmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 10 \\ 0 \\ 20 \end{pmatrix}$$

$$\Delta = \begin{vmatrix} -7 & 1 & 0 \\ 1 & -6 & 3 \\ 0 & 3 & -13 \end{vmatrix} = -470$$

$$\Delta_1 = \begin{vmatrix} 10 & 1 & 0 \\ 0 & -6 & 3 \\ 20 & 3 & -13 \end{vmatrix} = -630$$

$$\Delta_2 = \begin{vmatrix} -7 & 10 & 0 \\ 1 & 0 & 3 \\ 0 & 30 & -13 \end{vmatrix} = 550$$

$$\Delta_3 = \begin{vmatrix} -7 & 1 & 10 \\ 1 & -6 & 0 \\ 0 & 3 & 20 \end{vmatrix} = 850$$


$$i_1 = \frac{\Delta_1}{\Delta} = \frac{-630}{-470} = 1.340$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{550}{-470} = -1.1702$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{850}{-470} = -1.808$$

(Power):

$$P_{10V}$$

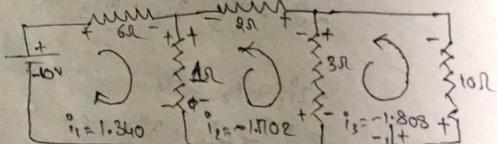

$$P = VI ; P = V^2/R ; P = I^2 R$$


$$P_{10V} = (1.340) \times 10 = 13.40$$

$$P_{60V} = 60 \times 10 = 13.40$$

$$P_{12\Omega} = i_1^2 R + \frac{i_2^2 R}{2} \\ = (1.340)^2 (12) + (-1.1702)^2 \times 1 \\ = 3.16496 \Omega$$

$$P_{2\Omega} = 10 \times -1.1702 = -11.702 \Omega$$
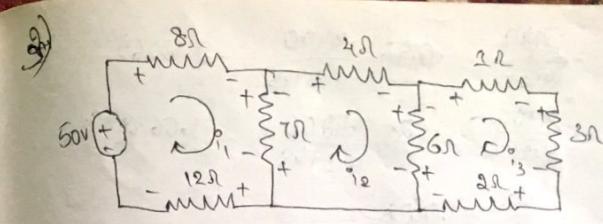
$$P_{3\Omega} = i_2^2 R + i_3^2 R \\ = (-1.1702)^2 \times 3 + (-1.808)^2 \times 3 = 11.175$$



$$50 - 8i_1 - 7i_1 + 7i_2 - 12i_1 = 0$$

$$-7i_2 + 7i_1 - 4i_2 - 6i_2 + 6i_3 = 0$$

$$-6i_3 + 6i_2 - i_3 - 3i_3 - 2i_3 = 0$$

$$-27i_1 + 7i_2 = -50$$

$$7i_1 - 17i_2 + 6i_3 = 0$$

$$6i_2 - 12i_3 = 0$$

$$\Delta = \begin{vmatrix} -27 & 7 & 0 \\ 7 & -17 & 6 \\ 0 & 6 & -12 \end{vmatrix} \begin{Bmatrix} i_1 \\ i_2 \\ i_3 \end{Bmatrix} = \begin{Bmatrix} 50 \\ 0 \\ 0 \end{Bmatrix}$$

$$\Delta = \begin{vmatrix} -27 & 7 & 0 \\ 7 & -17 & 6 \\ 0 & 6 & -12 \end{vmatrix} = -3948$$

$$\Delta_1 = \begin{vmatrix} 50 & 7 & 0 \\ 0 & -17 & 6 \\ 0 & 6 & -12 \end{vmatrix} = 8400$$


$$\Delta_2 = \begin{vmatrix} -27 & 50 & 0 \\ 7 & 0 & 6 \\ 0 & 0 & -12 \end{vmatrix} = 4800$$

$$\Delta_3 = \begin{vmatrix} -27 & 0 & 50 \\ 7 & 6 & 0 \\ 0 & -12 & 0 \end{vmatrix} = -4800$$

$$i_1 = \frac{\Delta 1}{\Delta} = \frac{2948}{-3948} = -0.74 \quad \frac{8400}{-3948} = -2.12765$$

$$i_2 = \frac{\Delta 2}{\Delta} = \frac{8400}{-3948} = 2.12765 \quad \frac{-21200}{-3948} = 1.063829$$
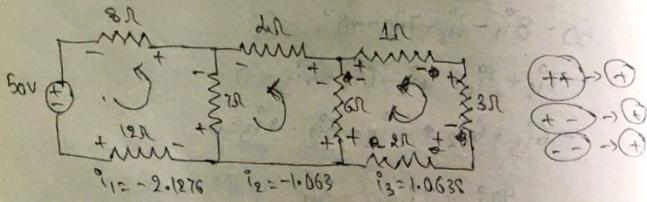
$$i_3 = \frac{\Delta 3}{\Delta} = \frac{-4200}{-3948} = 1.0638$$



$$P_{50V} = (-2.1276)^2 \times 8 = -17.016$$

$$P_{2\Omega} = (-2.1276)^2 \times 2 = -3.6193$$

$$P_{1\Omega} = (-2.1276)^2 \times 1 + (-1.063)^2 \times 3 \\ = -23.776$$

$$P_{3\Omega} = (-1.063)^2 \times 3 = -54.289$$


$$P_4 = (-1.063)^2 \times 4 = -4.519$$

$$P_6 = (-1.063)^2 \times 6 + (1.0638)^2 \times 8 \\ = 0.0102$$

$$P_1 = 1 \times 1.0638 = 1.0638$$

$$P_3 = 3 \times 1.063 = 3.189$$

$$P_2 = 2 \times 1.063 = 8.126$$

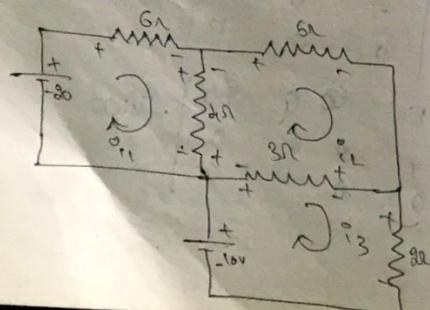

$$20 - 6i_1 - 4i_1 + 4i_2 = 0 \\ -2i_2 + 4i_1 - 5i_2 - 3i_2 + 3i_3 = 0 \\ 10 - 3i_3 + 3i_2 - 2i_3 = 0$$

$$-10i_1 + 4i_2 = -20$$

$$4i_1 - 12i_2 + 3i_3 = 0$$

$$3i_2 - 5i_3 = -10$$

$$\begin{vmatrix} -10 & 4 & 0 \\ 4 & -12 & 3 \\ 0 & 3 & -5 \end{vmatrix} \begin{Bmatrix} i_1 \\ i_2 \\ i_3 \end{Bmatrix} = \begin{Bmatrix} -20 \\ 0 \\ -10 \end{Bmatrix}$$

$$\Delta = \begin{vmatrix} -10 & 4 & 0 \\ 4 & -12 & 3 \\ 0 & 3 & -5 \end{vmatrix} = -430$$

$$\Delta_1 = \begin{vmatrix} -20 & 4 & 0 \\ 0 & -12 & 3 \\ -10 & 3 & -5 \end{vmatrix} = -1140$$


$$\Delta_2 = \begin{vmatrix} -10 & -20 & 0 \\ 4 & 0 & 3 \\ 0 & -10 & 5 \end{vmatrix} = 700$$

$$\Delta_3 = \begin{vmatrix} -10 & 4 & 20 \\ 4 & -12 & 0 \\ 0 & 3 & -10 \end{vmatrix} = -1280$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{-1140}{-430} = 2.676$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{700}{-430} = -1.62$$
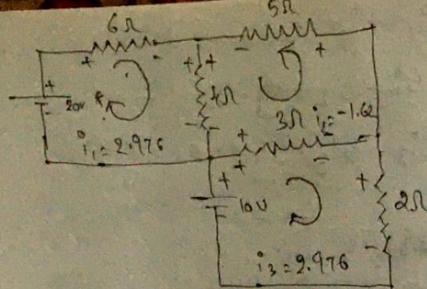
$$i_3 = \frac{\Delta_3}{\Delta} = \frac{-1280}{-430} = 2.976$$



$$P_{20} = 2.976 \times 20 = 59.52$$

$$P_6 = (2.976)^2 \times 6 = 53.13$$

$$P_4 = (2.976)^2 \times 4 + (-1.62)^2 \times 4$$

$$= 35.42 + -10.4976 = 24.922$$

$$P_5 = (-1.62)^2 \times 5 =$$


$$= -13.22$$

$$P_3 = (-1.62)^2 \times 3 + (2.976)^2 \times 3$$

$$= 18.696$$

$$P_2 = (2.976)^2 \times 2 = 17.113$$

$$P_{10} = 2.976 \times 10 = 29.76$$

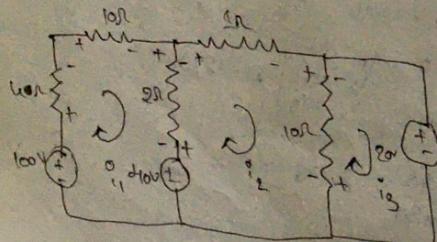

$$100 - 4.8i_1 - 10i_1 - 8i_1 + 2i_2 - 10 + 40 = 0$$

$$240 - 2i_2 + 2i_1 - i_2 - 10i_2 + 10i_3 = 0$$

$$-20 - 10i_3 + 10i_2 = 0$$

$$-16i_1 + 2i_2 = -100$$

$$-13i_2 + 2i_1 + 10i_3 = -40$$

$$10i_2 - 10i_3 = 20$$

$$\begin{vmatrix} -16 & 2 & 0 \\ 2 & -13 & 10 \\ 0 & 10 & -10 \end{vmatrix} \begin{Bmatrix} i_1 \\ i_2 \\ i_3 \end{Bmatrix} = \begin{Bmatrix} -100 \\ -40 \\ 20 \end{Bmatrix}$$

$$\Delta = \begin{vmatrix} -16 & 2 & 0 \\ 2 & -13 & 10 \\ 0 & 10 & -10 \end{vmatrix} = -440$$

$$\Delta_1 = \begin{vmatrix} -100 & 2 & 0 \\ -40 & -13 & 10 \\ 20 & 10 & -10 \end{vmatrix} = -3400$$

$$\Delta_2 = \begin{vmatrix} -16 & -100 & 0 \\ 2 & -40 & 10 \\ 0 & 20 & -10 \end{vmatrix} = -5200$$


$$\Delta_3 = \begin{vmatrix} -16 & 2 & -100 \\ 2 & -13 & -40 \\ 0 & 10 & 20 \end{vmatrix} = -6320$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{-3400}{-440} = 7.7272$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{-5200}{-440} = 11.818$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{-6320}{-440} = 14.364$$

Power :-

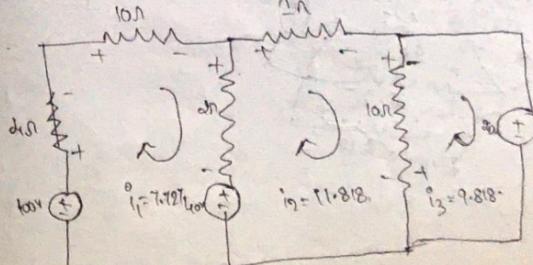

$$P_{100V} = 100 \times 7.727$$

$$= 772.7$$

$$P_{28} = (7.727)^2 \times 4 = 238.8$$

$$P_{100} = (7.727)^2 \times 100 = 5970.6$$

$$\begin{aligned} P_{28} &= (7.727)^2 \times 2 + (11.818)^2 \times 2 \\ &= 119.41 + 279.33 \\ &= 398.74 \end{aligned}$$

$$\begin{aligned} P_{40V} &= i_1 x v + i_2 x u \\ &= 7.727 \times 40 + 11.818 \times 40 \\ &= 309.08 + 472.72 \\ &= 781.8 \end{aligned}$$

$$P_{10V} = 139.66 \times 1$$

$$= 139.66$$

$$\begin{aligned} P_{10} &= 139.66 \times 10 + 96.393 \times 10 \\ &= 1396.6 + 963.93 \\ &= 2360.53 \end{aligned}$$

$$\begin{aligned} P_{80} &= 9.818 \times 20 \\ &= 196.36 \end{aligned}$$

$$P = Vi ; P = \frac{V}{R} ; P = i^2 R$$

$$\Rightarrow i_2 = 139.66$$

$$\begin{aligned} i_2 &= 139.66 \\ i_3 &= 96.393 \end{aligned}$$

$$-4i_1 + 20 - 4i_1 + 4i_2 = 0$$

$$-4i_2 + 4i_1 - 3i_2 + 3i_3 + i_2 + i_4 = 0$$

$$-3i_3 + 3i_2 - 6i_3 + 30 = 0.$$

$$-i_2 + i_3 - 2i_4 + 10 = 0$$

$$-8i_1 + 4i_2 = -20$$

$$4i_1 - 8i_2 + 3i_3 + i_4 = 0$$

$$-9i_3 + 3i_2 = -30$$

$$-3i_4 + i_3 + i_4 = -10$$

$$\left[ \begin{array}{cccc} -8 & 4 & 0 & 0 \\ 4 & -8 & 3 & 1 \\ 0 & 3 & -9 & 0 \\ 0 & 0 & 1 & -3 \end{array} \right] = \left[ \begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \end{array} \right] = \left[ \begin{array}{c} -20 \\ 0 \\ -30 \\ -10 \end{array} \right]$$

$$A = \left[ \begin{array}{cccc} -8 & 4 & 0 & 0 \\ 4 & -8 & 3 & 1 \\ 0 & 3 & -9 & 0 \\ 0 & 0 & 1 & -3 \end{array} \right]$$

$$|A| = -8|A| - 4|B| + 0 + 0 = 0$$

$$\text{Consider } |A| = \left| \begin{array}{ccc} -8 & 3 & 1 \\ 3 & -9 & 0 \\ 0 & 1 & -3 \end{array} \right| \Rightarrow |A| = \left| \begin{array}{ccc} -8 & 3 & 1 \\ 3 & -9 & 0 \\ 0 & 1 & -3 \end{array} \right|$$

$$-8|A| = -186 \times -8$$

$$= 1488.$$


$$|B| = \left| \begin{array}{ccc} 4 & 3 & 0 \\ 0 & -9 & 1 \\ 0 & 1 & 0 \end{array} \right| = |B| = -4$$

$$4 \times |B| = 4 \times -4 = -16$$

$$\text{Now: } |A| = -1488 - (-16) = 0$$

$$= 1488 + 16 = 1504$$

$$A_1 = \left| \begin{array}{cccc} -20 & 4 & 0 & 0 \\ 0 & -8 & 3 & 1 \\ -30 & 3 & -9 & 0 \\ -10 & 0 & 1 & -3 \end{array} \right|$$

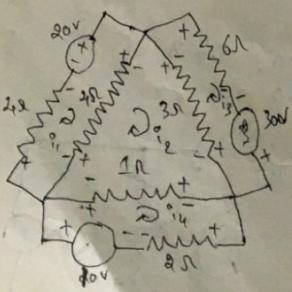

$$\text{now } |\Delta_1| = -20 \times |A| - 4 \times |B|$$

$$\text{now } A = \begin{vmatrix} -8 & 3 & 1 \\ 3 & -9 & 0 \\ 0 & 1 & -3 \end{vmatrix} \Rightarrow |A| = 1488$$

$$\therefore -20 \times |A| = -20 \times 1488 = -29760.$$

$$\text{now } B = \begin{vmatrix} 0 & 3 & 1 \\ -30 & -9 & 0 \\ -10 & 1 & -3 \end{vmatrix} \Rightarrow |B| = -390$$

$$\therefore -4 \times |B| = -390 \times -4 = 1560$$

$$|\Delta_1| = -29760 + 1560 = -28200$$

~~$$\Delta_2 = \begin{vmatrix} -8 & -20 & 0 & 0 \\ 4 & 0 & 3 & 1 \\ 0 & -30 & -9 & 0 \\ 0 & -10 & 1 & 3 \end{vmatrix}$$~~

$$|\Delta_2| = -8 \times |A| - (-20) \times |B|$$

$$A = \begin{vmatrix} 0 & 3 & 1 \\ -30 & -9 & 0 \\ -10 & 1 & 3 \end{vmatrix} \Rightarrow |A| = -390$$

$$\therefore -8 \times |A| = -390 \times -8 = 3120$$

$$B = \begin{vmatrix} 4 & 3 & 1 \\ 0 & -9 & 0 \\ 0 & 1 & 3 \end{vmatrix} \Rightarrow |B| = -16$$

$$-20 \times -16 = 320$$

$$\text{now } |\Delta_2| = 3120 - 320 = 2800$$

$$\Delta_3 = \begin{vmatrix} -8 & 4 & -20 & 0 \\ 4 & -8 & 0 & 1 \\ 0 & 3 & -30 & 0 \\ 0 & 0 & -10 & 3 \end{vmatrix}$$

+ - + -

$$|\Delta_3| = -8 \times |A| - 4 \times |B| - 20 \times |C|.$$

$$A = \begin{vmatrix} -8 & 0 & 1 \\ 3 & -30 & 0 \\ 0 & -10 & 3 \end{vmatrix} \Rightarrow |A| = 690$$

$$-8 \times |A| = -8 \times 690 = -5520$$

$$B = \begin{vmatrix} 4 & 0 & 1 \\ 0 & -30 & 0 \\ 0 & -10 & 3 \end{vmatrix} \Rightarrow |B| = -360$$

$$-4 \times |B| = 4 \times -360 = -1440$$

$$C = \begin{vmatrix} 4 & -8 & 1 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{vmatrix} = 36$$

$$20 \times |C| = 20 \times 36 = 720$$

$$|\Delta_3| = -5520 + 1440 - 720$$

$$= -3360$$

$$\Delta_4 = \begin{vmatrix} -8 & 4 & 0 & -20 \\ 4 & -8 & 3 & 0 \\ 0 & 3 & -9 & -30 \\ 0 & 0 & 1 & -10 \end{vmatrix}$$

$$|\Delta_4| = -8 \times |A| - 4 \times |B| - 20 \times |D|$$

$$A = \begin{vmatrix} -8 & 3 & 0 \\ 3 & -9 & -30 \\ 0 & 1 & -10 \end{vmatrix} \Rightarrow |A| = -870$$

$$-8 \times |A| = -8 \times -870 = 6960$$

$$B = \begin{vmatrix} 4 & -8 & 0 & 0 \\ 0 & +30 & 0 & 0 \\ 0 & -9 & -30 & 0 \\ 0 & 1 & -10 & 0 \end{vmatrix} = B = \begin{vmatrix} 4 & 3 & 0 \\ 0 & -9 & -30 \\ 0 & 1 & -10 \end{vmatrix}$$

$$\Rightarrow |B| = 480$$

$$-4 \times |B| = -4 \times 480 = -1920$$

$$D = \begin{vmatrix} 4 & -8 & 3 \\ 0 & 3 & -9 \\ 0 & 0 & 1 \end{vmatrix} \Rightarrow |D| = 12$$

$\therefore -20 \times 12 = -240$

$$|A_4| = +6960 - 1920 - 240$$


$\frac{4800}{4800}$

$$\therefore i_1 = \frac{A_1}{\Delta} = \frac{-28200}{1504} = -18.75$$

$$i_2 = \frac{A_2}{\Delta} = \frac{2800}{1504} = 1.8617$$

$$i_3 = \frac{A_3}{\Delta} = \frac{-3360}{1504} = -2.234$$
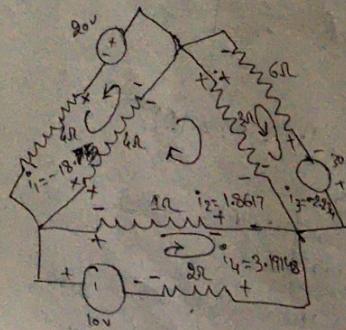
$$i_4 = \frac{A_4}{\Delta} = \frac{4800}{1504} = 3.19148$$



$$\therefore P_{4R} = i_1^2 \times 4 = (-18.75)^2 \times 4 = 1406.25$$

$$P_{20V} = (-18.75) \times 20 = -375.$$

$$P_{4R} = i_1^2 \times R + i_2^2 \times R$$

$$= (-18.75)^2 \times 4 + (1.8617)^2 \times 4$$

$$= -351.562 \times 4 + (3.465 \times 4)$$

$$= 1406.248 + 13.863 = -1290.785$$

$$P_3 = i_2^2 \times 3 + i_3^2 \times 3$$

$$= (3.465 \times 3) + (-4.99075 \times 3)$$

$$= 10.395 - 14.972$$

$$= -4.577$$

$$P_1 = i_2^2 \times 1 + i_4^2 \times 1$$

$$= 13.650$$



$$P_{6R} = i_3^2 \times 6 = -29.94$$

$$P_{30} = i_3 \times 30 = -66.9$$


$$P_2 = i_4^2 \times 2 = 20.37$$




$$P_{10} = i_4 \times 10 = 31.9148$$

Mesh Analysis:-

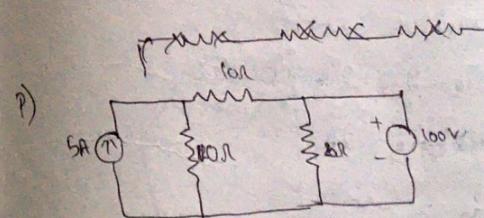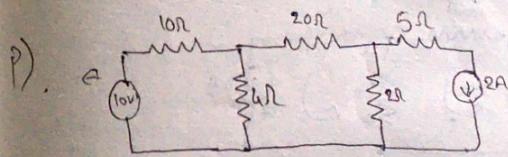

Super Mesh:-

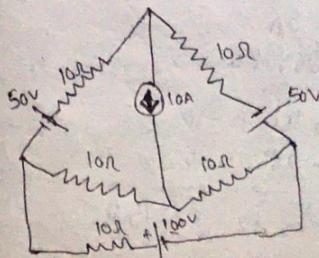

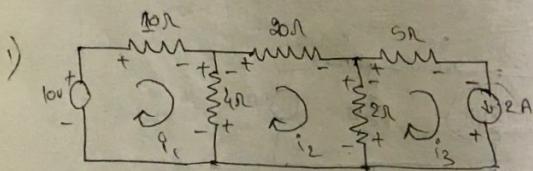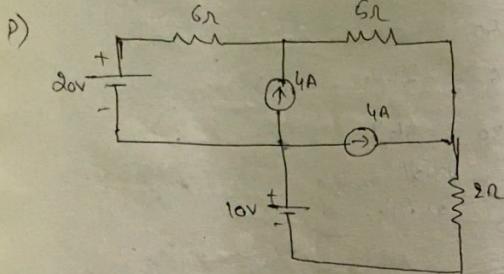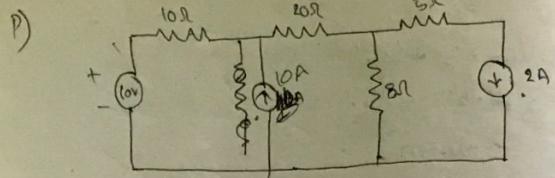

$$10 - 10i_1 - 4i_2 + 4i_2 = 0 \rightarrow ①$$

$$-4i_2 + 4i_1 - 20i_2 - 2i_2 + 2i_3 = 0 \rightarrow ②$$

$$-2i_2 - 3i_2 + 2i_3 = 2A$$

$$-14i_1 + 4i_2 = -10$$

$$-26i_2 + 4i_1 + 2i_3 = 0$$


$$i_3 = 8A$$

$$\Rightarrow +4i_1 - 26i_2 + 4 = 0$$

$$\Rightarrow -14i_1 + 4i_2 = -10$$

$$4i_1 - 26i_2 = -4$$
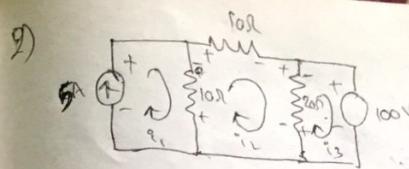
$$\underline{i_1 = 0.793A \quad i_2 = 0.275A}$$



$$i_1 = 5A$$

$$-10i_2 + 10i_1 - 10i_2 - 20i_2 + 20i_3 = 0$$

$$-20i_3 + 20i_2 - 100 = 0$$

$$\Rightarrow -40i_2 + 10i_1 + 20i_3 = 0 \Rightarrow -40i_2 + 50 + 20i_3 = 0$$

$$-20i_3 + 20i_2 = 100$$

$$\Rightarrow -40i_2 + 20i_3 = -50$$


$$-40i_2 + 20i_3 = -50$$

$$20i_2 - 20i_3 = 100$$

$$\underline{i_2 = -2.5A \quad i_3 = -7.5A}$$


$$i_1 = 5A \quad , \quad i_2 = -2.5A \quad ; \quad i_3 = -7.5A$$

Super mesh:-

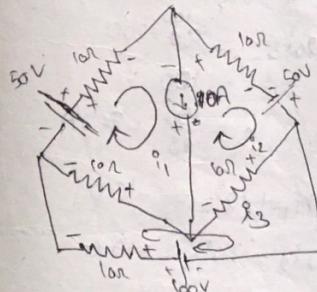

$$50 - 10i_1 - 10i_2 - 10i_1 + 10i_3 = 0 \quad (i_1 - i_2) \times 10$$

$$-20i_2 + 10i_3 = 50$$

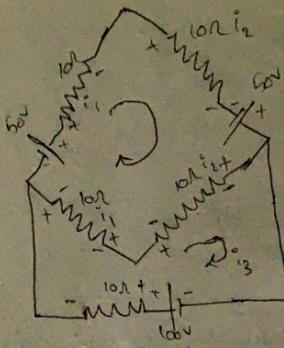

$$i_1 - i_2 = 10 \text{ A} \rightarrow ①$$

$$60 + 50 - 10i_1 - 10i_2 - 10i_2 + 10i_3 - 10i_1 + 10i_3 = 0 \quad ②$$

$$-10i_3 + 10i_1 - 10i_3 + 10i_2 + 100 - 10i_3 = 0 \rightarrow ③$$

$$-20i_1 - 20i_2 + 20i_3 = -100$$

$$-20(i_1 - i_2) + 20i_3 = -100$$

$$-20 \times 10 + 20i_3 = -100$$

$$-200 + 20i_3 = -100$$

$$20i_3 = -100 + 200$$

$$20i_3 = 100$$

$$i_3 = \frac{100}{20} = 5 \text{ A}$$

$$-30i_3 + 10i_1 + 10i_2 = -100$$

$$10i_1 + 10i_2 - 30i_3 = -100$$

~~$$100 = -10i_1 - 10i_2 + 30i_3$$~~

$$100 = -10(i_1 + i_2) + 30i_3$$

$$100 = -10(i_1 + i_2) + 30 \times 5$$

$$\times 50 = 10(i_1 + i_2)$$

$$i_1 + i_2 = \frac{50}{10} = 5$$

$$i_1 + i_2 = 5 \rightarrow ④$$

$$\text{Solving } i_1 - i_2 = 10$$

$$i_1 + i_2 = 5$$

$$i_1 - i_2 = 10$$

$$-2i_2 = 5$$


$$i_2 = -\frac{5}{2} = -2.5$$

$$i_2 = -2.5$$


$$i_1 = 7.5 ; i_2 = -2.5$$

$$i_1 = 7.5 \text{ A} ; i_2 = -2.5 \text{ A} ; i_3 = 5 \text{ A}$$

Method of analysis:-

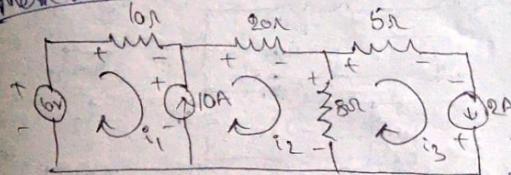

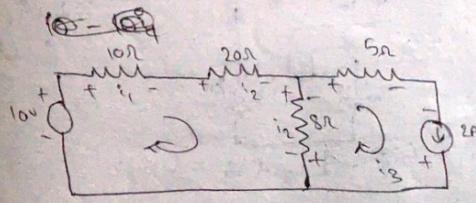here in last loop the 2A  
current is moving  
in clockwise direction  
so loop containing only 2A  
is i.e. i3 = 2A



$$i_1 + i_2 = 10 \text{ A}$$

$$10 - 10i_1 - 20i_2 - 8i_2 + 8i_3 = 0$$

~~$$-10i_3 + 8i_2 - 8i_2 = 10i_3 \quad i_3 = 2 \text{ A}$$~~

$$10 - 10i_1 - 28i_2 + 8i_3 = 0$$

~~$$-10i_1 - 28i_2 + 8 \times 2 = -10$$~~

~~$$-10i_1 - 28i_2 + 16 = -10$$~~



~~$$-10i_1 - 28i_2 = -26$$~~

~~$$\times (10i_1 + 28i_2) = +26$$~~

$$10i_1 + 28i_2 = 26$$

$$-i_1 + i_2 = 10$$
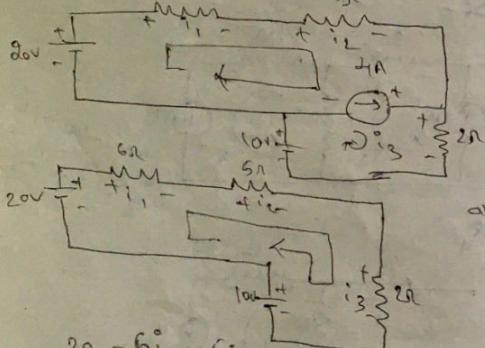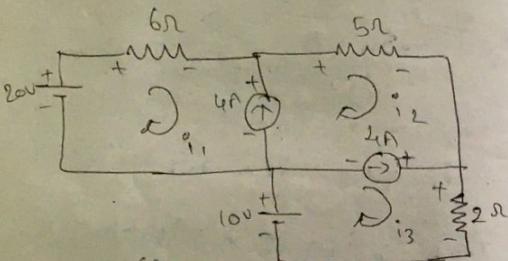
$$i_1 = -6.68 \quad ; \quad i_2 = 3.315$$



$$20 - 6i_1 - 5i_2 - 2i_3 + 10 = 0$$

$$-6i_1 - 5i_2 - 2i_3 + 30 = 0$$

$$30 = 6i_1 + 5i_2 + 2i_3$$

$$30 = 6i_1 + 20 - 5i_1 + 2i_3$$

$$10 = 6i_1 + 2i_3 \rightarrow ①$$

Solving ① and ②

$$i_1 + 2i_3 = 16$$

$$i_1 + 2i_3 = 10$$

$$i_1 = 22 \quad ; \quad i_2 = -6$$


$$i_1 = 22 \text{ A} ; \quad i_3 = -6 \text{ A}$$

now substitute in  $i_2 = i_1 - i_3$


$$i_2 = 4 - 22$$

$$i_2 = -18 \text{ A}$$

### Nodal Analysis

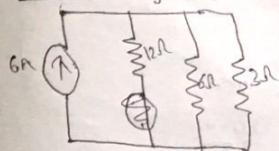

Circuit with Resistors  
Nodal Analysis

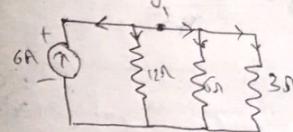



$$-6 + \frac{v_1 - 0}{12} + \frac{v_1 - 0}{6} + \frac{v_1 - 0}{3} = 0$$

$$\frac{v_1}{12} + \frac{v_1}{6} + \frac{v_1}{3} = 6$$

$$\frac{v_1 + 2v_1 + 18v_1}{36} = 6$$

$$\frac{22v_1}{36} = 6$$
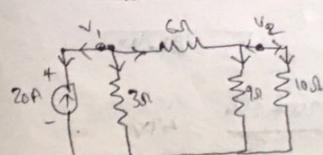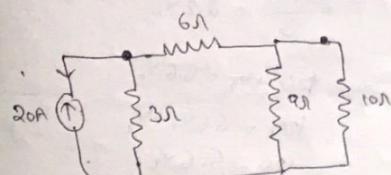
$$v_1 = \frac{72}{22} = 0.636 \text{ V} \approx 0.23$$



$$-20 + \frac{V_1 - V_2}{3} + \frac{V_1 - V_2}{6} = 0$$

$$\frac{V_1 - V_2}{3} + \frac{V_1 - V_2}{6} = 20$$

$$\frac{2V_1 + V_2 - V_L}{6} = 20$$

$$\frac{3V_1 - V_2}{6} = 20$$

$$3V_1 - V_2 = 120$$

$$3V_1 = \frac{120 + V_2}{3}$$

$$V_1 = \frac{120 + V_2}{9}$$

$$\frac{V_2 - V_1}{6} + \frac{V_2}{9} + \frac{V_1}{10} = 0$$

$$\frac{15V_2 - 15V_1 + 10V_1 + 9V_2}{90} = 0$$

$$\frac{3V_2 - 15V_1}{90} = 0$$

$$3V_2 - 15V_1 = 0$$

$$-15V_1 = 3V_2$$

$$V_1 = \frac{3V_2}{15}$$

$$V_1 = 2.2V_2$$

$$\frac{120 + V_2}{3} = 2.2V_2$$

$$120 + V_2 = 6.6V_2$$

$$120 = 6.6V_2 - V_2$$

$$120 = 5.6V_2$$






$$V_2 = 21.42$$

$$V_1 = \frac{120 + 21.42}{3} = 47.47$$

$$\begin{matrix} 2(6, 9, 10) \\ 3(3, 9, 5) \\ 1(1, 3, 5) \end{matrix}$$

$$\frac{V_2 - V_1}{6} = 20$$

$$\frac{120}{15} = 8$$

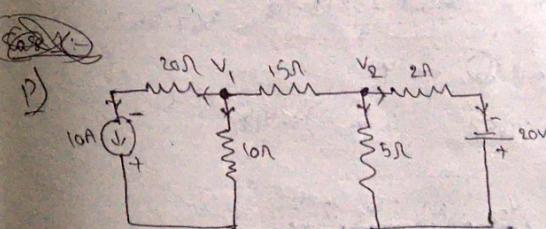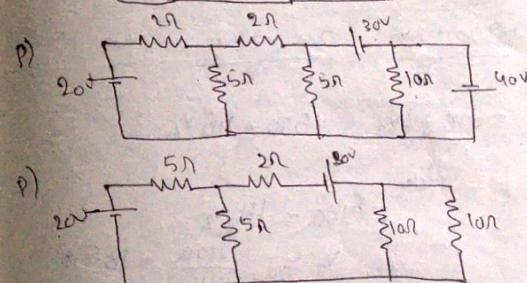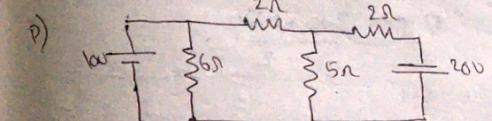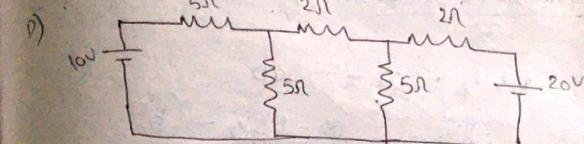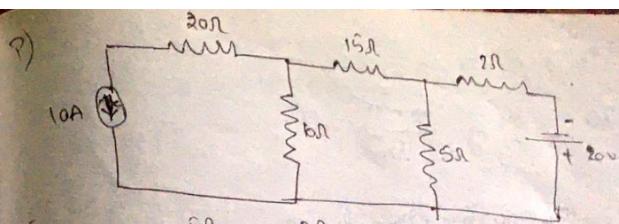

At Node  $V_1$

$$10 + \frac{V_1}{10} + \frac{V_1 - V_2}{15} = 0$$

$$10 + \frac{3V_1 + 2V_1 - 2V_2}{30} = 0$$

$$300 + 5V_1 - 2V_2 = 0$$

$$5V_1 - 2V_2 = -300 \rightarrow (1)$$

$$5V_1 - 2V_2 = -300 + 2V_2$$

$$5V_1 = -300 + 2V_2$$

At node 'V<sub>2</sub>' :-

$$\frac{V_2 + 20}{2} + \frac{V_2}{5} + \frac{V_2 - V_1}{15} = 0$$

$$V_2 \frac{15V_2 + 300 + 6V_2 + 2V_2 - 2V_1}{30} = 0$$

$$23V_2 - 2V_1 = -300$$

$$-2V_1 = -300 - 23V_2 \rightarrow (b)$$

$$V_1 = \frac{300 + 23V_2}{2}$$

Solving 'a' we get

$$\frac{-300 + 2V_2}{5} = \frac{300 + 23V_2}{2}$$

$$-600 + 4V_2 = 1500 + 115V_2$$

~~(a)~~


$$-2100 = 111V_2$$

$$V_2 = \frac{-2100}{111} = 18.918$$

$$V_1 = \frac{-300 + 23 \times 18.918}{2} = 367.562$$

Solving (a) and (b) we get
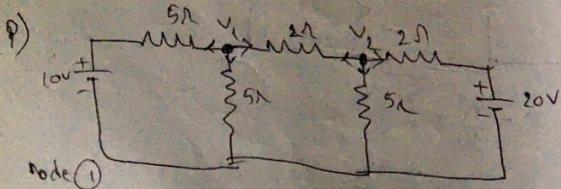
$$V_1 = -67.56 \quad ; \quad V_2 = 18.918$$



$$\frac{V_1 - 10}{5} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{2V_1 - 20 + 2V_1 + 5V_1 - 5V_2}{10} = 0$$

$$9V_1 - 20 - 5V_2 = 0$$

$$9V_1 - 5V_2 = 20 \rightarrow (a)$$

node ② :-


$$\frac{V_2 - 20}{2} + \frac{V_2}{5} + \frac{V_2 - V_1}{2} = 0$$

$$\frac{5V_2 - 100 + 2V_2 + 5V_2 - 5V_1}{10} = 0$$

$$12V_2 - 5V_1 = 100 \rightarrow (b)$$

Solving (a) and (b)

$$V_1 = 8.91 \quad ; \quad V_2 = 12.04$$

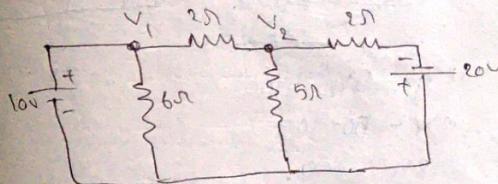

$$\text{Node } ① : \quad V_1 = -10V$$

node ② :-


$$\frac{V_2 + 20}{2} + \frac{V_2}{5} + \frac{V_2 - V_1}{2} = 0$$

$$\frac{5V_2 + 100 + 2V_2 + 5V_2 - 5V_1}{10} = 0$$

$$12V_2 - 5V_1 = -100$$

$$12V_2 = -150$$

$$V_2 = -150 / 12 = -12.5$$

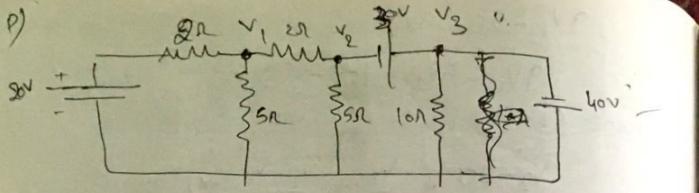

$$\frac{V_1 - 20}{2} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 0 \quad V_3 = 40$$


$$\frac{5V_1 - 100 + 2V_1 + 5V_1 - 5V_2}{10} = 0 \quad V_3 - V_2 = 30V$$

$$12V_1 - 5V_2 = 100 \quad 12V_1 - 5V_2 = 100$$

$$12V_1 - 50 = 100 \quad 12V_1 = 150$$

$$V_1 = 12.5V$$
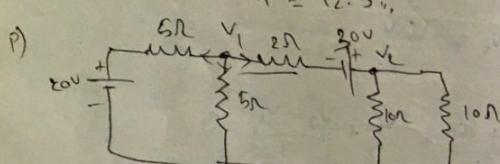
$$V_3 = 40 \\ V_3 - V_2 = 30V \\ 20 - V_2 = 30V \\ V_2 = -10V$$



node  $V_1$

$$\frac{V_1 - 20}{5} + \frac{V_1}{5} + \frac{V_1 + 30 - V_2}{2} = 0$$

$$\frac{9V_1 - 40 + 2V_1 + 5V_1 + 150}{10} = 0$$

$$9V_1 = -110$$

$$V_1 = -12.22$$

$$9V_1 + 5V_2 = -110$$

node  $V_2$  :-

$$\frac{V_2}{10} + \frac{V_2}{10} + \frac{V_2 - 30 - V_1}{2} = 0$$

$$2V_2 - 300 = 0 \quad 2V_2 = 300 \quad V_2 = 150$$

$$7V_2 - 5V_1 = 150$$

$$9V_1 + 750 = -110$$


$$9V_1 = -860$$

$$V_1 = -95.5$$

$$V_1 = -0.5$$


$$V_2 = 21.05$$

Circ(1) :-

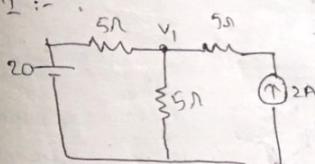


$$\frac{V - 20}{5} + \frac{V}{5} - 2A = 0$$

Circ(2) :-

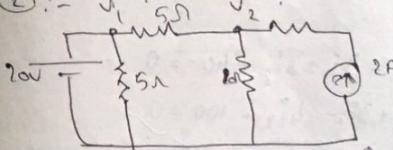




$$V_1 = 10 \quad V_2 = \frac{20}{5} + \frac{V_2}{10} - 2 = 0$$

Circ(3) :-

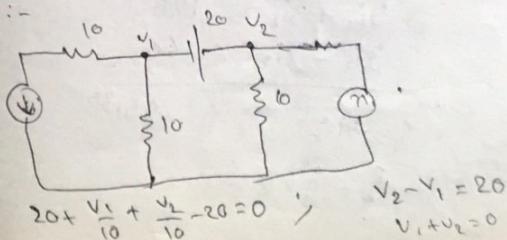

$$20 + \frac{V_1}{10} + \frac{V_2}{10} - 20 = 0 \quad V_2 - V_1 = 20$$

$$V_1 + V_2 = 0$$

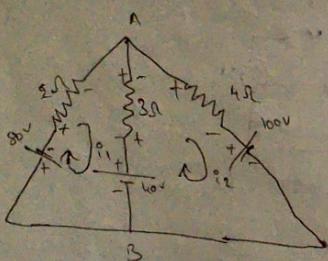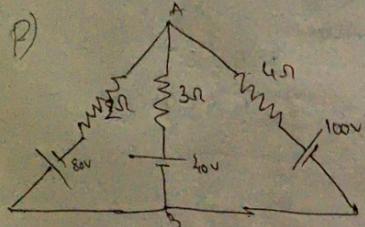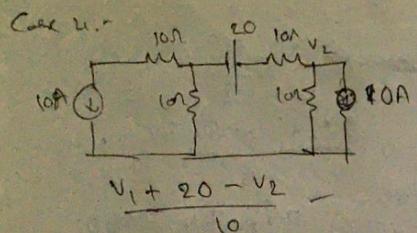

$$-80 - 2i_1 - 3i_1 + 3i_2 - 40 = 0$$

$$40 - 3i_2 + 3i_1 - 4i_2 - 100 = 0$$

$$-120 - 5i_1 + 3i_2 = 0$$

$$3i_1 - 7i_2 - 60 = 0$$

$$-5i_1 + 3i_2 = 120$$

$$3i_1 - 7i_2 = 60$$

$$\underline{i_1 = -99.2 \quad i_2 = -25.38}$$



$$P_L = i_2^2 \times 4 =$$

R

P) Thevenin:-

Voltage - short

Current - open

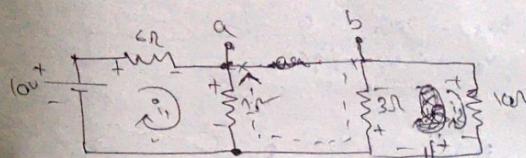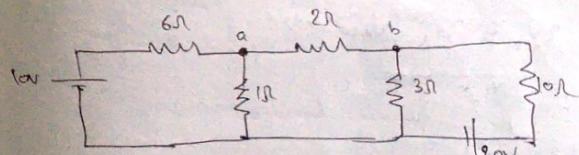


$$10 - 6i_1 - i_1 = 0$$

$$-7i_1 = 10 \Rightarrow i_1 = \frac{10}{7} = 1.428$$

$$-3i_2 - 10 = 0$$

$$-3i_2 = 10 \Rightarrow i_2 = -\frac{10}{3}$$


$$i_2 = \frac{20}{7} \approx 2.857$$

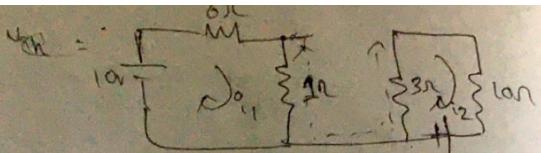

$$i_1 \times 1 + i_2 \times 3 = V_{th}$$

$$1 \cdot 4.28 + 1.539 \times 3 = V_{th}$$

$$V_{th} = 3.189$$

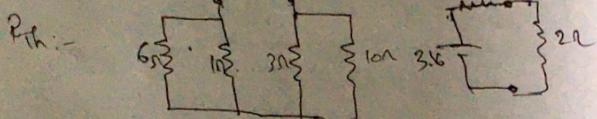

$$R_{th} = \frac{6.5}{7} + \frac{30}{13} = 0.857 + 2.30 = 3.16\Omega$$

$$\frac{V_1}{2} + \frac{V_1}{3} + \frac{V_1 - V_2}{2} = 0 \quad \text{--- (1)}$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{2} + \frac{V_2 - 20}{2} = 0$$









$$3V_1 + 2V_1 + 3V_2 - 3V_2 = 0$$

$$8V_1 - 3V_2 = 0$$

$$3V_2 - V_1 = 20$$

$$8V_1 - 3V_2 = 0$$

$$-V_1 + 3V_2 = 20$$

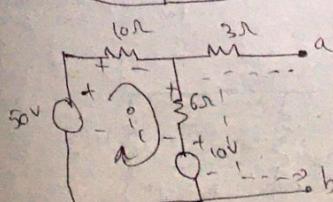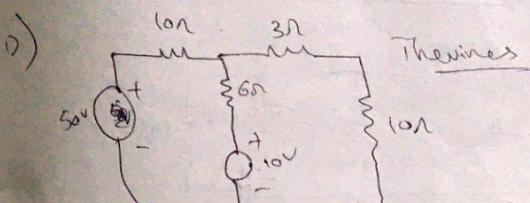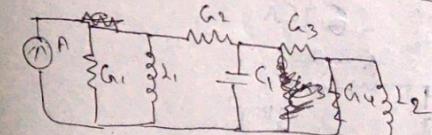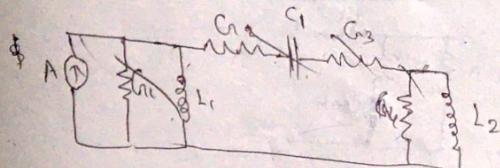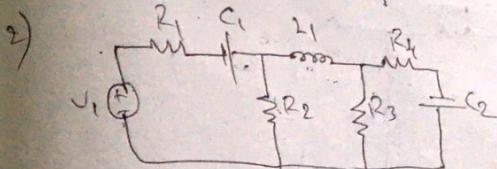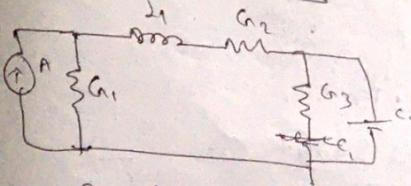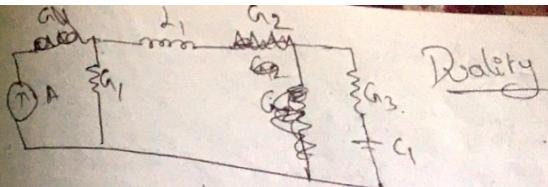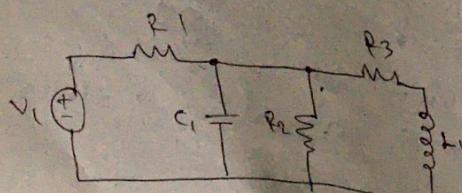

$$50 - 10i_1 - 6i_1 - 10 = 0$$




$$-16i_1 = -40$$

$$16i_1 = 40$$



$$i_1 = 2.5$$

$$V_{Th} = \frac{1}{2} \times 2.5 + 10$$

$$V_{Th} = 15 + 10 = 25V$$

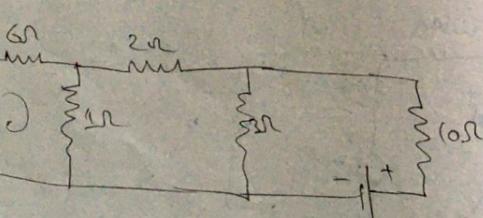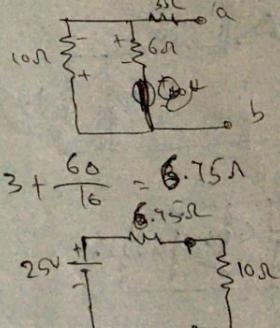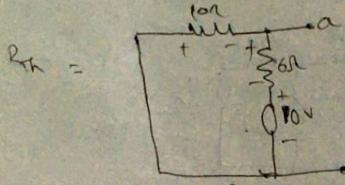

Find Thévenin at 1Ω

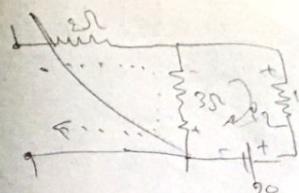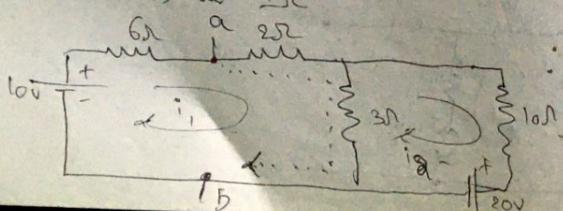

$$10 - 6i_1 - 2i_1 - 3i_1 + 8i_2 = 0$$

$$10 = 1i_1 + 3i_2 \rightarrow (a)$$

$$\frac{10}{1+3} = 2.5 \Omega$$

$$+3i_1 - 2i_1 - 3i_2 - 10i_2 = 0$$

$$3i_1 - 13i_2 = 20 \rightarrow (b)$$


$$2i_1 = 1.53$$

$$V_{Th} = \begin{cases} 3 \times 1.53 & i_1 = 0.46 \\ 4.5V & i_2 = 1.46 \end{cases}$$

$$R_{Th} =$$

$$\Rightarrow$$


$$2.3076 \approx 21.3076\Omega$$

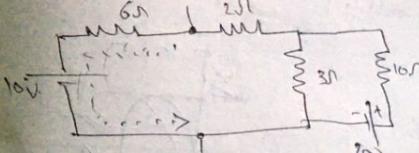

$$V_{Th} = i_1 \times 6$$

$$= 0.46 \times 6 = 2.76$$

$$R_{Th} =$$

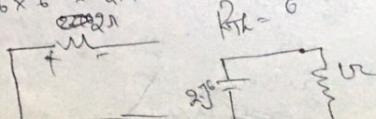

Chapter 2

$$V_{av} = \frac{1}{T} \int v(t) dt$$

P) Calculate frequency.

a) 0.2 s. :-  $f = \frac{1}{T} = \frac{1}{0.2} = 5 \text{ Hz}$

b) Some :-  $f = \frac{1}{50} = 0.02 \text{ kHz}$ .

c) ~~Amplitude~~

d)  $T = \frac{1}{f} = \frac{1}{50} = \frac{1}{50} = 0.02 \text{ s}$

$$\omega = \frac{1}{T \text{ kHz}} = 1 \text{ rad/s}$$

$$T = \frac{1}{200 \text{ ms}} = -0.005 \text{ ms}$$

e) Given  $\omega = 30^\circ$

$$v(t) = 20 \sin \omega t$$

$$= 20 \sin 30^\circ$$

$$= 20 \times 0.5 \text{ sin } 30^\circ$$

$$= 10.89 \text{ V}$$

$$v(t) = 20 \sin 110^\circ$$

$$= 18.29 \text{ V}$$

$$v(t) = 20 \sin 148^\circ = 11.47 \text{ V}$$

$$v(t) = 20 \sin 325^\circ = -11.47 \text{ V}$$

f)

g)  $v(t) = 15 \sin 30^\circ$



$$\approx 7.5$$

$$v(t) = 15 \sin 90^\circ$$

$$15$$


$$v(t) = 15 \sin 45^\circ$$

$$= 10.60 \text{ V}$$

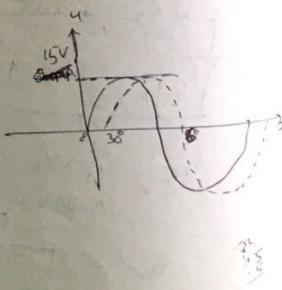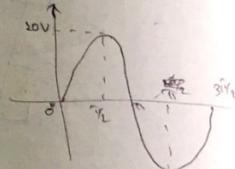


$$v(t) = 15 \sin 180^\circ = 0 \text{ V}$$
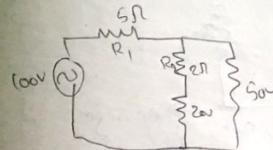
$$v(t) = 15 \sin 30^\circ = -12.99 \text{ V}$$


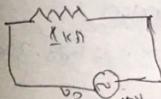
$$\sqrt{\frac{R^2 + X^2}{R^2}} = \sqrt{\frac{1^2 + 2^2}{1^2}} = \sqrt{5}$$





The function given to circuit is

$$v(t) = V_p \sin \omega t = 10 \sin \omega t$$

where known resistance is  $i(t) = \frac{v(t)}{R} = \frac{10}{1} = 10 \text{ A}$

$$Q_{avg} = \sqrt{\frac{1}{T} \int [v(t)]^2 dt}$$
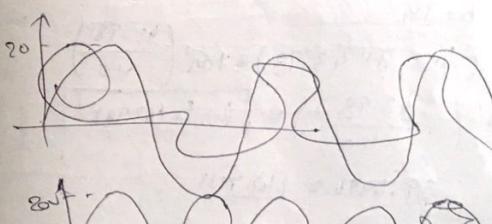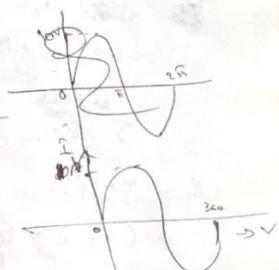
$$I = \frac{V_p}{R} = \frac{10}{1} = 10 \text{ A}$$




$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} 20 \sin \omega t d(\omega t)$$

$$= \frac{20}{\pi} (-\cos \omega t)$$

$$= 6.366 \times \{-\cos 0 - (\cos \pi)\}$$

$$= 3.183$$

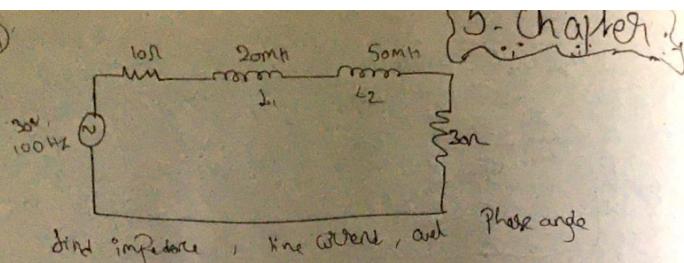

Find impedance, line current, and phase angle

$$V_m = 30 \quad f = 100\text{Hz} \quad \omega = 2\pi f$$

$$R = 10\Omega \quad \omega = 2\pi \times 100$$

$$= 200\pi \approx 628.31 \Omega$$
 ~~$X_L = 2\pi f L$~~ 

$$= 628.31 \times 30 \times 10^{-3}$$

$$= 18.849 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + 18.849^2} = 21.81 \Omega$$

$$X_L = j\omega L$$

$$= 628.31 \times 30 \times 10^{-6} = 1.8849 \times 100$$

$$= 18.849 \Omega$$

$$Z = R + jX_L$$


$$Z = (10 + j \times 18.849) \times \tan\left(\frac{43.98^\circ}{10}\right)$$

~~$Z = 10 \tan\left(\frac{43.98^\circ}{10}\right) \times \sqrt{(10)^2 + (18.849)^2}$~~

$$Z = 59.4496 \times 147.7133$$


Phase angle :-
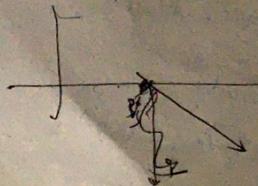
$$i_g = \frac{V_s}{Z} = \frac{30 \angle 0^\circ}{59.4496 \angle 147.71^\circ} = 0.5 \angle -147.71^\circ$$



$V_s$  leads  $i_g$  by  $42.21^\circ$

$$\theta = 42.21^\circ$$

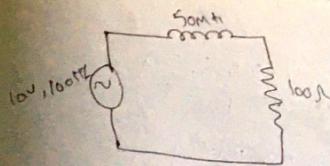

$$V = 10 \quad f = 100\text{Hz} \quad L = 30\text{mH}, R = 10\Omega$$

$$\omega = 2\pi f$$

$$= 2\pi \times 100 = 628.31$$

$$X_L = j\omega L$$

$$= 628.31 \times 30 \times 10^{-3} = 18.849 \Omega$$

~~$Z = R + jX_L = 10 + j18.849$~~ 

$$= (10 + j18.849) \tan\left(\frac{43.98^\circ}{10}\right)$$

$$= \sqrt{(10)^2 + (18.849)^2} \tan\left(\frac{314.515^\circ}{100}\right)$$

$$= \sqrt{10000 + 314.515^2} = 189.817$$

Phase angle :-  $i_g = \frac{V_s}{Z} = \frac{10 \angle 0^\circ}{189.817} = -0.0031831$

$$Z = R + jX_L$$

~~$Z = 100 + j(-0.0031831) \tan\left(\frac{-0.0031831}{100}\right)$~~

~~$= \sqrt{(100)^2 + (-0.0031831)^2} \tan\left(\frac{-0.0031831}{100}\right)$~~


~~$= \sqrt{10000 + 0.0001} = 100 \tan\left(-1.799 \times 10^{-5}\right)$~~

$$= \frac{10 \angle 0^\circ}{100 \tan(1.799 \times 10^{-5})} = 0.1 \angle 1.799 \times 10^3$$



$$= 0.1 \angle 0.0031831$$

$$\begin{aligned}
 Z &= R + jX_L \\
 &= 100 + (31415.9) \tan^{-1} \left( \frac{31415.9}{100} \right) \\
 &= \sqrt{(100)^2 + (31415.9)^2} \tan^{-1} \left( \frac{31415.9}{100} \right) \\
 &= 104.818 \angle 17.993^\circ \\
 &= i = \frac{V_S}{Z} = \frac{10 \angle 0^\circ}{104.818 \angle 17.993^\circ} = 0.0951 \angle -17.993^\circ
 \end{aligned}$$

$$V_S = iR = 0.0951 \times 100 = 9.51V$$

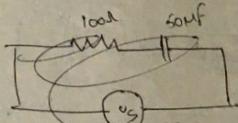

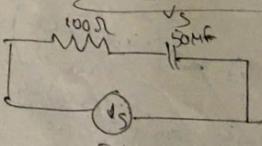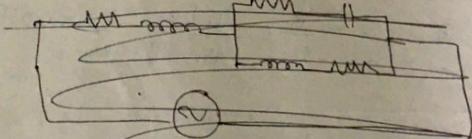$V_S = 50\text{V}$   $\rightarrow R = 100\Omega$ ,  $\omega C = 50\text{Hz}$



$$R = 100\Omega, C = 50\mu\text{F}$$

$$V_S = ? \quad f = 50\text{Hz}$$

$$\omega = 2\pi f$$


$$= 2\pi \times 50 = 100\pi = 314.15$$

$$(R = X_L = \sqrt{50})$$

Impedance Diagram:-

\* Series of R-L circuit
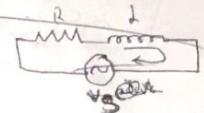
$$X_L = \omega L \rightarrow \text{Inductance}$$



$$\because G = \frac{1}{R}$$

$$\text{Impedance: } Z = \sqrt{R^2 + (j\omega L)^2}$$

$$Z = (R + j\omega L)\Omega$$

$$Z = \sqrt{R^2 + (X_L)^2} \Omega \quad (\text{induced voltage leads})$$

$$\text{Current } I = \frac{V_S}{Z} = A$$


$$\text{Phase angle } \theta = \tan^{-1} \left( \frac{X_L}{R} \right)$$

\* Polar form of total impedance  $Z =$

$$\text{Voltage across resistance } V_R = IR$$

$$\text{" " " inductive resistance } V_L = I X_L \cdot V$$
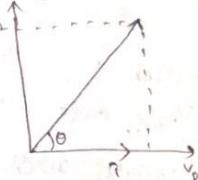
$$\begin{aligned}
 M.H. &= 10 \\
 1\text{HF} &= 10^6 \\
 \tan \left( \frac{b}{a} \right)
 \end{aligned}$$



\* Series of R-C circuit: (Capacitor voltage lags)

$$X_C = \frac{1}{\omega C}, X_C = \frac{1}{2\pi f C}$$

$$Z = \left( R + j \frac{1}{\omega C} \right) \Omega$$

$$Z = (R - j\omega C)\Omega$$

$$Z = \sqrt{R^2 + (X_C)^2}$$


$$\theta = \tan^{-1} \left( -\frac{X_C}{R} \right)$$

$$I = V_S / Z$$

$$\text{Capacitive voltage } V_C = I X_C$$


$$\text{Resistive voltage } V_R = IR$$
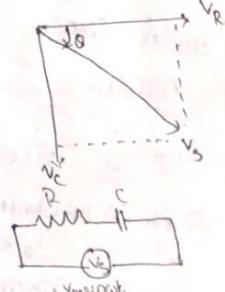
$$\text{Total voltage applied } V_S = V_R - jV_C$$



=  $v_{msin\omega t}$

### \* Series of RLC Circuits:-

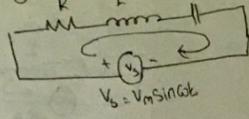

$$X_L = \omega L = 2\pi f L$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = -2\pi f C$$

$$\text{impedance } Z = (R + jX_L + j(X_C)) \Omega$$

$$Z = \sqrt{R^2 + j(X_L)^2 + j(X_C)^2}$$

$$\text{Current } I = \frac{V_s}{Z}$$

$$\text{Phase angle } \theta = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

$$\text{Voltage across } V_R = IR$$

$$\text{" " Capacitive resistance } = jX_C$$

$$\text{" " inductive " } = jX_L$$


### \* Parallel Circuits:-

Rc circuit:-

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = -2\pi f C$$

Current in Resistance

$$I_R = \frac{V_s}{R}$$

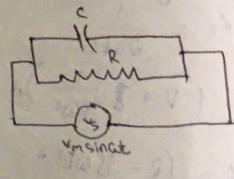

(current lags)

Current in Capacitive

$$I_C = \frac{V_s}{X_C}$$

$$\text{Total current in two branches } = I_T = (I_R + I_C) A$$

In polar form :- change in angles

$$\text{Impedance } Z = \frac{V_s}{I_T} = \frac{V_s \angle 0^\circ}{I_T \angle \theta}$$

### \* The RL Circuits:-

$$X_L = \omega L = 2\pi f L$$

$$I_R = \frac{V_s}{R}$$



$$I_{LR} = \frac{V_s}{Z_L} =$$

$$\text{total current } I_T = (I_R + I_L)$$

change in Polar form

(current lags behind voltage)
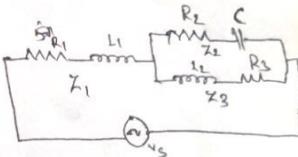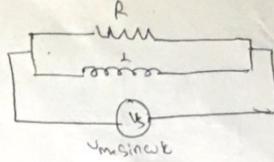
$$\text{impedance } Z = \frac{V_s}{I_T}$$



### \* Compound Circuits:-

here  $Z_1$  is in series, and  $Z_2$  and  $Z_3$  are in parallel


$$\text{now:- } Z_1 = (R_1 + jL_1) \Omega$$

$$Z_2 = (R_2 + jC_2) \Omega$$

$$Z_3 = (R_3 + jL_3) \Omega$$

$$\text{Total impedance } Z_T = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3}$$

Phase angle :-

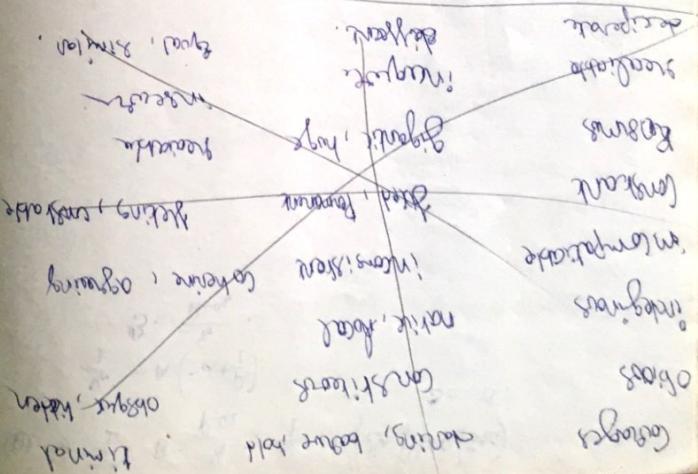

# Network Analysis:-

## 3. Useful theorems in Circuit analysis.

(1)

### 1) Thevenin's Theorem:-





Statement:- Any two terminal bilateral linear dc. circuit can be replaced by equivalent circuits consisting voltage source and series resistors.

Explanation:-

Let us consider a simple dc circuit as shown in fig (a)  
we are to find  $I_L$  by Thevenin's theorem.

In order to find the equivalent voltage source  $\gamma_1$  is removed  
and  $V_{oc}$  is calculated.
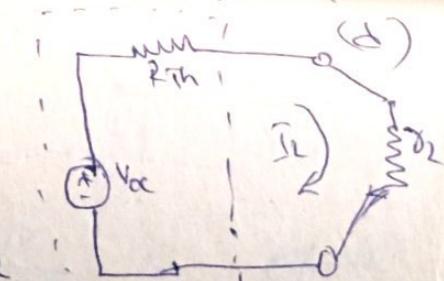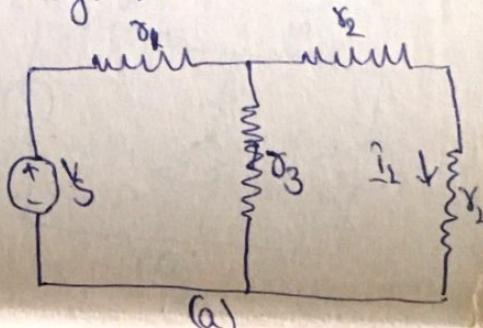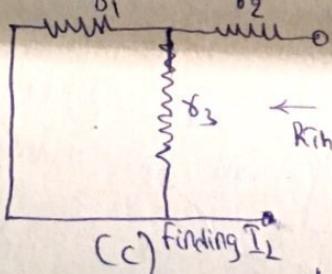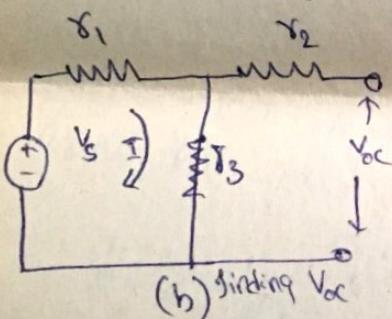
$$V_{oc} = \gamma_3 = \frac{V_s}{\gamma_1 + \gamma_3} \cdot \gamma_3$$



Next to find the internal resistance of the network in series with  $V_{oc}$  the voltage source is moved by a short circuit as shown in fig(c) source network

$$R_{th} = \gamma_2 + \frac{\gamma_1 \gamma_3}{\gamma_1 + \gamma_3}$$

As per Thevenin's Theorem the equivalent circuit being

$$I_L = \frac{V_{oc}}{R_{th} + \gamma_2} \cdot A.$$

\* Steps for solving source network is:-

- 1) Remove the load resistance  $R_L$  and find the open circuit voltage across open circuited load terminals.
- 2) Deactive the constant sources and find internal resistance of the source of side looking through open circuited load terminals. Let this resistance be  $R_{th}$ .




- 3) Obtain Thevenin's equivalent circuit by placing  $R_{th}$  in series with  $V_{oc}$
- 4) Reconnect  $R_L$  across the load terminals as shown in fig(d)  
(Obviously),  $i$  (load current)

$$I_{th} = \frac{V_{oc}}{R_{th} + R_L}$$

## Q) Superposition Theorem:-

Statement:- This Th finds use in solving a network where two or more sources are present and connected either in series or in parallel.

Explanation:-

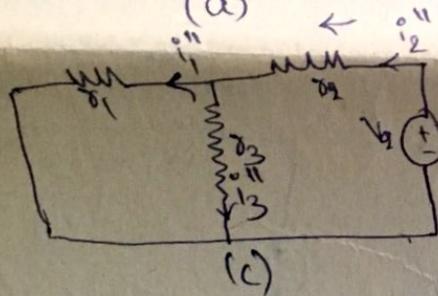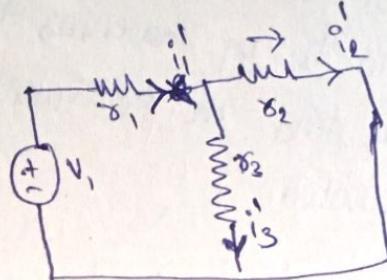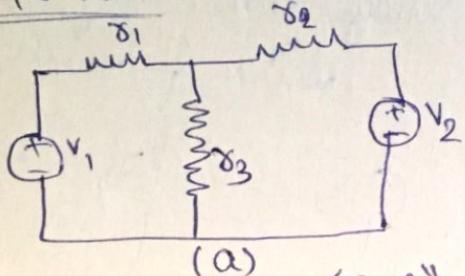

Let us first take the source  $V_1$  alone at first replacing  $V_2$  by short circuit

$$i_1' = \frac{V_1}{r_1 + r_3}; i_2' = \frac{r_3}{r_2 + r_3} i_1' ; i_3' = i_1' - i_2'$$

Let the circuit be energised

next removing  $V_1$  by short circuit

$$\text{by only } i_2'' = \frac{V_2}{r_1 + r_3 + r_2} \text{ and } i_1'' = i_2'' \cdot \frac{r_3}{r_1 + r_2} \\ i_3'' = i_2'' - i_1''$$

As per Superposition theorem:-

$$i_3 = i_3' + i_3''$$

$$i_2 = i_2' - i_2''$$


$$i_1 = i_1' - i_1''$$

## Millman's Theorem:-

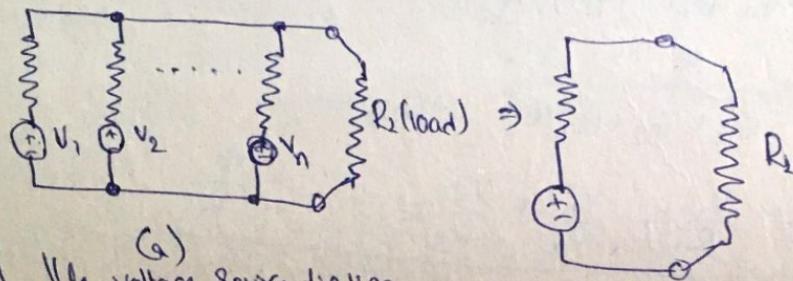(2)

Statement:- The utility of this th is that any no:- of like voltage sources can be reduced to one equivalent one.

\* when a no:- of voltage sources ( $V_1, V_2, \dots, V_n$ ) are in like having internal resistance ( $R_1, R_2, R_3, \dots, R_n$ ) respectively. The argument can be replaced by single equivalent voltage source  $V$ , Series Resistance ' $R$ '



(a) No of like voltage source finding power to a load resistance


(b) Equivalent voltage and resistance of the source network following

As per Millman's th:-

$$V = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}; R = \frac{1}{G_n} = \frac{1}{G_1 + G_2 + \dots + G_n}$$

Explanation:-

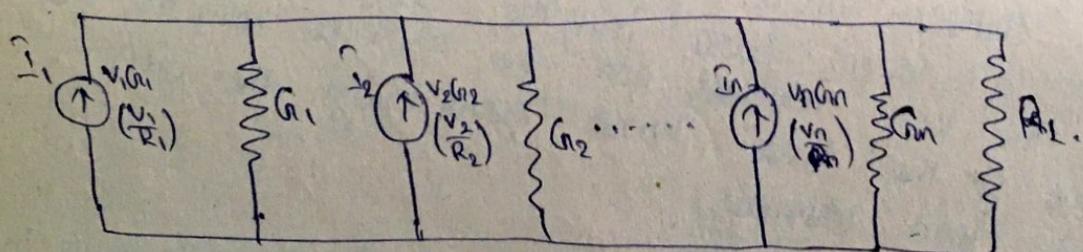Assuming a dc network of numerous like voltage sources with internal resistance supplying power to a load resistance  $R_L$ , all voltage sources are connected to current source as shown below





Let  $I$  represents the resultant current of the current sources

while  $G_n$  the equivalent conductance

$$I = I_1 + I_2 + I_3 + \dots + I_n; G_n = G_1 + G_2 + G_3 + \dots + G_n$$

~~Note~~

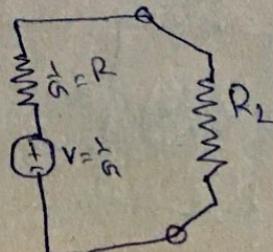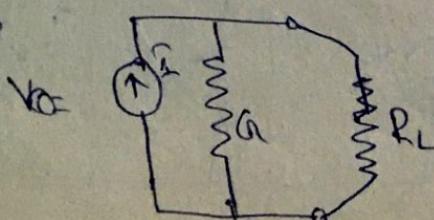

next the resulting Current Source is converted to an equivalent voltage source as depicted in fig above

$$\text{Thus : } R_{\text{eq}} \cdot I = I = VR \Rightarrow V = \frac{I}{R}$$

$$V = \frac{I}{R} = \frac{\pm I_1 + \pm I_2 + \pm I_3 + \pm I_4 + \dots + \pm I_n}{G_1 + G_2 + G_3 + G_4 + \dots + G_n}$$

+ and - ve sign appeared to include the cases where sources is connected to may be supplying current in the same direction

$$R = \frac{1}{G} = \frac{1}{G_1 + G_2 + G_3 + \dots + G_n}$$

$$V = \frac{\pm \frac{V_1}{R_1} \pm \frac{V_2}{R_2} \pm \frac{V_3}{R_3} \pm \dots \pm \frac{V_n}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}}$$


where 'R' is equivalent resistance connected with equivalent value source in series.

$$V = \frac{\pm V_1 G_1 \pm V_2 G_2 \pm V_3 G_3 \pm V_4 G_4 + \dots + V_n G_n}{G_1 + G_2 + G_3 + \dots + G_n}$$

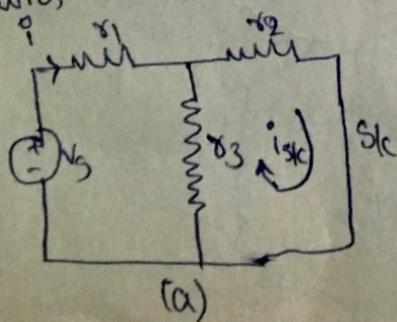
### Norton's Theorem:-

Statement:- A linear active network consisting of independent and dependent voltage and current source and linear bilateral network elements can be replaced by an equivalent circuit consisting of a current source being the short circuited current across the load terminal and the resistance being the internal resistance of the source network looking through the open circuited load terminals.

Explanation:- In order to find the current through  $\delta_2$  the load resistance by Norton's Th, let us replace  $\delta_2$  by short circuit.



(a)

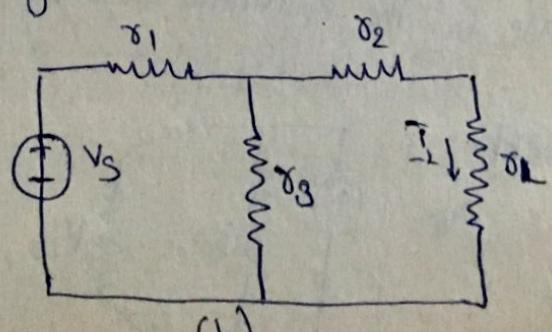


(b)

Obviously:-

$$i = \frac{V_s}{\gamma_1 + \frac{\gamma_2 \gamma_3}{\gamma_2 + \gamma_3}} \quad \text{and} \quad i_{sc} = \frac{V_s}{\gamma_2 + \gamma_3}$$

Next, the short circuit is removed and the independent source is deactivated as done in Thevenin's Th.

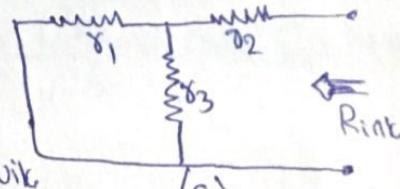
From fig (c)  $R_{int} = \gamma_2 + \frac{\gamma_1 \gamma_3}{\gamma_1 + \gamma_3}$



As per Norton's Th, the equivalent source circuit would contain a current source in parallel to the internal resistance the current source being the short circuited voltage across the shorted terminals of the load resistor (from fig (d))

obviously  $i_L = i_{sc} \cdot \frac{R_{int}}{R_{int} + \gamma_2}$

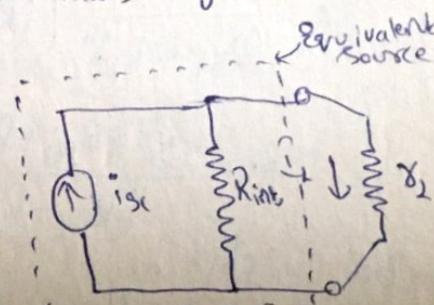It may be noted here that determination of  $R_{int}$  for the source system Norton's theorem is identical to that of Thevenin's theorem already described.





### Maximum Power Transfer Th:-

This Th is used to find the value of load resistance for there would be maximum amount of power transferred from source to load.

Statement:- A resistance receives maximum power to internal resistance terminal.

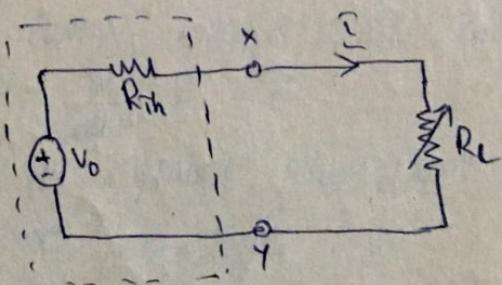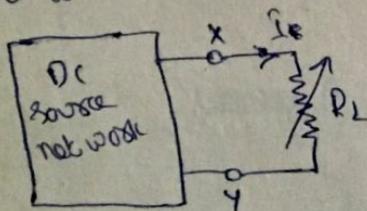load being connected to dc network when the load resistance is equal of source network as seen from load



with reference to fig

$$i = \frac{V_o}{R_{int} + R_L} \rightarrow ①$$

while the power delivered to resistive load is

While the Power delivered to the resistive load is from Eq(1)  $P_L = \frac{V_0^2}{R_{Th} + R_L} \times R_L \rightarrow ②$

$P_L$  can be maximized by varying  $R_L$  and hence, maximum power can be delivered when  $(dP_L/dR_L) = 0$

However:-  $\frac{d(P_L)}{dR_L} \geq \frac{dR_L}{dR_L} \left[ \frac{1}{(R_{Th} + R_L)^2} \right] \times$   $\frac{\frac{d}{dx}(u/v)}{u \cdot \frac{dv}{dx} - v \cdot \frac{du}{dx}}$

$$\approx \left[ (R_{Th} + R_L)^2 \cdot \frac{d}{dR_L} (V_0^2 R_L) - V_0^2 R_L \cdot \frac{d}{dR_L} (R_{Th} + R_L)^2 \right] \rightarrow ③$$

$$= \frac{1}{(R_{Th} + R_L)^4} \left\{ (R_{Th} + R_L)^2 V_0^2 - V_0^2 R_L \times 2(R_{Th} + R_L) \right\} \rightarrow ④$$

$$= \frac{V_0^2 (R_{Th} + R_L - 2R_L)}{(R_{Th} + R_L)^3} = \frac{V_0^2 (R_{Th} - R_L)}{(R_{Th} + R_L)^3} \rightarrow ⑤$$

$$\text{But: } \frac{dP_L}{dR_L} = 0 \Rightarrow \frac{V_0^2 (R_{Th} - R_L)}{(R_{Th} + R_L)^3} = 0 \rightarrow ⑥$$

$$R_{Th} - R_L = 0 \Rightarrow R_{Th} = R_L$$

Hence it is proved that Power transfer from dc source network is resistive network is maximum when internal resistance of dc network is equal to load resistance.

Again here  $R_{Th} = R_L$ . Substituting in ②

$$P_{max} = \left( \frac{V_0^2 R_{Th}}{(R_{Th} + R_{Th})^2} \right)^2 = \frac{V_0^2 R_{Th}}{4 R_{Th}^2} = \frac{V_0^2}{4 R_{Th}}$$

This is Power consumed by the load.  
load Power and source Power being the same  
The total Power supplied is thus.

$$P = 2 \cdot \frac{V_0^2}{4 R_{Th}} = \frac{V_0^2}{2 R_{Th}}$$

During max power transfer the efficiency  $\eta$  becomes

$$\eta = \frac{P_{max}}{P} \times 100 = 50\%$$


4

## Compensation Th:-

Statement:- In a linear time-invariant network when the resistance ( $R$ ) of an uncoupled branch, carrying a current ( $I$ ) is changed by ( $\Delta R$ ) the currents in all branches would change and can be obtained by assuming that an ideal voltage source of ( $V_c$ ) has been connected [such that  $V_c = I(\Delta R)$ ] in series with ( $R + \Delta R$ ) when all other sources in network are replaced by their internal resistance.


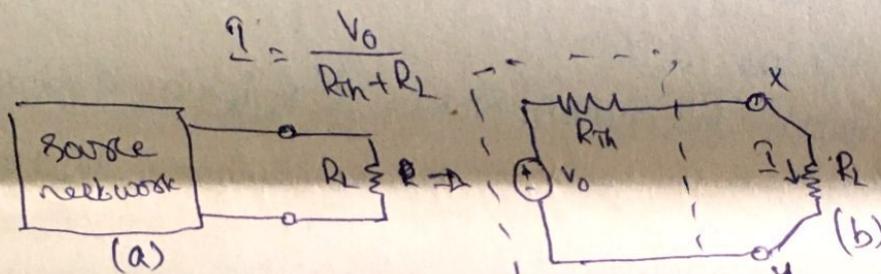
## Explanation:-

Let us assume a load  $R_L$  be connected to a dc source network whose Thevenin equivalent gives  $V_0$  as the Thevenin voltage and  $R_{th}$  as Thevenin resistance as evident from fig (a)



Let the load resistance  $R_L$  be changed to  $(R_L + \Delta R_L)$  since the rest of the circuit remains unchanged, the Thevenin equivalent network remains the same

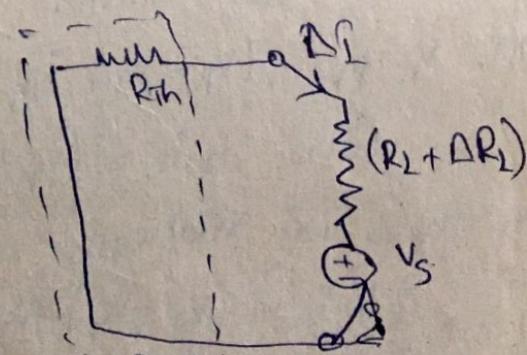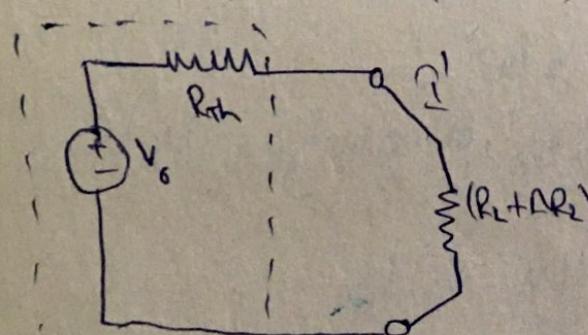Note:-  $I' = \frac{V_0}{R_{th} + (R_L + \Delta R_L)}$



The change of current being denoted as  $\Delta I$ , we find

$$\Delta I = I' - I$$

$$= \frac{V_0}{R_{th} + (R_L + \Delta R_L)} - \frac{V_0}{R_{th} + R_L}$$

$$\frac{V_o(R_{Th} + R_L - (R_{Th} + R_L + \Delta R_L))}{(R_{Th} + R_L + \Delta R_L)(R_{Th} + R_L)}$$

$$= -\left(\frac{V_o}{R_{Th} + R_L}\right) \cdot \frac{\Delta R_L}{R_{Th} + R_L + \Delta R_L} = -\frac{\Delta R_L}{R_{Th} + R_L + \Delta R_L}$$

$$= -\frac{V_c}{R_{Th} + R_L + \Delta R_L}$$

$V_c$  is equal to  $\dot{I}(\Delta R_L)$  and is termed as (Compensating voltage)

### \* Tellegen's Th:-

Statement:- Tellegen's Th. is applicable to any network made up of lumped two terminal elements.

for any given time, the sum of power delivered to each branch of any electric network is zero

thus for  $k^{\text{th}}$  branch this theorem states  $\sum_{k=1}^n V_k i_k = 0$ ;  $n$  being the number of branches  $V_k$  the drop in the branch and  $i_k$  the branch current.

### Explanation:-

Let  $i_{pq} (= i_k)$  =  $k^{\text{th}}$  branch through current.

$V_k$  = Voltage drop in branch  $k = V_p - V_q$  while  $V_p$  and  $V_q$  are the respectively node voltages at P and Q nodes.


We have  $V_k i_{pq} = (V_p - V_q) i_{pq} = V_k i_k$

(also  $V_k i_k = (V_q - V_p) i_{qp}$ , obviously  $i_{qp} = -i_{pq}$ )

Summing these two relations

$$V_k i_k = (V_p - V_q) i_{pq} + (V_q - V_p) i_{qp}$$
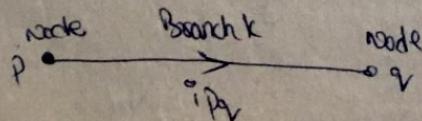
$$V_k i_k = \frac{1}{2} [(V_p - V_q) i_{pq} + (V_q - V_p) i_{qp}]$$



Such an Eq can be written for every branch (5) of the network assuming n branches generalization yields

$$\sum_{k=1}^n V_k i_k = \frac{1}{2} \sum_{p=1}^n \sum_{q=1}^n (V_p - V_q) i_{pq}$$

$$= \frac{1}{2} \sum_{p=1}^n V_p \left( \sum_{q=1}^n i_{pq} \right) - \frac{1}{2} \sum_{q=1}^n V_q \left( \sum_{p=1}^n i_{pq} \right)$$

However following Kirchhoff's current law the algebraic sum of currents at each node is equal to zero

$$\sum_{p=1}^n i_{pq} = 0; \sum_{q=1}^n i_{qp} = 0$$

with this finally we get  $\sum_{k=1}^n V_k i_k = 0$

### Problems:-

Thevenin's Th:-

In a circuit network therefore current through  $10\Omega$  resistor utilising

Thevenin's Th:-

Sol:- In the Given Circuit Voltages of

$$V_1 = 10V; V_2 = 12V; V_3 = 20V$$

$$\gamma_1 = 2\Omega; \gamma_2 = 5\Omega; \gamma_3 = 10\Omega; \gamma_4 = 10\Omega$$

Let the resistance  $\gamma_4$  be removed and

below circuit

At nod 'c' application of KCL yields

$$i_1 + i_3 - i_2 = 0$$


$$W.R. \frac{V}{R}$$

$$\frac{V_1 - V_{oc}}{\gamma_1} + \frac{V_3 - V_{oc}}{\gamma_3} - \frac{V_{oc} + V_2}{\gamma_2} = 0.$$

Summing the open circuits of fig (C).


terminal X-Y to be  $V_{oc}$  is obviously

The potential at 'c' node is  $V_{oc}$

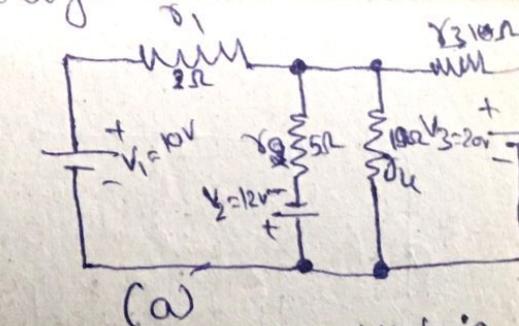


(a)

the circuit exhibited in

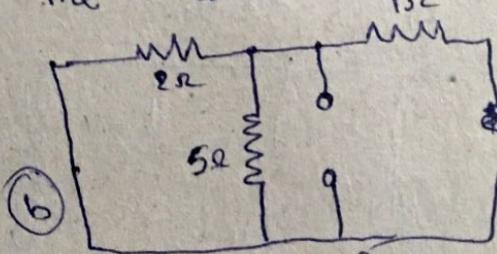

(b)

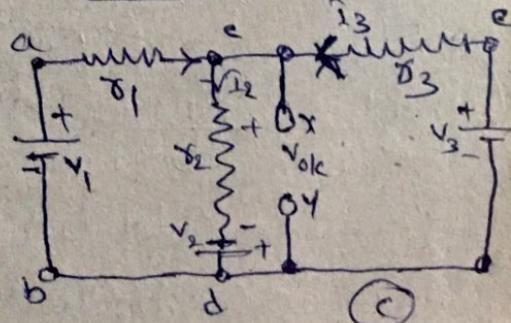

(c)

$$\frac{10 - V_{oc}}{2} + \frac{20 - V_{oc}}{1} - \frac{V_{oc} + 12}{5} = 0$$

$$-0.5V_{oc} - V_{oc} - 0.2V_{oc} = 20.4 \approx 20.5$$

$$1.07V_{oc} + 22.6V$$

$$V_{oc} = 13.29V$$


$$\therefore \text{here } \frac{1}{R_{Th}} = \frac{1}{2} + \frac{1}{5} + \frac{1}{1}$$

$$R_{Th} = \frac{10}{17} \Omega$$


Thevenin's Eq circuit being shown in fig (c)

$$I_u = T_{Th} = \frac{V_{oc}}{R_{Th} + R_u}$$

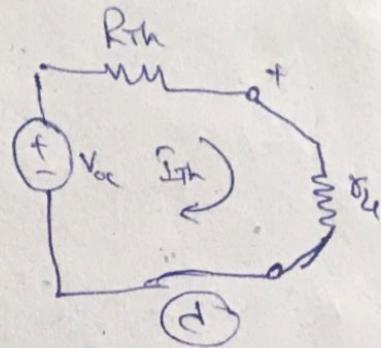
$$I_u = \frac{13.29}{\frac{10}{17} + 10} = 1.26A$$



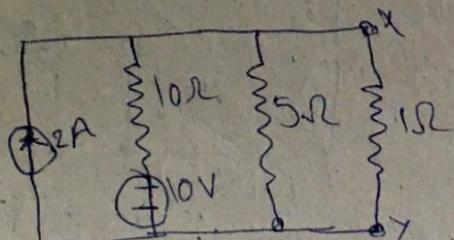Q2) Given an circuit of fig find the power 188 in 1Ω resistor by Thevenin's Th: -



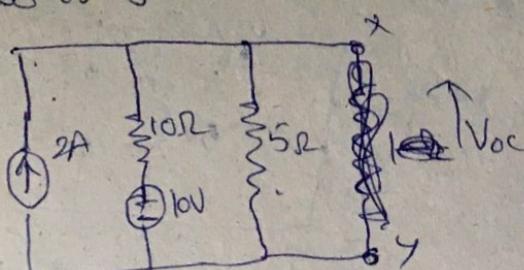Q3) Let us first remove 10Ω resistor from x-y terminal



now Applying KCL at x-y junction

when  $I = 2$  another voltage of 10V

source are 5, 10.

$$\left(\because I = \frac{V}{R}\right) \frac{V_{oc}}{5} + \frac{V_{oc} - 10}{10} = 2$$

$$0.2V_{oc} + 0.1V_{oc} - 1 = 2$$

$$0.2V_{oc} + 0.1V_{oc} - 1 = 2 \Rightarrow \cancel{V_{oc}} = 0.3$$

$$\therefore V_{oc} = \frac{0.3}{0.2} =$$

$$V_{oc} (0.2 + 0.1) = 3$$

(6)



$$V_{oc} (0.3) = 3$$

$$V_{oc} = 10 \text{ V}$$

$$\text{here } \frac{1}{R_{Th}} = \cancel{\frac{1}{10}} + \cancel{\frac{1}{50}} + \frac{1}{5} + \frac{1}{10}$$

$$\frac{1}{R_{Th}} = \frac{10 + 5}{50} = \frac{15}{50}$$

$$R_{Th} = \frac{50}{15} = 3.33 \Omega$$

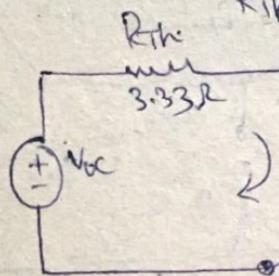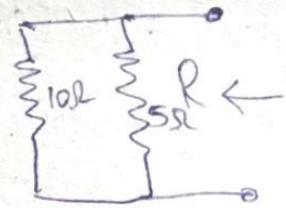

here 1 ohm resistor is given by


$$I_{Th} = \frac{V_{oc}}{R_{Th} + \cancel{1}} = \frac{10}{3.33 + 1} = \frac{10}{4.33} = 2.307$$

Power loss in 1 ohm resistor is  $P = I^2 R = (2.30)^2 \times 1 = 5.3255$ ,


Paste paper:-

Given an circuit and we are to find 1 ohm resistor

in the figure:-

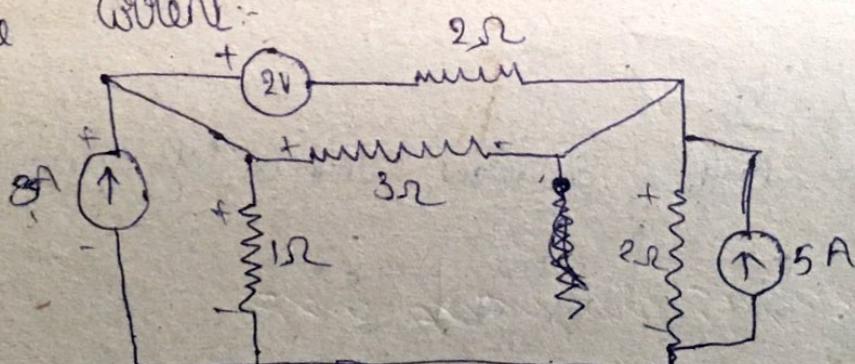

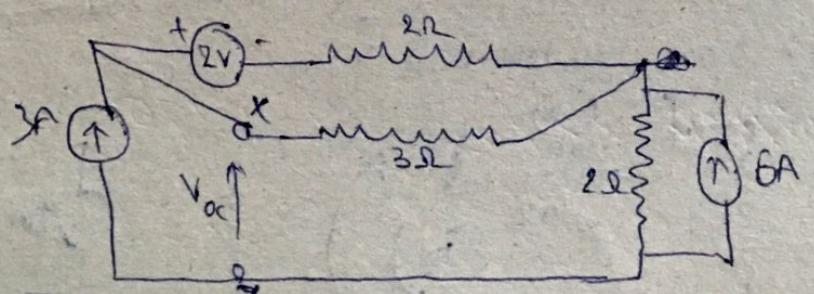Let us remove the 1 ohm resistor using X-Y terminals



W.L.F.:-  $I = \frac{V}{R}$

Now apply KCL to above circuit of XY terminals

$$\frac{V_{oc}-2}{2} + \frac{V_{oc}}{3} = 3A$$

$$0.5V_{oc} - 1 + 0.33V_{oc} = 3$$


$$V_{oc}(0.5 + 0.33) - 1 = 3$$

$$V_{oc} = \frac{4}{0.833} = 4.8019V$$

$$V_{oc} = 4.8019V$$

$$\text{Now } V_{xy} = \frac{5 \times 2}{2+3} = 10V$$

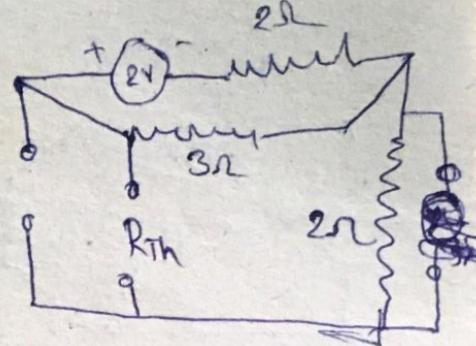Obviously  $V_{xy}$  is identical to  $V_{th}$




$$R_{Th} \approx \frac{1}{R_{Th}} = \frac{1}{\frac{2 \times 3}{2+3}} = \frac{2+3}{2 \times 3} = \frac{5}{6}$$

$$R_{Th} = \frac{6}{5} = 1.2\Omega$$


$$I_{12} = I = \frac{V_{oc}}{R_{Th} + 1} = \frac{4.8019}{1.2 + 1} = \frac{4.8019}{2.2} = 2.1826818A$$

Norton's Th:-

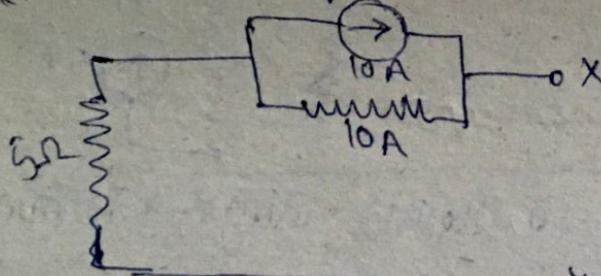B) find Norton's equivalent circuit to left of terminals X, Y




Now short the terminals X-Y

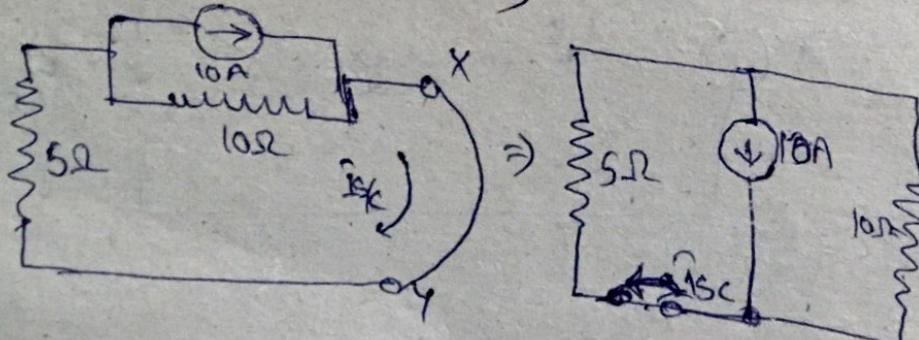

~~I<sub>SC</sub>~~ is current through the 5Ω resistor (T)

$$I_{SC} = 10 \times \frac{10}{10+5} = 6.67 \text{ A} \quad (\because I_{SC} = \frac{V_3}{R_3 + R_2})$$

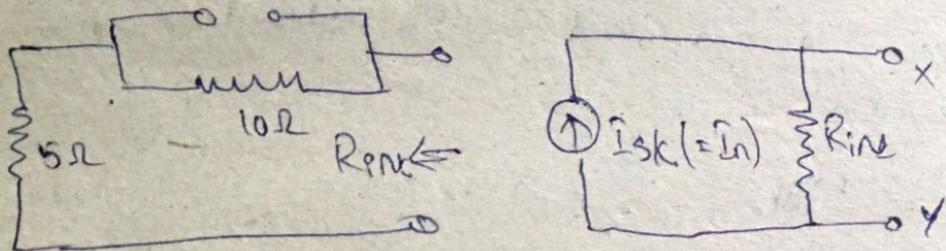
To determine the equivalent resistance  $R_{in}$  short circuit  
y of circuit looking through X-y Constant source is  
deactivated as shown in fig.



$R_{in} = 10 + 5 = 15 \Omega$  has been shown in  
Norton's equivalent circuit.

$$I_n = 6.67 \text{ A} ; R_{in} = 15 \Omega$$

P) find current in 5Ω resistor.

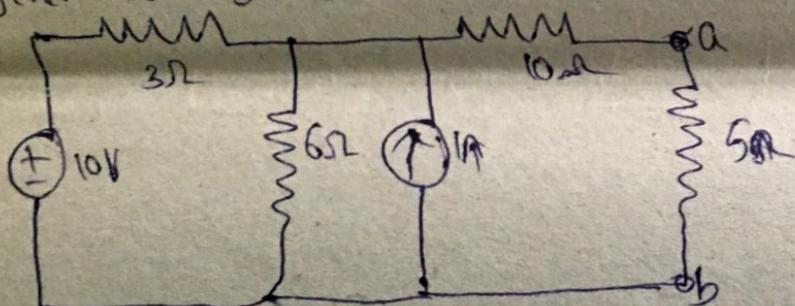

Sol. Let us first remove 5Ω resistor and short the  
a-b terminals.


Assuming the voltage to be +ve at node 1 in fig.

$$\frac{V - 10}{3} + \frac{V - 1}{6} + \frac{V}{10} = 0$$

$$0.33V - 3.33 + 0.16V + 0.1V = 0$$

$$V(0.33 + 0.16 + 0.1) = 3.33 + 1$$
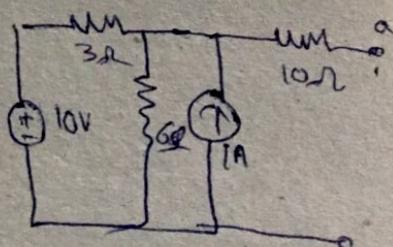
$$V = \frac{4.33}{0.59} = 7.33 \text{ V}$$



Apply KVL at right most loop (1-a,b-2)


$$-V + i_{sc} \times 10 = 0$$

$$-7.22 \times 10 i_{sc} = 0$$

$$i_{sc} = 0.722 \text{ A (In)}$$

To find Norton's equivalent resistance through a**1**, b, 5-21  
resistor removed and all the constant sources are deactivated
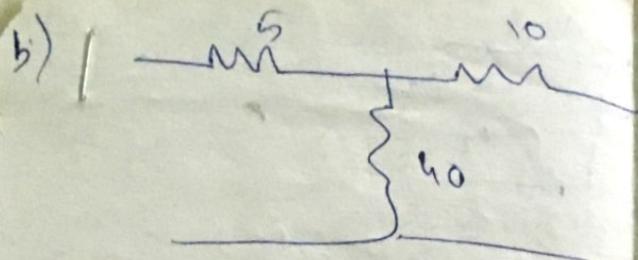
$$\text{here } R_{eq} = \frac{3 \times 6}{3+6} + 10 = 12 \Omega$$



E Parallel

$$V_1 = Z_{11} \hat{I}_1 + Z_{12} \hat{I}_2$$

$$V_2 = Z_{21} \hat{I}_1 + Z_{22} \hat{I}_2$$

when  $\hat{I}_2 = 0$  then

$$Z_{11} = \frac{V_1}{\hat{I}_1} \Big|_{\hat{I}_2=0}$$

$$\bullet V_1 = 13 \hat{I}_1$$

$$Z_{11} = \frac{13 \hat{I}_1}{\hat{I}_1} = 13 \Omega$$

$$Z_{21} = \frac{V_2}{\hat{I}_1} \Big|_{\hat{I}_2=0} \quad \text{--- } 2$$

$$V_2 = \hat{I}_1 \times \left( \frac{10}{40+10} \right) \times 40$$

$$V_2 = \cancel{10} \times 0.4 \times 40$$

$$\text{now:- } Z_{21} = \cancel{10} \times 0.4 = 8 \Omega$$

when  $\hat{I}_1 = 0$  then

$$Z_{12} = \frac{V_1}{\hat{I}_2} \Big|_{\hat{I}_1=0}$$






$$V_1 = \frac{\hat{I}_2}{40} \times 10 =$$

$$\Rightarrow \hat{I}_2 \times 0.4$$


$$Z_{12} = \frac{\hat{I}_2 \times 0.4}{\hat{I}_2} = 0.4 \Omega$$

$$V_1 = \hat{I}_1 \quad \hat{I}_2$$

$$V_2 = \hat{I}_1 \quad \hat{I}_2$$

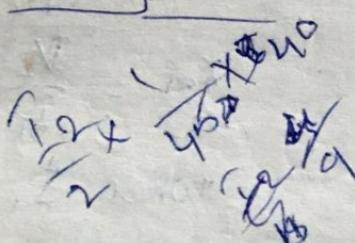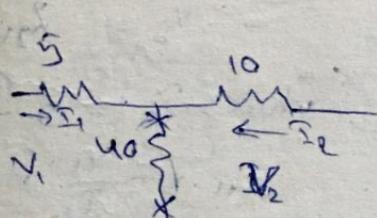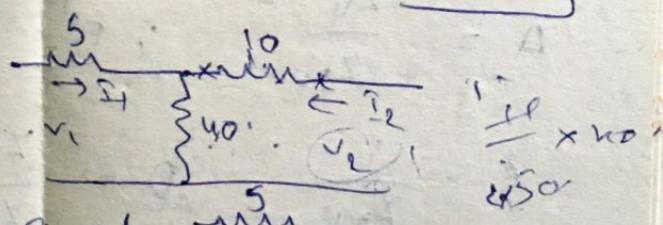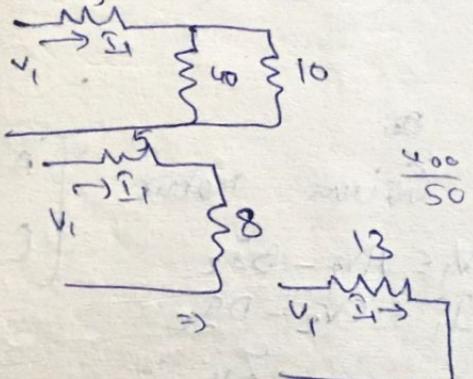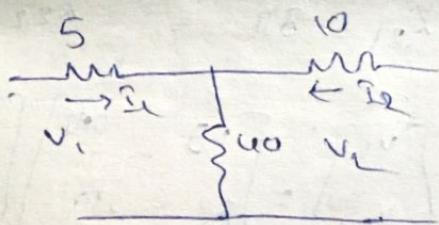

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

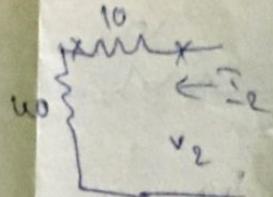

$$V_2 = Z_2 \times 10$$

$$Z_{22} = \frac{Z_2 \times 10}{Z_2} = 10\Omega$$

$$\therefore Z_{11} = 13\Omega ; \quad Z_{12} = 0.2\Omega$$

$$Z_{21} = 8\Omega$$

$$Z_{22} = 10\Omega$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 13 & 0.4 \\ 8 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}.$$

3)  $\ddot{\text{Z}}_2$

Given matrix

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 2 & 8 \\ 9 & 16 \end{bmatrix}$$

$$A = \frac{Z_{11}}{Z_{21}} \quad ; \quad B = \frac{Z_{12}}{Z_{21}}$$

$$V_2 = \frac{V_1 + BI_2}{A}$$

$$C = \frac{1}{Z_{21}} \quad D = \frac{Z_{22}}{Z_{21}}$$

$$\therefore V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

when  $I_2 = 0$

$$Z_{11} = \frac{V_1}{I_1} \Rightarrow \frac{AV_2}{CI_2} = \frac{A}{C} = \frac{2}{9} = 0.22\Omega$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{V_2}{CI_2} = \frac{1}{C} = \frac{1}{9} = 0.11\Omega$$

when  $I_1 = 0$

$$\text{find } H_2 = \frac{V_2}{I_2} = \frac{AV_2 - BI_2}{C} \quad V_1 = AV_2 - BI_2 \Rightarrow \frac{V_1 + BI_2}{A} = V_2$$


$$Z_{12} = \frac{C(AV_2 - BI_2)}{C}$$

$$Z_{12} = \frac{\Delta T}{C} = \frac{1AB - BC}{C} = \frac{32 - 72}{9} = \frac{-40}{9} = -4.44 \Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_2=0} = \frac{D}{C} = 1.77 \Omega$$

$$\begin{pmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{pmatrix} = \begin{pmatrix} 0.22 & -4.44 \\ 0.11 & 1.77 \end{pmatrix}.$$

1)  $\gamma$ -parameter

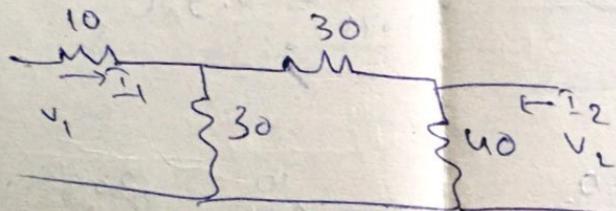


$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$


$$\begin{aligned} I_1 &= V_1 & V_2 \\ I_2 &= V_1 & V_2 \end{aligned}$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$
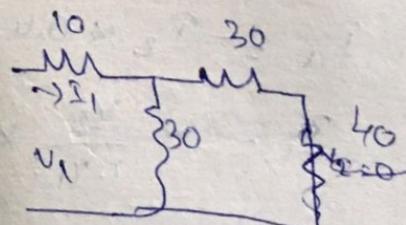
$$V_1 = 25 \times I_1 \Rightarrow I_1 = \frac{V_1}{25}$$



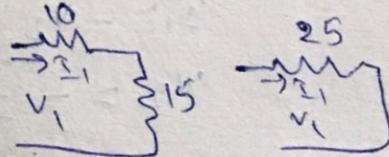
$$Y_{11} = \frac{I_1}{25 \times V_1} = \frac{1}{25} = 0.04 \Omega$$



$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$-I_2 = \frac{I_1}{30+30} \times 30$$

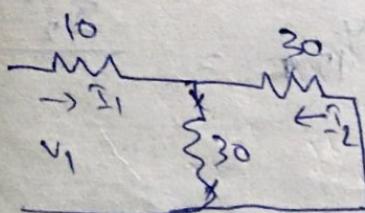

$$-I_2 = I_1 \times 0.5 \Rightarrow I_2 = -\frac{V_1}{25} \times 0.5 \Rightarrow I_2 = V_1 \times 0.02$$

as shown in fig

$$\gamma_{21} = \frac{\dot{I}_2}{V_1}$$

$$\gamma_{21} = \frac{\dot{I}_2}{\frac{\dot{I}_2}{\frac{10}{70}} + \frac{30}{70}} \Rightarrow -\frac{0.02 \times \dot{I}_2}{\dot{I}_2} = -0.02 \Omega$$

when  $V_1 = 0$

$$\gamma_{22} = \frac{\dot{I}_2}{V_2} \Big|_{V_1=0}$$

$$V_2 = \dot{I}_2 \times \frac{120}{70}$$

$$V_2 = \dot{I}_2 \times \frac{1.71}{70} \Rightarrow \dot{I}_2 = \frac{V_2}{1.71}$$

$$\gamma_{22} = \frac{\dot{I}_2 \times 1.71}{1.71} = \frac{1}{1.71} = 0.5 \Omega$$

$$\gamma_{12} = \frac{\dot{I}_2}{V_2} \Big|_{V_1=0}$$

$$-\dot{I}_1 = \frac{\dot{I}_2}{70} \times 30$$

$$-\dot{I}_1 = \dot{I}_2 \times 0.42 \Rightarrow \dot{I}_1 = \frac{V_2}{1.71} \times 0.42$$

$$\dot{I}_1 = -\dot{I}_2 \times 0.42 \Rightarrow \dot{I}_2 = \frac{\dot{I}_1}{0.42}$$




$$\dot{I}_1 = -\frac{V_2}{1.71} \times 0.42$$

$$\dot{I}_1 = -V_2 \times 0.25$$

$$V_2 = -\frac{\dot{I}_1}{0.25}$$

$$\gamma_{12} = \frac{\dot{I}_2}{V_2}$$

N

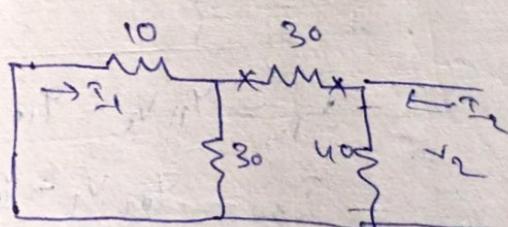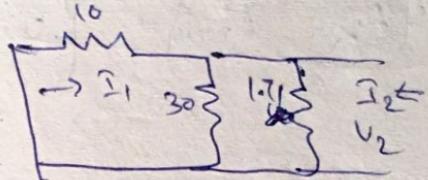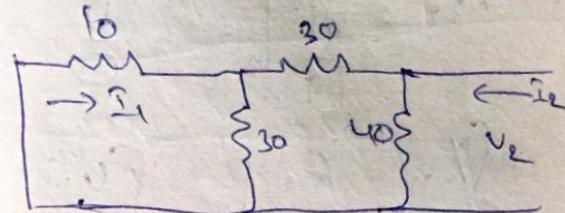

$$V_2 = -\frac{\dot{I}_1}{0.25}$$

Ans.

$$find \quad v_1 = h_{11} i_1 + h_{12} v_2$$

$$i_2 = h_{21} i_1 + h_{22} v_2$$

$$\begin{pmatrix} v_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} 1 & 2 \\ 1 & 2 \end{pmatrix} \begin{pmatrix} v_2 \\ i_1 \end{pmatrix}$$

$$v_1 = Z_{11} i_1 + Z_{12} i_2 \quad \rightarrow Z$$

$$v_2 = Z_{21} i_1 + Z_{22} i_2$$

$$Y \quad \begin{cases} i_1 = Y_{11} v_1 + Y_{12} v_2 \\ i_2 = Y_{21} v_1 + Y_{22} v_2 \end{cases} \quad Y$$


$$v_1 = A v_2 - B i_2 - A B C D$$

$$i_1 = C v_2 - D i_2$$

$$\begin{matrix} v_1 \\ i_2 \end{matrix} = \begin{matrix} h_{11} i_1 + h_{12} v_2 \\ h_{21} i_1 + h_{22} v_2 \end{matrix} \quad \rightarrow h$$

$$\sum x = \frac{1+2+5}{2}$$

S - T :-

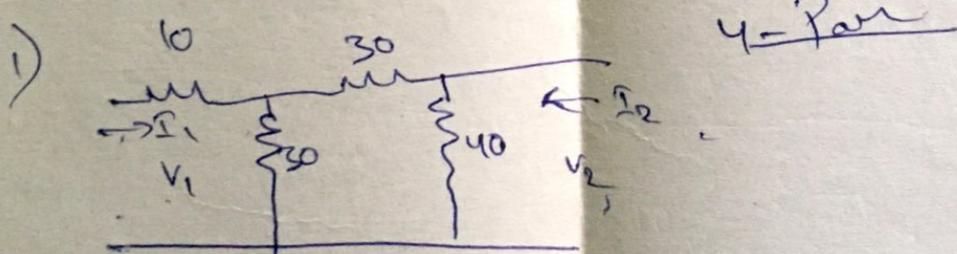

$$i_1 = Y_{11} v_1 + Y_{12} v_2$$

$$i_2 = Y_{21} v_1 + Y_{22} v_2$$

when  $v_2 = 0$

$$i_1 = Y_{11} v_1 \quad Y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0}$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$\therefore V_1 = I_1 \times R_{11}$

$V_1 = I_1 \times 25$



$$Y_{11} = \frac{V_1}{I_1 \times 25} = 0.04$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$-\frac{I_2}{V_1} = \frac{-I_1}{90} \times 20$$



$$= -\frac{2}{9}$$

Network shown in fig

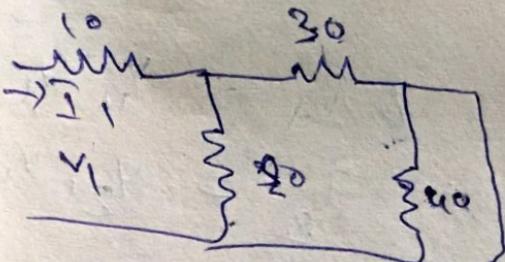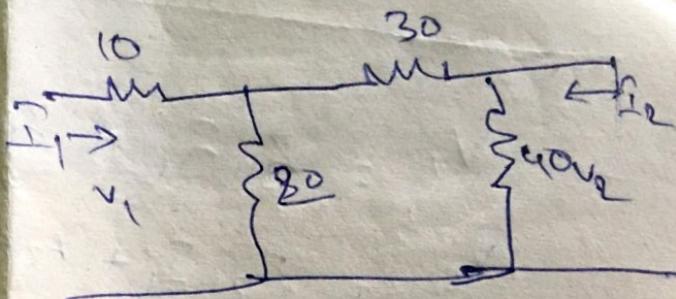



80 // 70

15.6

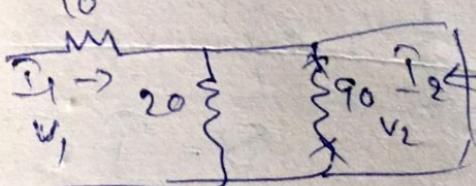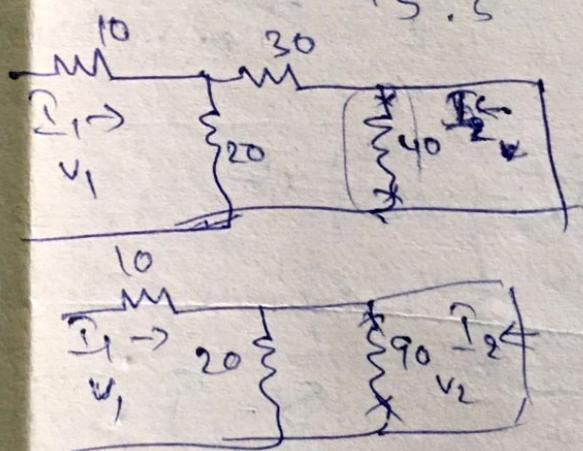

$$(D^2 + 4D + 3)y = e^t \sin x + x$$

~~equation~~

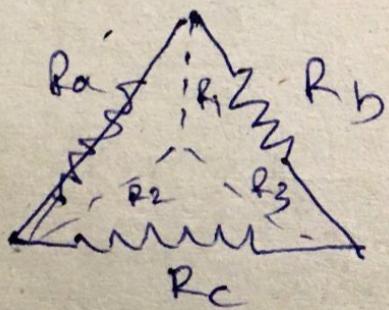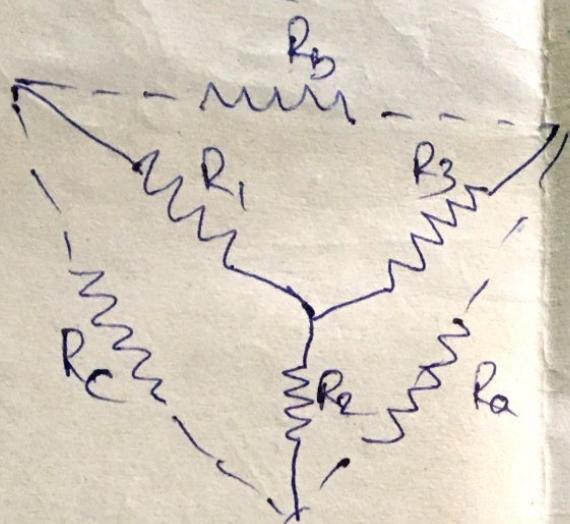


$$R_a = \frac{1}{R_1} (R_1 R_2 + R_2 R_3 + R_3 R_1)$$

$$R_b = \frac{1}{R_2} (R_1 R_2 + R_2 R_3 + R_3 R_1)$$

$$R_c = \frac{1}{R_3} (R_1 R_2 + R_2 R_3 + R_3 R_1)$$

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$
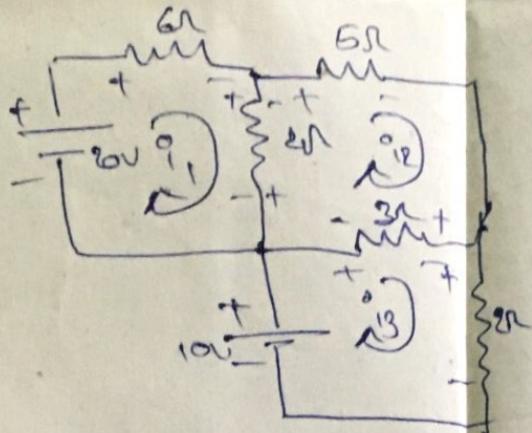
$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$



$$20 - 6i_1 - 4i_1 + 4i_2 = 0 \rightarrow ①$$

$$-4i_2 + 4i_1 - 5i_2 - 3i_2 + 3i_3 = 0 \rightarrow ②$$

$$10 - 3i_3 + 3i_2 - 2i_3 = 0 \rightarrow ③$$

$$10 = 10i_1 - 6i_2$$

$$-12i_2 + 4i_1 + 3i_3 = 0$$

$$10 = i_3 - 3i_2$$

$$\begin{bmatrix} 10 & -4 & 0 \\ 4 & -12 & 3 \\ 0 & -3 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 10 \end{bmatrix}$$

$$\Delta_1 = \begin{vmatrix} 10 & -4 & 0 \\ 4 & -12 & 3 \\ 0 & -3 & 1 \end{vmatrix} = -14$$

$$i_1 = \frac{\Delta_1}{\Delta} = 12.85$$

$$\Delta_2 = \begin{vmatrix} 20 & -4 & 0 \\ 0 & -12 & 3 \\ 10 & -3 & 1 \end{vmatrix} = -180$$




$$i_2 = \frac{\Delta_2}{\Delta} = 27.14$$

$$\Delta_3 = \begin{vmatrix} 10 & 20 & 0 \\ 4 & 0 & 3 \\ 0 & 10 & 1 \end{vmatrix} = -380$$






$$i_3 = \frac{\Delta_3}{\Delta} = 91.42$$

$$\Delta_3 = \begin{vmatrix} 10 & -4 & 20 \\ 4 & -12 & 0 \\ 0 & -3 & 10 \end{vmatrix} = -1280$$

~~10 = 10i\_1 - 6i\_2~~

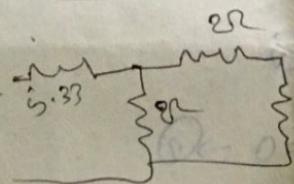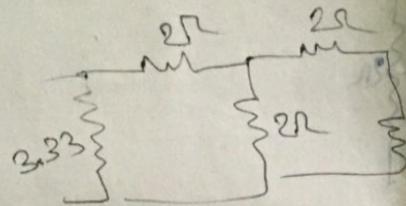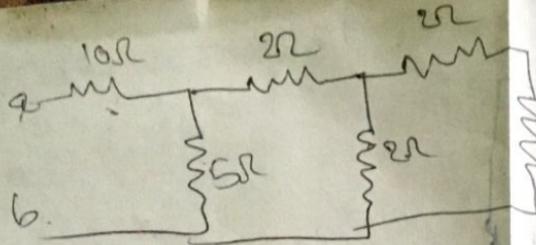

U

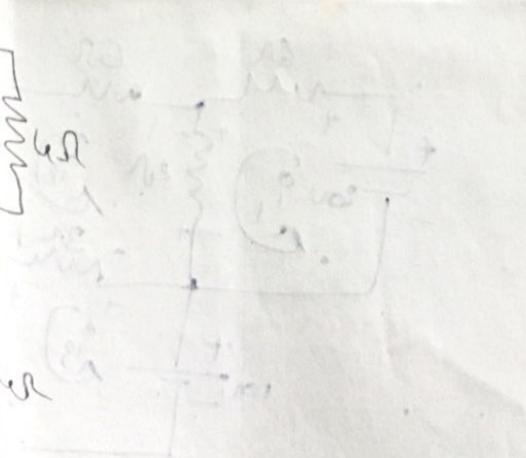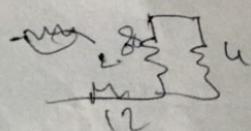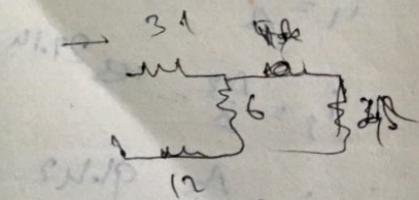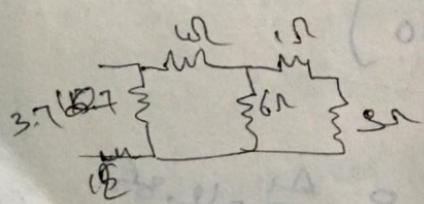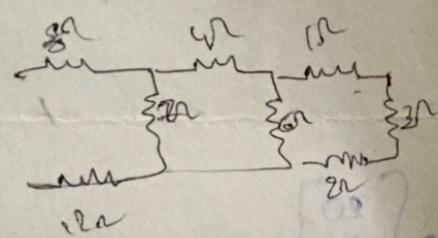


$$-0.5V + 0.1V - 0.1V = 0.0V$$

$$0.1V + 0.1V - 0.1V = 0.1V$$



$$0.1V + 0.1V - 0.1V = 0.1V$$

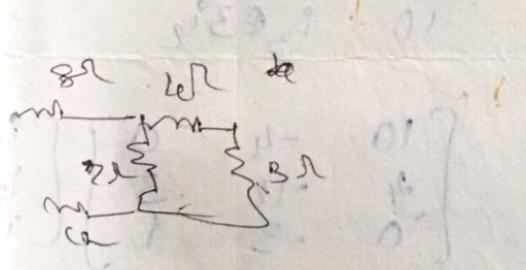


$$0.1V + 0.1V - 0.1V = 0.1V$$

$$\begin{aligned} & V_2 \\ & 2V_2 + 2V_2 = 2V_2 \end{aligned}$$

$$\begin{aligned} & 2V_2 + 2V_2 = 2V_2 \\ & 2V_2 + 2V_2 = 2V_2 \\ & 2V_2 + 2V_2 = 2V_2 \\ & 2V_2 + 2V_2 = 2V_2 \end{aligned}$$

$$\begin{aligned} & 2V_2 + 2V_2 = 2V_2 \\ & 2V_2 + 2V_2 = 2V_2 \\ & 2V_2 + 2V_2 = 2V_2 \end{aligned}$$

Given CR :-

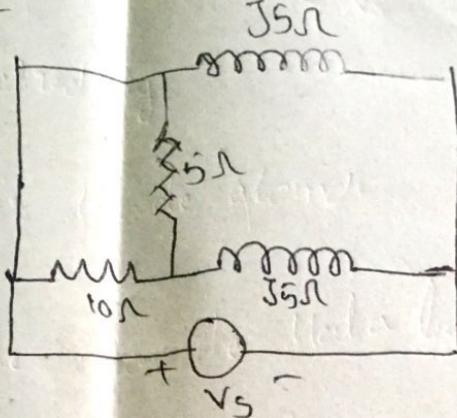

Given  $P = 100 \text{ watts}$  in  $5\Omega$  resistance

$$\therefore (\because P = VI)$$

$$P = I^2 \times R$$

$$100 = I^2 \times 5$$

$$\Rightarrow I^2 = \frac{100}{5} \Rightarrow I_5 = \sqrt{20} = 4.47 \text{ A}$$

$$\text{Now: } V = \frac{P}{I} = \frac{100}{4.47} = 22.3 \text{ V}$$

Power  $P = 100 \text{ watts}$  in  $10\Omega$  resistance

$$P = VI$$

$$P = I^2 \times R$$

$$\Rightarrow 100 = I^2 \times 10$$

$$I^2 = \frac{100}{10} = 10 \Rightarrow I_{10} = \sqrt{10} = 3.16 \text{ A}$$



$$I_{10} = 3.16 \text{ A}$$

$$\text{Now: } V = \frac{P}{I} = \frac{100}{3.16} = 31.62 \text{ V}, 41.84$$


$$\therefore \text{Voltage across } 35\Omega = (I_5 + I_{10}) 35$$

$$= (4.47 + 3.16) 35$$

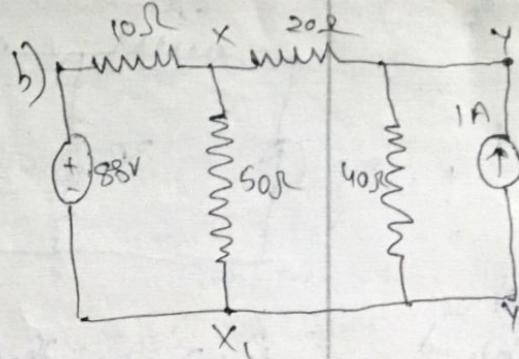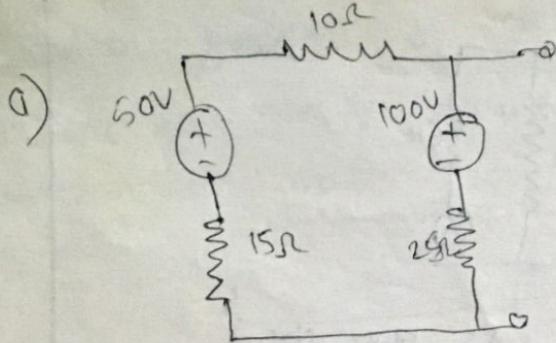
Find the Thevenin's Equivalent for Network shown in fig



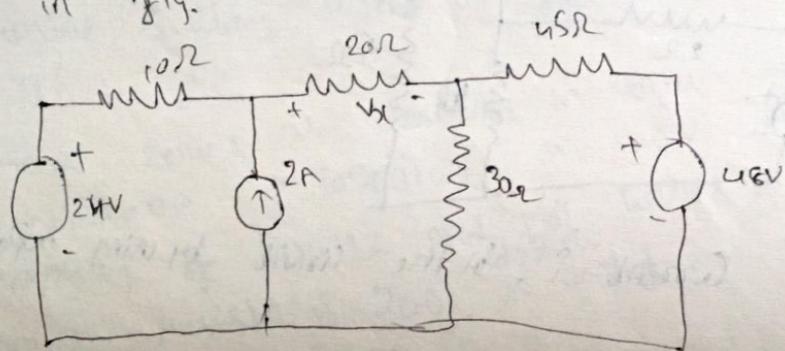- 2) By using Superposition Principle find the value of  $V_x$  as shown in fig.




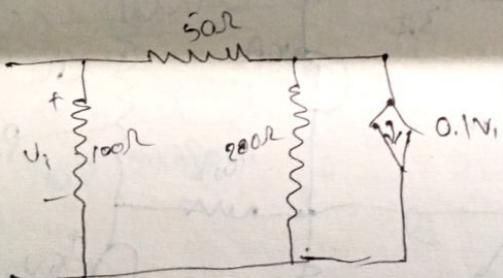- 3) Find the Norton's Equivalent for given circuit:



- 4) State and Derive Condition for the Maximum Power Condition Transfer Theorem

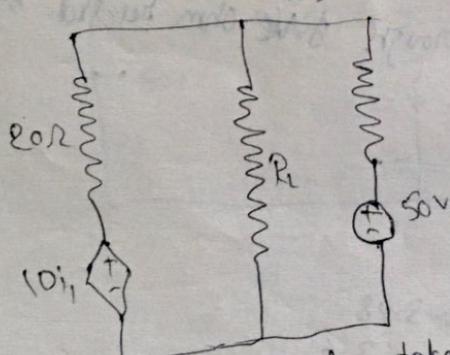
5) Determine value of  $R_L$  to which maximum power can be delivered




- 6) Using the Compensation th determine the ammeter reading where it is connected to the 6Ω resistor as shown in fig. The internal resistance of ammeter is 2Ω

NN Textbook  
Page 3.35


Ex - 3.13

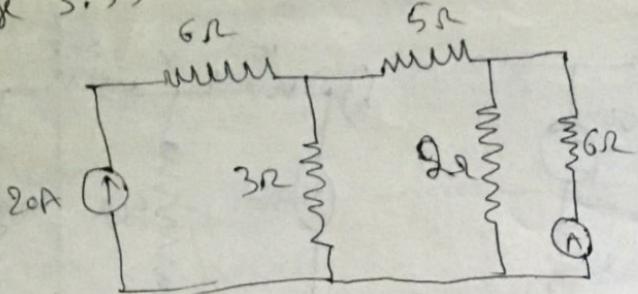

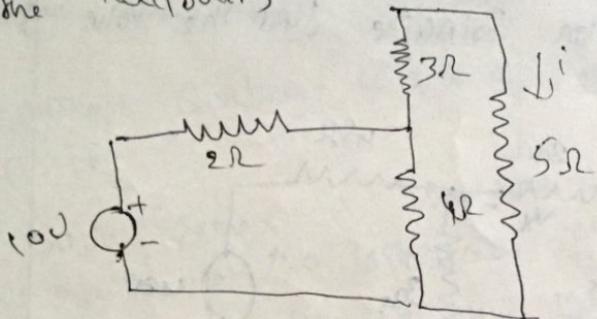(a) State and verify the Reciprocity Theorem for given circuit




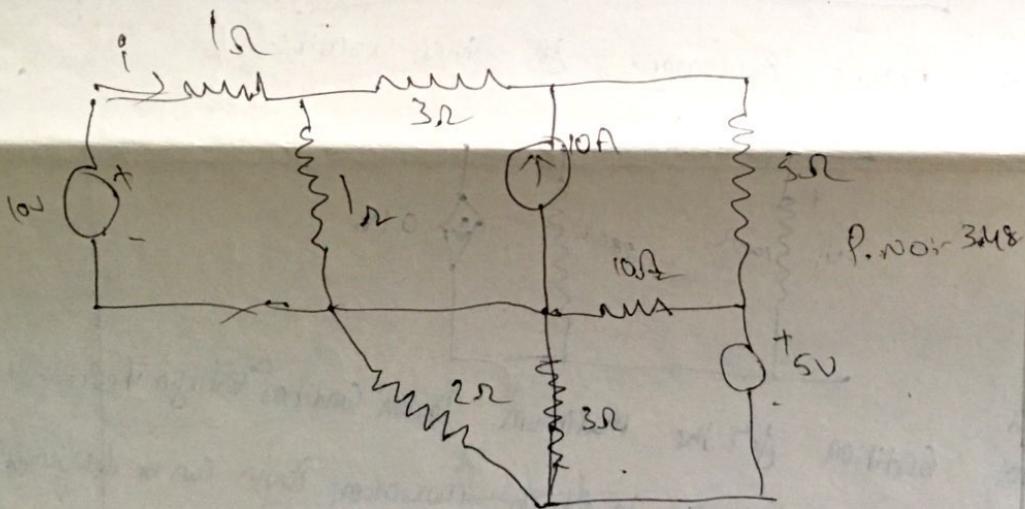(b) Determine the Current 'i' in the circuit by using Superposition theorem



(a) State and Explain the Maximum Theorem

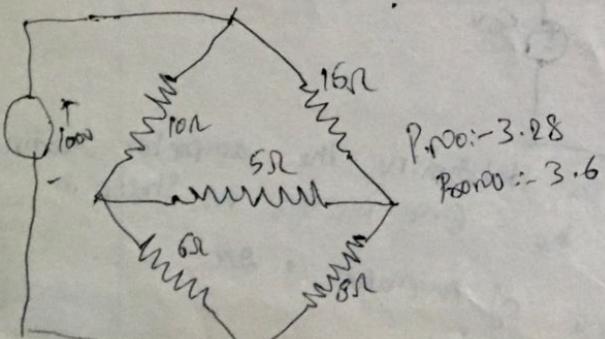(b) Find the current flowing through 5Ω ohm resistor by using Nodal Equivalent circuit




P<sub>max</sub> = 3.28

P<sub>min</sub> = 3.6

1) Define Resonance in an electrical circuit and determine the resonance frequency for an RLC Series Circuit

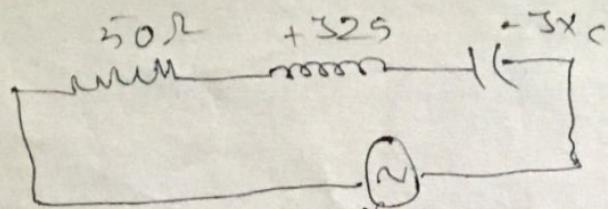2) Determine the values of capacitive reactance and impedance for given circuit



Prob: 8.22


Prob: Inv. No: 8.9

3) Ques: Define band width of RLC circuit and determine the equivalent approximate circuit parameters

4) Determine Quality circuit of coil consisting  $\gamma = 10\text{SL}$ ;  $L = 0.1\text{H}$  with resistor having

$$C = 10 \mu\text{F}$$

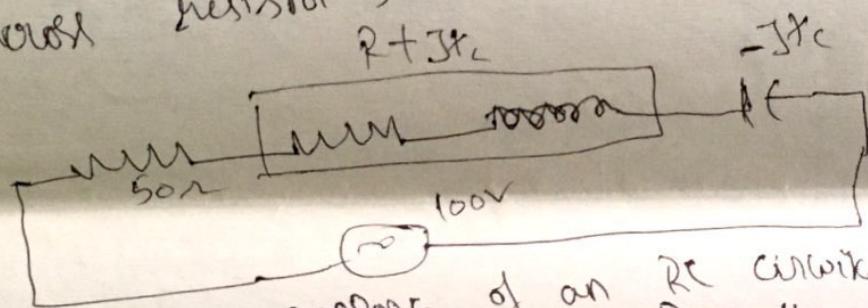5) A  $50\Omega$  series internal resistance is connected in parallel with a capacitor of  $200\text{Hz}$  and a current of  $0.7\text{Amp}$  and voltage across resistor is  $200$  with variable is constant



Step response of an RC circuit

16) Determine


17) "



18) "

a) for

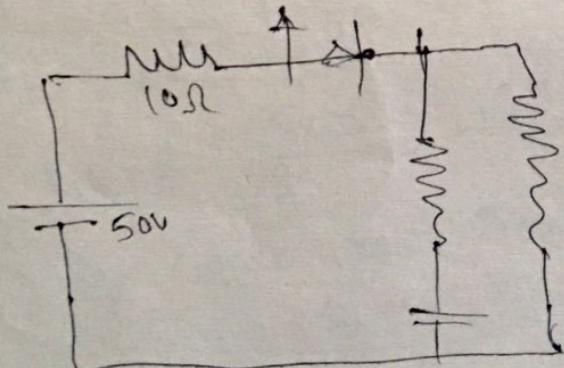b)  $t = 0$

Sigmoidal response " find current for when switch is opened



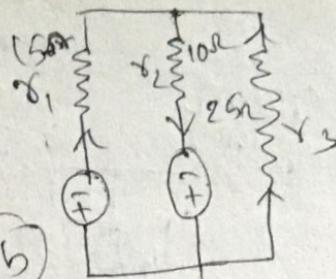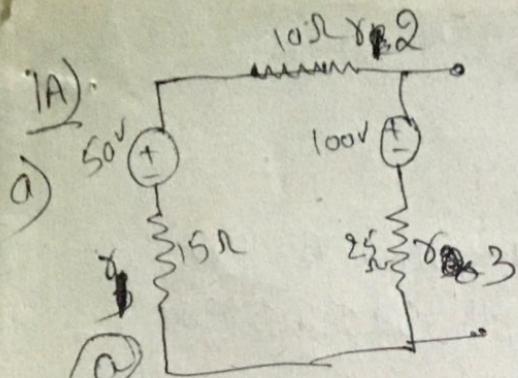


Let the resistance  $\gamma_3$  be removed and circuit exhibited in below circuit.

When no current  $I = 0$

At node application by KCL yields  
terminal 'X4'
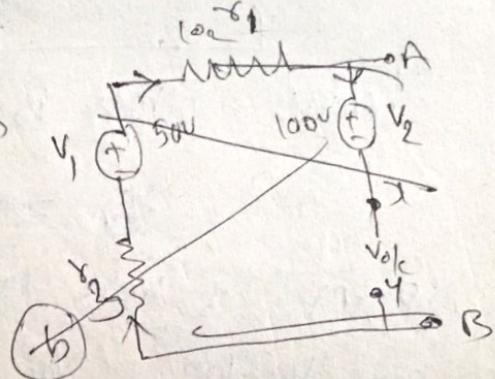
$$\text{Now: } \frac{V_1 - V_{oc}}{\gamma_1} + \frac{V_2 + V_{oc}}{\gamma_2} = 0$$



$$\therefore \frac{50 - V_{oc}}{15} + \frac{V_{oc} + 100}{10} = 0$$

$$3.3 - 0.06V_{oc} - 0.1V_{oc} - 10 = 0$$

$$-0.16V_{oc} = -7 = 0$$

$$-0.16V_{oc} = 7$$


$$V_{oc} = -\frac{7}{0.16} = 42 \text{ V}$$

$$\text{here: } \frac{1}{R_{th}} = \frac{1}{15} + \frac{1}{10}$$


$$R_{th} = \frac{15 \times 10}{25} = \frac{150}{25} = 6 \Omega$$

by Thevenin's eq circuit being shown in fig (c)
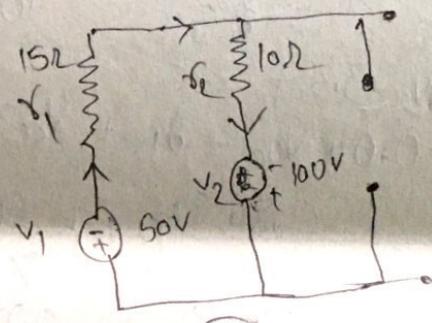
$$I_3 = I_{th} = \frac{V_{oc}}{R_{th} + \gamma_3} = \frac{42}{6 + 25} = 1.354 \text{ A}_{\parallel}$$



(2)

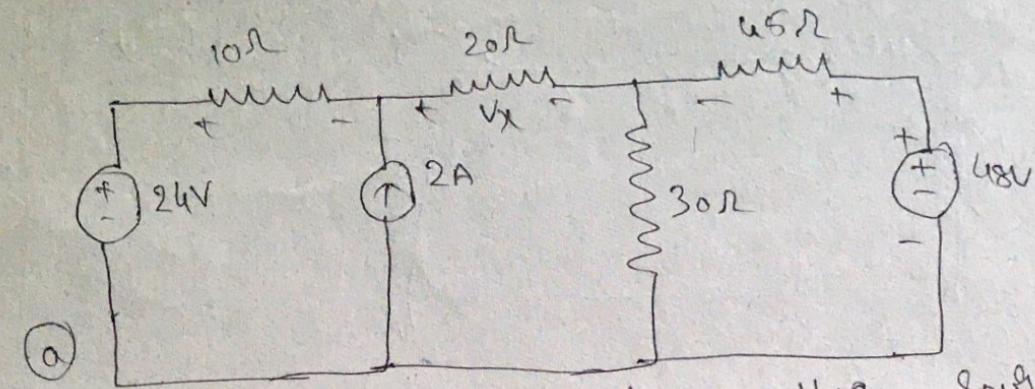


first we have to find out the voltage source

at  $20\Omega$  then

assuming Voltage 'Voc' at nodes 'A'

$$\text{Voc} = \frac{24}{10} + 2A$$

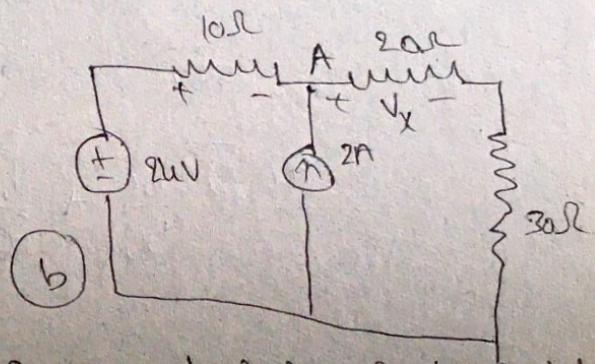

When the resistance of  $20\Omega$  and  $30\Omega$  are in series

so resistance is  $50\Omega$

$$\text{now: } \frac{\text{Voc} - 24}{10} + \frac{\text{Voc}}{50} = 2$$

$$0.1\text{Voc} - 2.4 + 0.02\text{Voc} = 2$$

$$0.12\text{Voc} = 2$$

$$\text{Voc} = \frac{2}{0.12} = 16.66 \approx 20\text{V}$$


The voltage across  $20\Omega$  is due to voltage source of 24V is

$$V_x = \frac{\text{Voc}}{50\Omega} \times 20 = \frac{20}{50} \times 20 = 8\text{V}$$

now we have to find out the voltage across  $20\Omega$  resistor

due to 48V source while other source are set equal to zero

The circuit is as follows

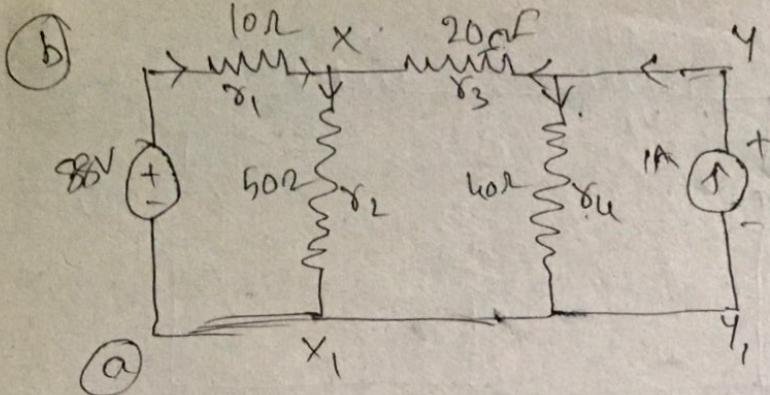

(2)

8V

Let the resistance  $\gamma_4$  be removed  
now applying KCL for AB terminals when  $I = 1$  another


Voltage  $V_{oc} = 88V$  Resistors  $\gamma_1 = 10\Omega$ ,  $\gamma_2 = 50\Omega$ ,  $\gamma_3 = 20\Omega$

$\gamma_3$  is in series with

$\gamma_1$ ,  $\gamma_2$  the two each other

$$\frac{V_{oc} - 88}{10} + \frac{V_{oc}}{50} + \frac{V_{oc}}{20} = 1$$
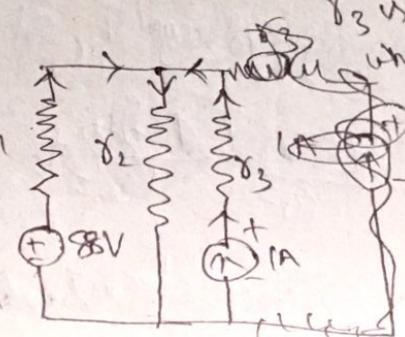
$$0.01 V_{oc} - 8.8 - 0.02 V_{oc} + 0.05 V_{oc} = 1$$



$$0.13 V_{oc} = 1 + 8.8$$

$$V_{oc} = \frac{9.8}{0.13} = 75.3 \text{ V}$$



$$\frac{1}{R_{Th}} = \frac{1}{10} + \frac{1}{50}$$

$$R_{Th} = \frac{10 \times 50}{60} = \frac{500}{60} = 8.33 \Omega$$


∴ By Thevenin Theorem the equivalent of

$$I_{Th} = \frac{V_{oc}}{R_{Th} + \gamma_4} = \frac{75.3}{8.33 + 40} = \frac{75}{8 + 40} = 1.56 \text{ A.}$$

$$I_{Th} = 1.56 \text{ A.}$$

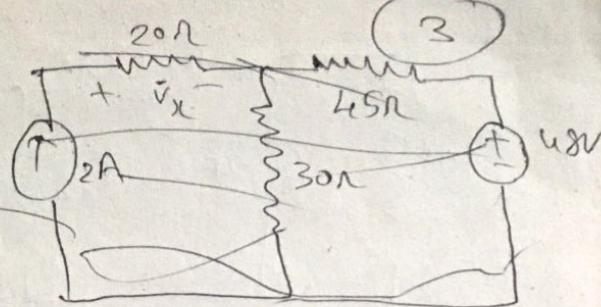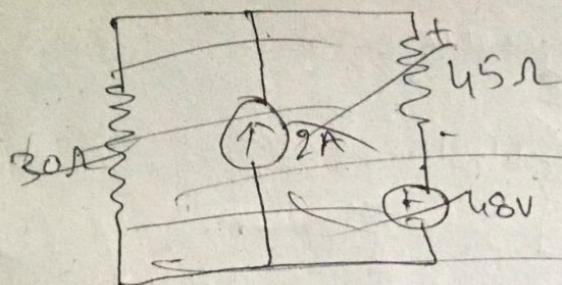

$$V_{ox} = ?$$

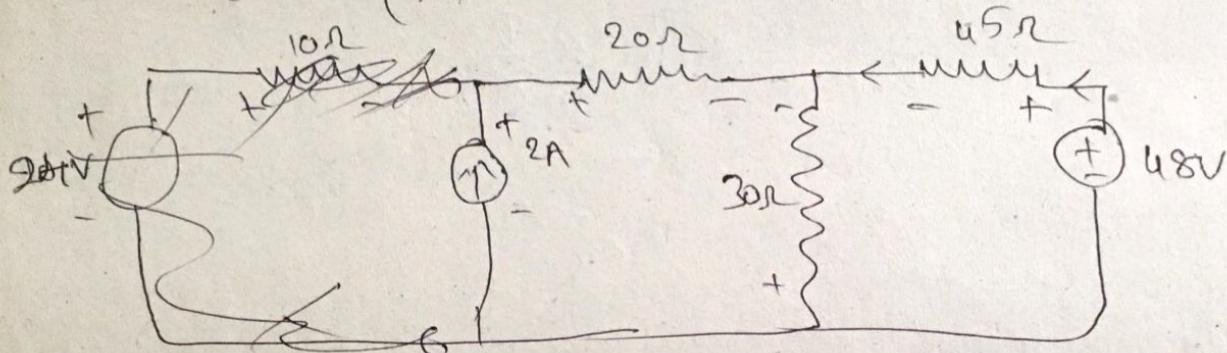

$$\frac{V_{oc}}{50} + \frac{V_{oc} + 48}{45} = 0$$

$$0.02 V_{oc} + 0.02 V_{oc} + 1.06 = 0$$

$$0.04 V_{oc} = -1.06$$


$$V_{oc} = -\frac{1.06}{0.04} = 26.6 \text{ V}$$

The voltage across 20Ω resistor due to the 48V source

$$V_{ox} = \left( \frac{V_{oc}}{50} \right) * \left( \frac{V_{oc} + 48}{45} \right) * 20$$

$$V_{ox} = \frac{26 + 48}{45} * 20 = 32.88 \text{ V}$$

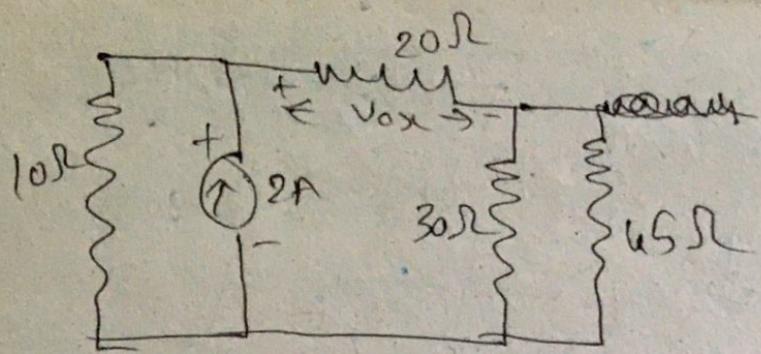Now we have to find out the voltage across 20Ω resistor due to '2A' current source while other source are set equal to zero. The circuit is



$$V = IR$$

$$I = \frac{V}{R}$$

The current through 20 ohm resistor =  $20 \times \left( \frac{30 \times 45}{30 + 45} \right)$

~~$I = R \frac{V}{C}$~~

$$\sum I =$$