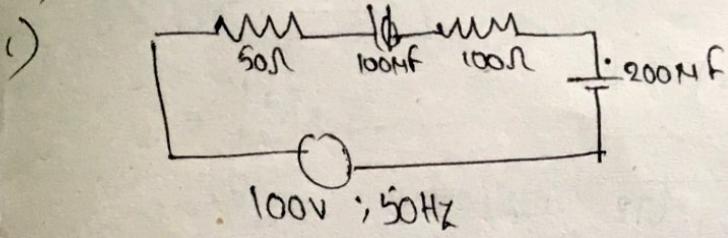


P) Practice Problem:-



$$V_s = 100V ; F = 50\text{Hz}$$

$$R = 150\Omega ; S.C = 300\text{mH}$$

$$\omega = 2\pi f = 2\pi \times 50 = \frac{100\pi}{628.318}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = -628.318 \times 300 \times 10^{-6} \\ = 0.18849.$$

$$Z = \left( R + j \frac{1}{\omega L} \right) = (R - j X_C) \\ = (150 - j 0.18849) \\ = \sqrt{(150)^2 - (0.18849)^2}$$


$$Z = 150.0$$

~~$$R = \frac{V_s}{Z} = \frac{100}{150} = \frac{100}{150}$$~~

$$\text{Phase angle } \theta = \tan^{-1} \left( \frac{-0.18849}{150} \right) = -0.071$$

$$I = \frac{V_s}{Z} = \frac{100}{150} = 1.510.071^\circ$$

P)

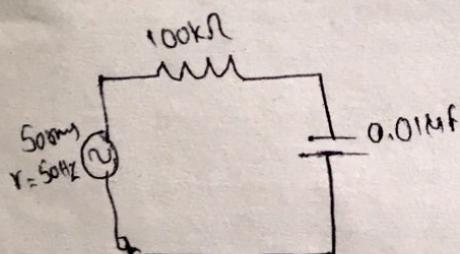


$$V = 50 ; F = 50\text{Hz} ; R = 100\text{k}\Omega \\ R = 100 \times 10^3 = 0.1$$

$$C = 0.01\text{mF} \\ = 0.01 \times 10^{-6} \\ = 1 \times 10^{-8} \\ = 3.16 \times 10^{-8}$$

$$X_C = \frac{1}{\omega C} = -j \omega C \\ = -2\pi f C = -2\pi \times 50 \times 1 \times 10^{-8} = -3.14 \times 10^{-6}$$

P)

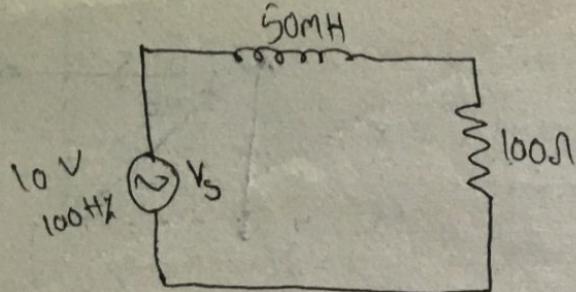

$$V_s = 10V ; F = 100\text{Hz} ; L = 50\text{mH} \quad R = 100\Omega$$

$$= 50 \times 10^{-3}$$

$$X_L = \omega L$$

$$= 2\pi f L = 2\pi \times 100 \times 50 \times 10^{-3}$$

$$= 31.415 \Omega$$

$$Z = (R + j\omega L)$$

$$= (100 + j31.415)$$

$$Z = \sqrt{(100)^2 + (31.415)^2}$$

$$Z = 104.818$$


$$\theta = \tan^{-1} \left( \frac{31.415}{100} \right) = 17.460$$

$$I = \frac{V_s}{Z} = \frac{10 \angle 0^\circ}{104.818 \angle 17.4^\circ} = 0.095 \angle -17.4^\circ$$

voltage across resistance  $V_R = I R$   
 $= 0.095 \times 100 = 9.5V$

voltage across inductor  $V_L = I X_L$   
 $= 0.095 \times 31.415 \angle 90^\circ = 2.997 \angle 90^\circ$

3)

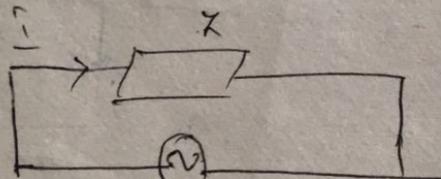


Given  $V_s = 30 + j50$  ;  $I = -5 + j15$

$$Z = \frac{V_s}{I} = \frac{30 + j50}{-5 + j15}$$

Q)

$$X_C = \frac{1}{2\pi f C}$$
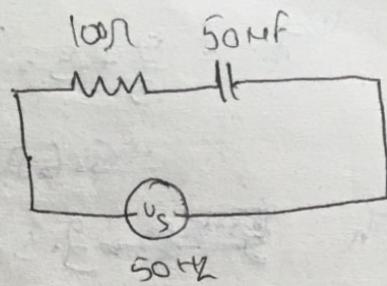
$$X_C = \frac{1}{2\pi \times 50 \times 10^{-6}} = 0.015 \Omega$$



$$Z = (R + jX_C)$$

$$= (100 - j \times 0.015)$$

$$= \sqrt{(100)^2 - (0.015)^2}$$



$$= 99.9$$

$$\theta = \tan^{-1} \left( \frac{0.015}{100} \right) = 0.085^\circ$$

$$I = \frac{V_s}{Z} = \frac{\sqrt{V_R^2 + V_C^2}}{Z}$$

$$\text{Voltage at Resistor: } V_R = I \times R$$

The answer:-

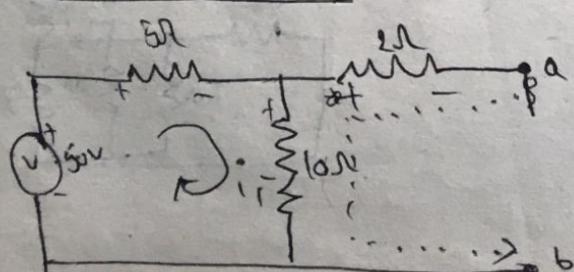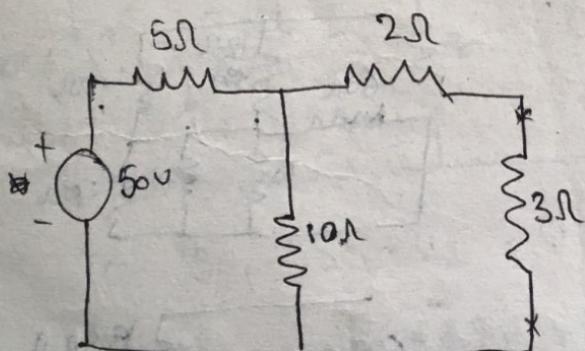

$$50 - 5i_1 - 10i_1 + 10i_2 = 0$$

$$50 - 15i_1 + 10i_2 = 0$$

$$50 = 15i_1 - 10i_2$$

$$i_1 = \frac{50}{15} = 3.33$$

$$i = 3.33$$

$$V_{th} = i \times 10$$

$$= 333 \times 10$$











$$= 33.3V$$

$$R_{th} = \frac{5 + 5}{3} = \frac{20}{3}$$

$$= 6.6\Omega$$

$$R_{th} = \cancel{5.3} + 2$$



$$= 5.33$$

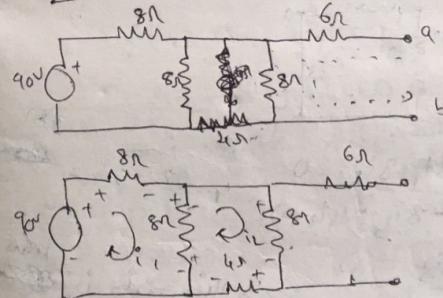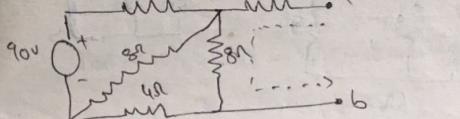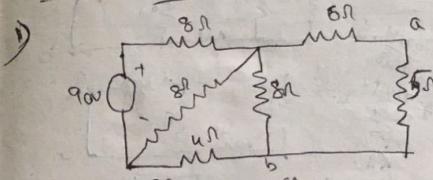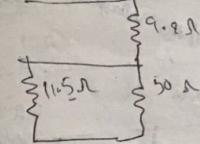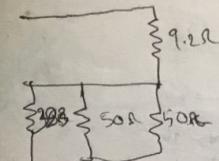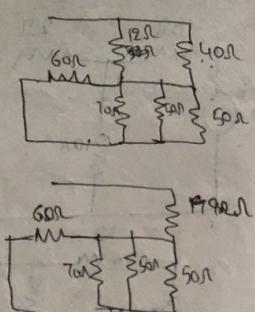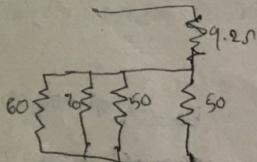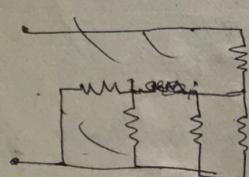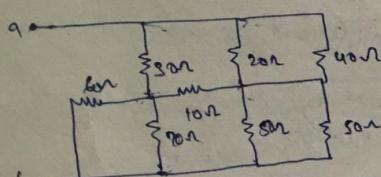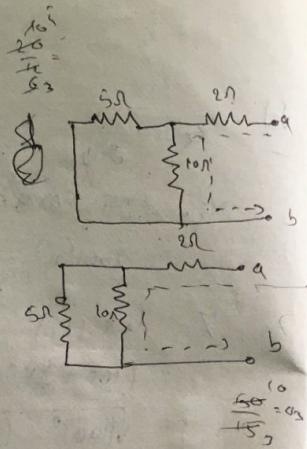

$$90 - 8i_1 - 8i_1 + 8i_2 = 0 \Rightarrow 90 = 16i_1 - 8i_2$$


$$-8i_2 - 4i_2 + 8i_2 + 8i_1 = 0 \Rightarrow -20i_2 + 8i_1 = 0$$
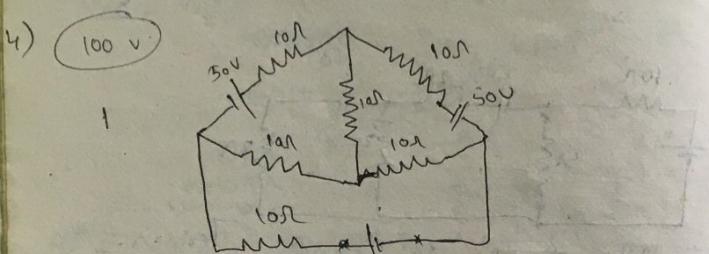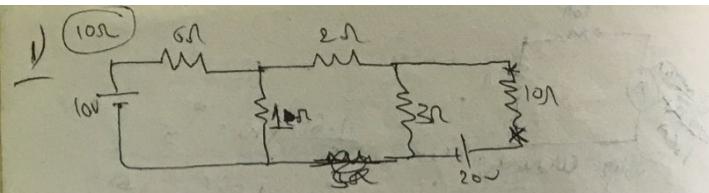
$$i_1 = -22.5 ; i_2 = \frac{-8i_1}{20} = \frac{180}{20} = 9V$$





Determined current supplied through 100V

5) Assume across 4Ω

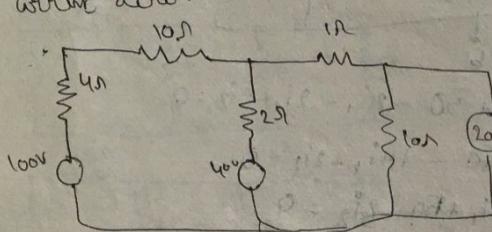


Nodding Th. - 1st 2nd Circuit:-

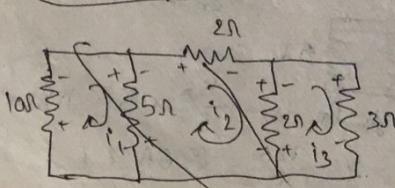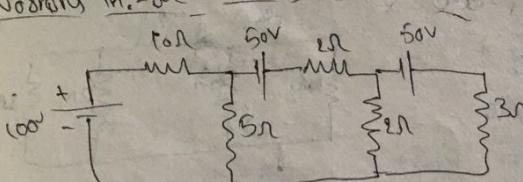

$$\begin{aligned} -10i_4 - 5i_1 + 5i_2 &= 0 \Rightarrow -15i_1 + 5i_2 = 10 \rightarrow @ \\ -2i_2 - 2i_1 + 2i_3 - 5i_2 + 5i_1 &= 0 \Rightarrow -9i_2 + 2i_3 = 0 \rightarrow (b) \\ -2i_3 + 2i_2 - 3i_3 &= 0 \Rightarrow -5i_3 + 2i_2 = 0 \rightarrow (c) \end{aligned}$$

~~Solving (b) and (c)~~
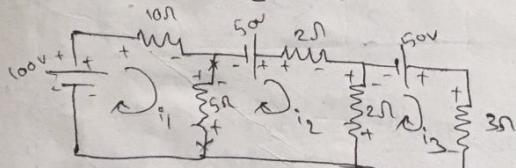
$$\begin{aligned} -2i_2 - 5i_3 &= 0 \\ -9i_2 + 2i_3 &= 0 \Rightarrow 2i_2 = 9i_3 \\ 2i_2 - 5i_3 &= 0 \Rightarrow 2i_2 = 5i_3 \end{aligned}$$



$$100 - 10i_1 - 5i_1 + 5i_2 = 0$$

$$-5i_2 + 5i_1 + 50 - 2i_2 - 2i_2 + 2i_3 = 0$$

$$-2i_3 + 2i_2 + 50 - 3i_3 = 0$$

$$100 - 15i_1 + 5i_2 = 0$$

$$\Rightarrow -9i_2 + 5i_1 + 2i_3 + 50 = 0$$

$$\Rightarrow -5i_3 + 2i_2 + 50 = 0$$

$$\Rightarrow -15i_1 + 5i_2 + 100 = 0 \rightarrow (@)$$

$$-9i_2 + 5i_1 + 2i_3 + 50 = 0 \rightarrow (b)$$

$$\Rightarrow -5i_3 + 2i_2 + 50 = 0$$

From @ and (b)

$$i_1 = -10.4; i_2 = -11.36 + 2i_3$$

$$i_2 = -10.4$$

$$-5i_3 + (-11.36 + 2i_3) + 50 = 0$$


$$-5i_3 - 22.6 + 4i_3 + 50 = 0$$

$$i_3 = 22.6 + 50 = 0$$

$$i_2 = -9.76$$



$$-6i_2 + 62i_1 - 60 = 0$$

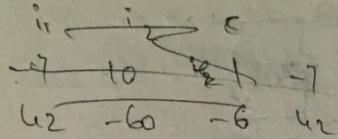

$$A = \begin{vmatrix} 1 & -7 & 0 \\ 1 & 1 & 0 \\ 0 & -6 & 3 \end{vmatrix} ; \quad D = \begin{bmatrix} -10 \\ 0 \\ +20 \end{bmatrix}$$

$$\Delta = |A| = -470$$

$$\Delta_1 = \begin{vmatrix} -10 & 1 & 0 \\ 0 & -5 & 3 \\ 20 & 3 & -13 \end{vmatrix} = -630$$


$$\Delta_2 = \begin{vmatrix} -7 & -10 & 0 \\ 1 & 0 & 3 \\ 0 & 20 & -13 \end{vmatrix} = 290$$

$$\Delta_3 = \begin{vmatrix} -7 & 1 & -10 \\ 1 & -6 & 0 \\ 0 & 3 & 20 \end{vmatrix} = 790$$


$$i_1 = \frac{\Delta_1}{\Delta} = \frac{-630}{-470} = 1.340 \text{ A}; \quad i_2 = \frac{\Delta_2}{\Delta} = \frac{290}{-470} = -0.61 \text{ A}$$

$$i_3 = \frac{\Delta_3}{\Delta} = 1.68 \text{ A}$$


7-chapter..

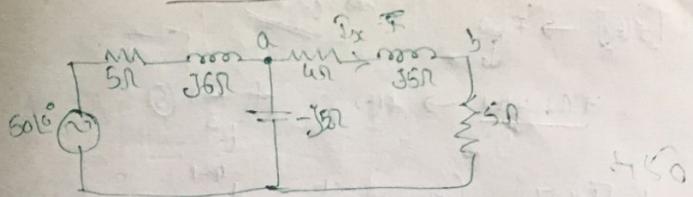

$$Z = 5 + j5 \text{ ohm node a and b}$$

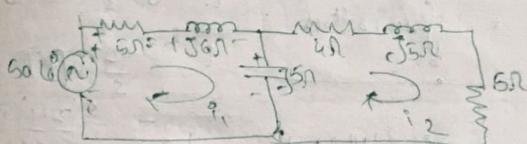
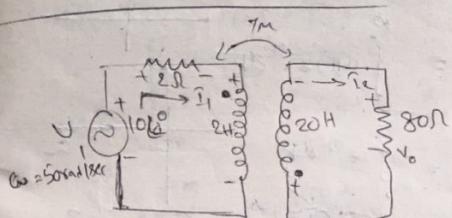
$$50\angle 0^\circ + j56i_1 - j56i_2 + j5i_3 -$$



$$10\angle 0^\circ - 2i_1 - 2 \frac{di_1}{dt} + 2 \frac{di_2}{dt} + 7 \cdot \frac{di_2}{dt} = 0$$

$$-20 \frac{d^2i_2}{dt^2} + 20 \frac{di_1}{dt} - 20i_2 + 7 \frac{di_1}{dt} = 0$$

$\Rightarrow$






$$[af(t)] = a \cdot L[f(t)] \quad [f(t) + g(t)] = L +$$

$$L \left[ \frac{d[f(t)]}{dt} \right]$$

1) h-Parameters


$$h_{11} = \left| \frac{V_1}{I_1} \right|_{V_2=0}$$

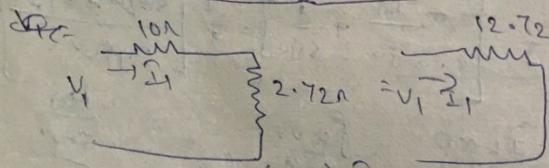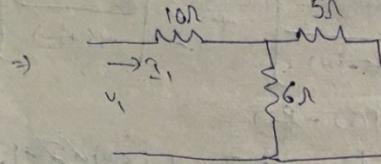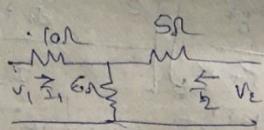

$$\left| \frac{V_1}{I_1} \right|_{V_2=0} = 12.72 \Omega$$

$$h_{11} = 12.72 \Omega$$


$$h_{21} = \left| \frac{V_2}{I_1} \right|_{V_2=0}$$

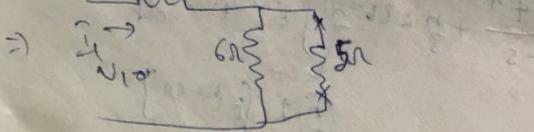

$$I_2 = \frac{-I_1}{(6+5)} \times 6$$

$$\Rightarrow \frac{I_2}{I_1} = -\frac{6}{11} = -0.545$$


$$h_{21} = \left| \frac{V_2}{I_1} \right|_{I_1=0}$$

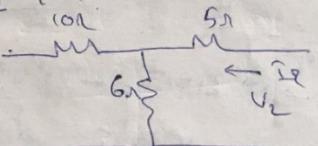

$$V_1 = 6I_2 \quad ; \quad V_2 = 11 \cdot I_2$$

$$\Rightarrow \frac{V_2}{I_1} = \frac{6}{11} = 0.545$$

$$h_{22} = \left| \frac{V_2}{I_2} \right|_{I_1=0}$$

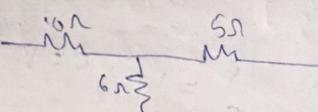


$$I_2 = \frac{V_2}{11} = \frac{V_2}{11} = \frac{1}{11} = 0.09 \cdot V$$

$$A = \left| \frac{V_1}{V_2} \right|_{I_2=0} = 0$$


$$V_1 = I_1 \times 6.5$$

$$V_2 = \frac{I_1}{2} \times 2 = I_1$$

$$A = \frac{I_1 \times 6.5}{I_1} = 6.5$$

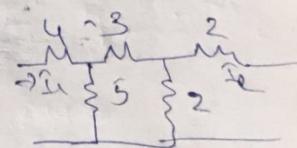

$$B = -\frac{V_1}{I_2} \Big|_{V_2=0}$$

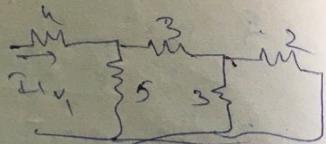

$$V_1 = 6.25 \times I_1$$

$$I_2 = -\frac{I_1}{9} \times \frac{5}{2}$$


$$\Rightarrow 22.5 I_1 + 22.5 I_2 = 0 \quad \text{or} \quad I_2 = -22.5 I_1$$

$$B = 22.5 \times 10$$

$$\frac{1}{C} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$V_2 = \frac{I_1}{2} \times 2$$



$$I_1 =$$

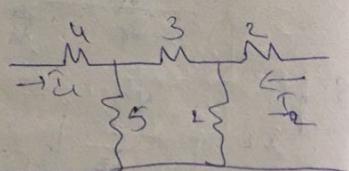


$$C = \frac{1}{I_1} \Rightarrow C = 1$$

$$-D = \frac{I_1}{I_2} \Big|_{V_2=0}$$

$$-D = \frac{I_1}{-8 \times 9/18}$$

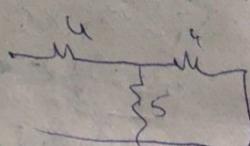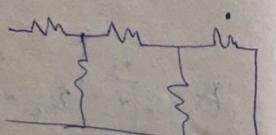


Set-1:-

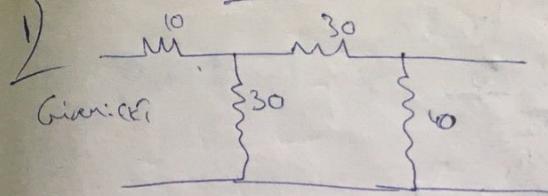

Y-parameter eq

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

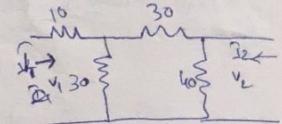


$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} ; Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} ; Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

when  $V_2 = 0$  then

$$V_1 = 25 \times I_1$$

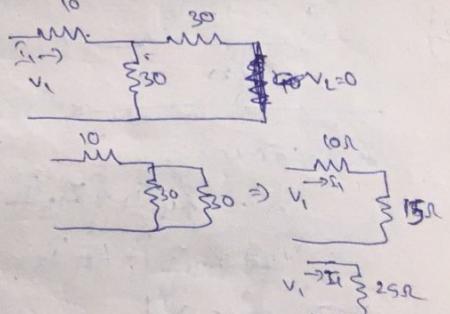

$$* \therefore Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{11} = \frac{X_1}{25 \times X_1}$$


$$Y_{11} = \frac{1}{25} = 0.04 \Omega$$

$$* Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$I_2 = 10 \times \frac{V_1}{30+40} = \frac{V_1}{70}$$

$$I_2 = 10 \times 0.05 \times \frac{V_1}{60} = \frac{V_1}{120}$$

$$Y_{21} =$$

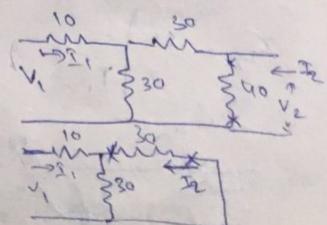


$$Y_{21} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

$$-I_2 = \frac{I_1 \times 30}{30+30}$$

$$-I_2 = \frac{130 \times I_1}{60} = \frac{I_1}{2}$$

$$I_1 = -2I_2$$

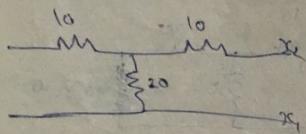


Z parameters:-

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad ; \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad ; \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

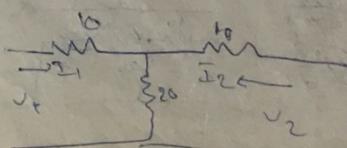

when  $V_2 = 0$  then

$$V_1 = 16.6 \times I_1$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{11} = \frac{16 \times I_1}{I_1} = 16 \Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = 36 \Omega$$

$$V_2 = 6.66 \times I_1$$

$$Z_{21} = \frac{36 \times I_1}{I_1} = 36 \Omega$$

$$I_2 = -\frac{I_1}{(20+10)} \times 20$$

$$I_2 = -I_1 \times 0.66$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{0.66 \times 0.66}{I_1} = +6.66 \Omega \quad \checkmark$$

when  $I_1 = 0$  then

$$A_{21} = \frac{V_1}{I_2} \Big|_{I_1=0} = 0$$

$$V_2 = I_2 \times 20$$


$$V_2 = I_2 \times 36$$

$$I_2 = \frac{V_2}{36}$$

$$\text{now } Z_{12} = \frac{V_1}{V_2} = \frac{V_1}{36} = \frac{16.6}{36} = \frac{1}{2}$$

$$Z_{12} = 1 \Omega$$


$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

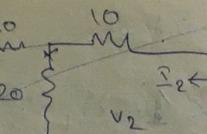

$$\therefore V_2 = \frac{1}{2} \times 30$$

$$Z_{22} = \frac{X_2 \times 30}{R_L} = 30\Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

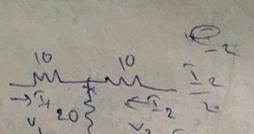


$$\text{As } V_1 = \frac{I_2 \times 10}{20}$$

$$V_1 = I_2 \times 0.2$$

$$Z_{12} = \frac{X_2 \times 0.2}{R_L} = 0.2\Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

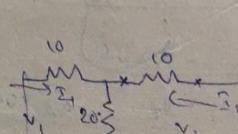


$$V_2 = \frac{I_2 \times 10}{20}$$

$$Z_{12} = \frac{X_2 \times 10}{R_L} = 10\Omega$$

$$\therefore Z_{11} = 16\Omega ; Z_{22} = 6.66\Omega ; Z_{12} = 0.2\Omega$$

$$Z_{22} = 10\Omega$$
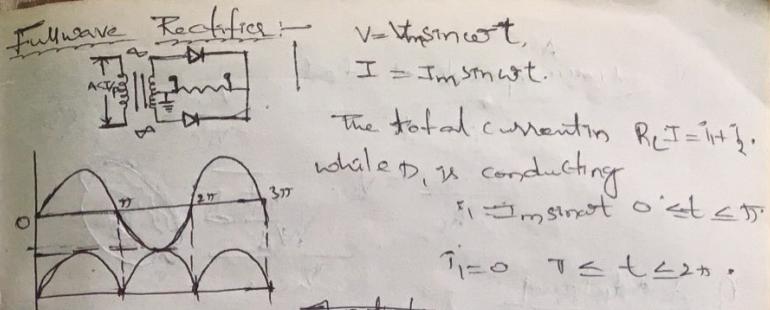
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 16 & 0.2 \\ 6.6 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



In the -ve half cycle  $D_2$  is conducting but  $D_1$  is not conducting.

$$I_2 = 0 \quad 0 \leq t \leq \pi$$

$$I_2 = I_m \sin \omega t \quad \pi \leq t \leq 2\pi$$

$$I_{avg} = I_{dc} = \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t \frac{I_m}{2\pi} (\cos \omega t) d\omega t$$

$$= \frac{I_m}{2\pi} [(-1) - (-1)] = \frac{2I_m}{\pi}$$

$$V_{av} = I_{dc} R_L = \frac{2I_m}{\pi} \times R_L = \frac{2V_m}{\pi}$$

$$I_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} I^2 \sin^2 \omega t d\omega t}$$

$$= \sqrt{\frac{I^2}{2\pi}} \left[ 1 - \cos \omega t \right]$$

$$= \sqrt{\frac{I^2}{2\pi} \left[ (\omega t)_0 - \frac{(\cos \omega t)_0}{2} \right]}$$

$$= \sqrt{\frac{I^2}{2\pi} [\pi - 0]} = \sqrt{\frac{I^2}{2\pi} \times \pi} = \frac{I}{\sqrt{2}}$$

$$V_{rms} = \frac{I_m}{\sqrt{2}} R_L = \frac{V_m}{\sqrt{2}}$$

$$V_{rms}^2 = V_{av}^2 - V_{dc}^2 = \frac{V_m^2}{2} - \frac{4V_m^2}{\pi^2}$$

$$= \frac{(\pi^2 - 8)V_m^2}{\pi^2}$$

$$\Rightarrow V_{rms} = (0.0947) V_m$$

$$\eta = \frac{\text{AC Components of output}}{\text{DC components.}} = \frac{V_{\text{rms}}}{V_{\text{dc}}} \quad \text{ve ni phter Ro}$$

$$= \frac{I_{\text{rms}}}{I_{\text{dc}}} = V_{\text{dc}} \sqrt{\frac{V_{\text{rms}}^2 - 1}{V_{\text{dc}}^2}}$$

$$\eta = \frac{\text{dc output power}}{\text{AC input power}} = \frac{V_{\text{dc}}}{V_{\text{rms}}} \cdot$$

$$= \sqrt{\frac{V_{\text{dc}}^2 \cdot \pi^2}{2 \cdot 4 \cdot V_{\text{rms}}^2}} - 1$$

$$= 0.6834 //$$

If diode forward resistance and transformer resistance included then

$$P_{\text{ac}} = \frac{V_{\text{dc}}^2}{V_{\text{rms}}^2 / R_C + R_f} = V_{\text{dc}}^2 \left( \frac{1 + \frac{R_f + R_s}{R_L}}{V_{\text{rms}}^2} \right) = 0.81$$

$$P_{\text{dc}} = \frac{V_{\text{dc}}^2 / R_C}{V_{\text{rms}}^2 / R_C + R_f}$$

\* Maximum efficiency %.

$$\eta = 0.81056$$

max % efficiency  $\approx 81.056\%$

PIV :- ~~for tve cycle, D1 is forward biased and D2 is reverse bias, at that time, the diode is withstand without destroying the junction for maximum reverse voltage  $V_m$ .~~

1/2 for tve cycle, D1 is reverse bias and D2 is forward bias, at that time, the diode is withstand without damaging the junction for tve cycle, maximum reverse voltage  $V_m$


$$\therefore \text{Total} = V_m + V_m = 2V_m$$

# Network Analysis:-

$$\text{Voltage: } V = IR \quad i = \frac{Q}{t}$$

$$\text{Power: } P = VI$$

## Circuit elements:

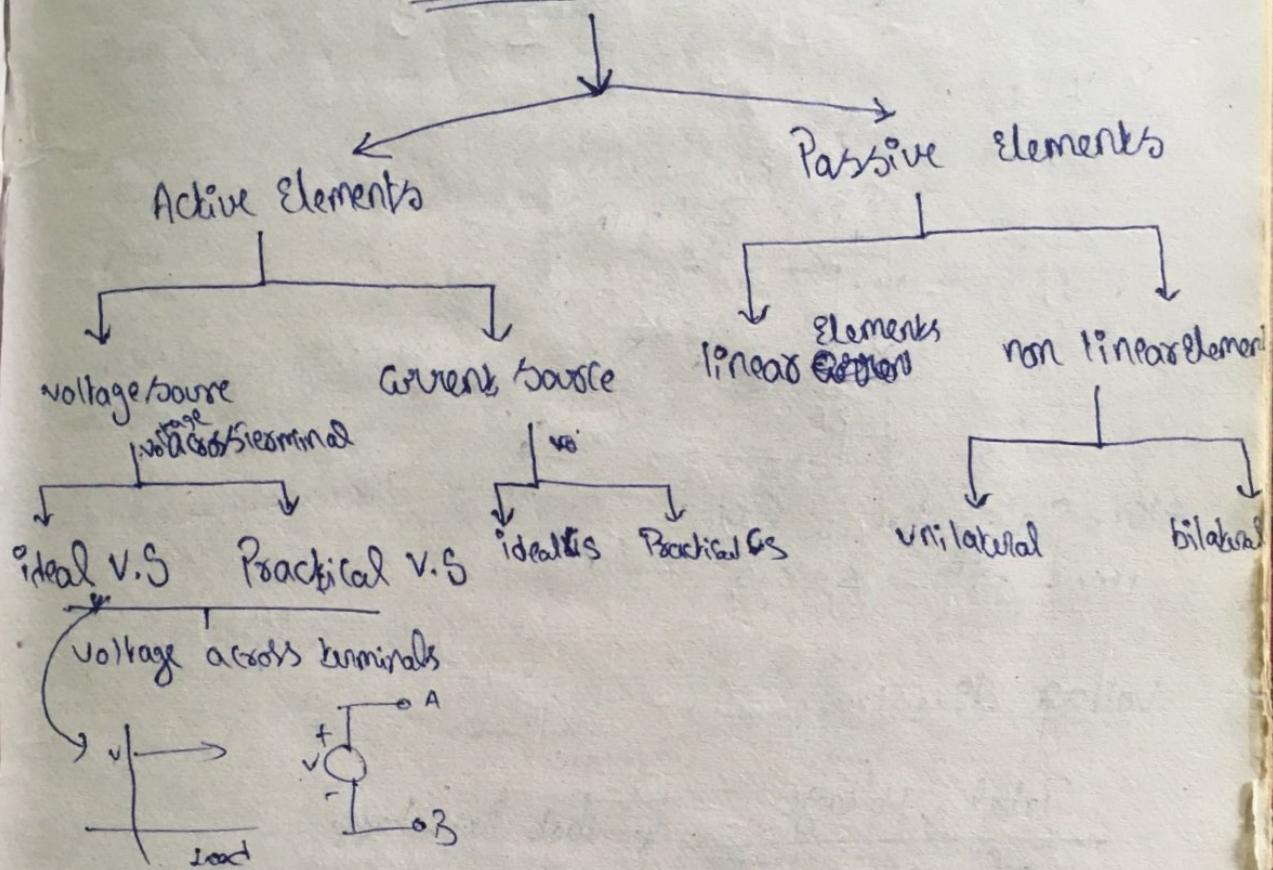

## Resistance:-

$$i = \frac{V}{R}$$

$$\therefore \frac{V}{R}$$

$$\therefore V = R \cdot \frac{di}{dt} \quad \text{units: ohms} \Omega$$

$$\left( \because i = \frac{dq}{dt} \right)$$

## Inductance:-

$$V = L \frac{di}{dt}$$

$$\therefore di = \frac{1}{L} V dt$$

Integrating B.S

unit:- Henry

$$\int_0^t di = \int_0^t \frac{1}{L} \cdot V dt$$

### Capacitance:-


$$C = \frac{Q}{V} \quad (\text{A}) \quad C = \frac{q}{v}$$

units - farads.

$$i = C \frac{dv}{dt}$$

$$dv = \frac{1}{C} \cdot i \cdot dt$$

### KVL:-

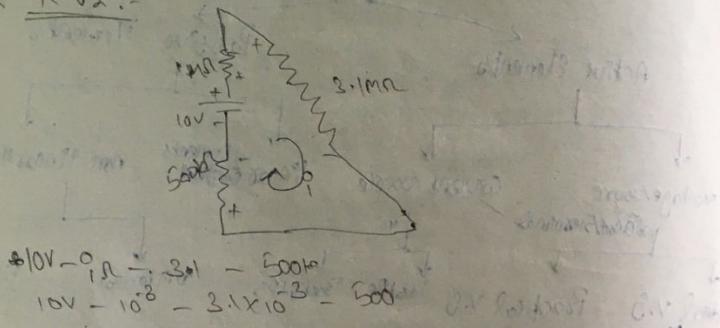

### Voltage division:-

$$\frac{\text{Total Voltage}}{\text{Sum of Resistances}} \times \text{That Resistance}$$

### Current division:-

$$\frac{\text{Total Current}}{\text{Sum of Resistances}} \times \text{The opposite resistance.}$$

### Power Resistance:-


$$P = iV$$

### Ideal voltage & Current sources:-

Independent Sources  
Voltage Source  
Current Source.





### Dependent sources:-

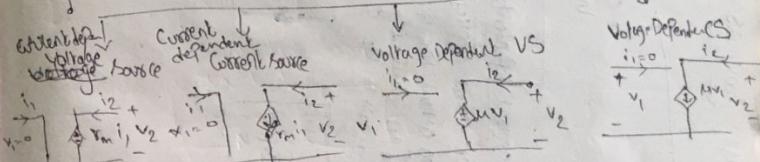

### Independent Sources:-
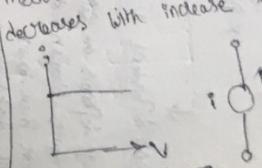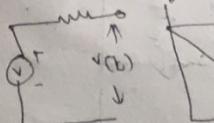
#### (i) Independent V.S

- Maintains constant voltage no charges occurs which gives constant current
- Independent current through source should have zero internal resistance that does not change when changes takes place in net work
- In practical independent VS have some internal resistance due to which voltage decrease with increase in current & it has infinite internal resistance
- In practical independent CS have some internal resistance due to which current decreases with increase in voltage.



## Dependent Voltage Sources:-

Dependent voltage source  
\* Depends on current through branches

Current dependent V.S  
\* Voltage depends on current  
through some branch of electrical  
network. This source is called  
current dependent V.S.

## Voltage dependent V.S




\* If voltage " " on voltage  
across some branch of electric net.  
then source is said to be voltage  
dependent voltage source.








Dependent Current source  
\* Current supplied by a source depends upon  
through some branches

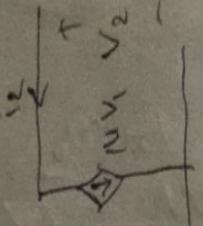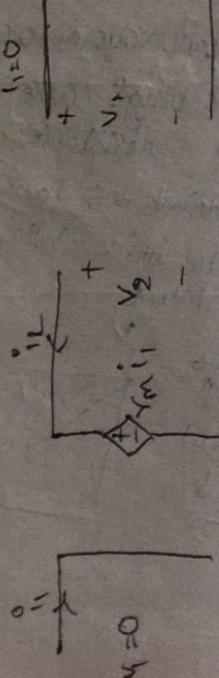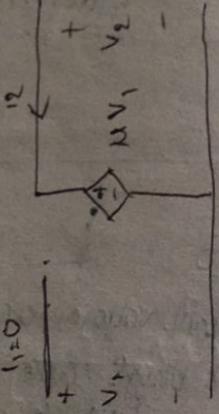
## Current dependent C.S

If current supplied by some  
branch depends on current through  
some branch of an electrical net  
then source is said to be current  
dependent C.S


Voltage dependent C.S  
If current supplied by some  
branch depends on voltage across  
some branch of an electrical net  
then source is said to be V.D.S




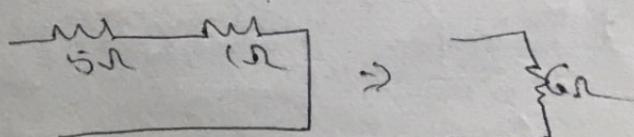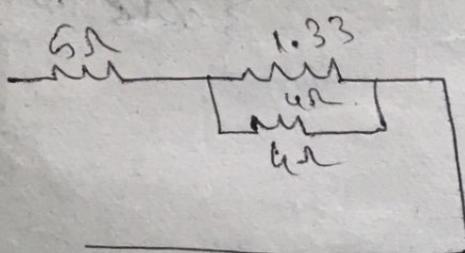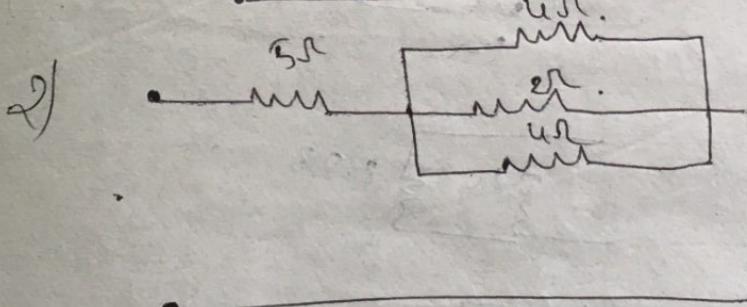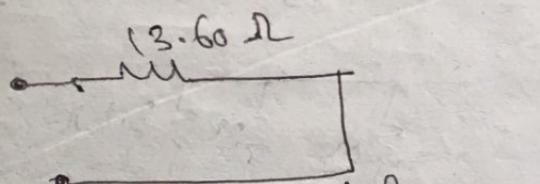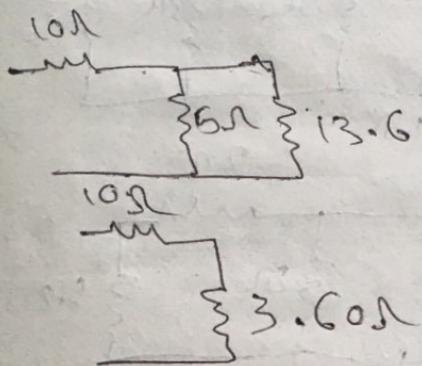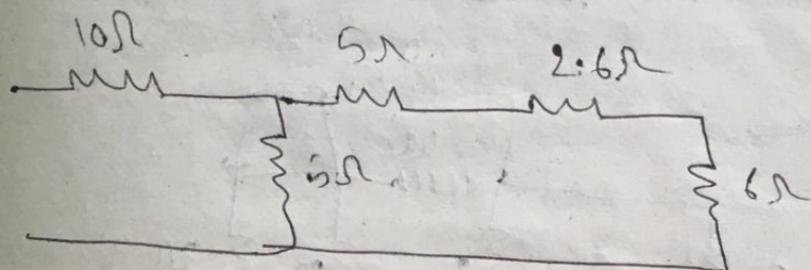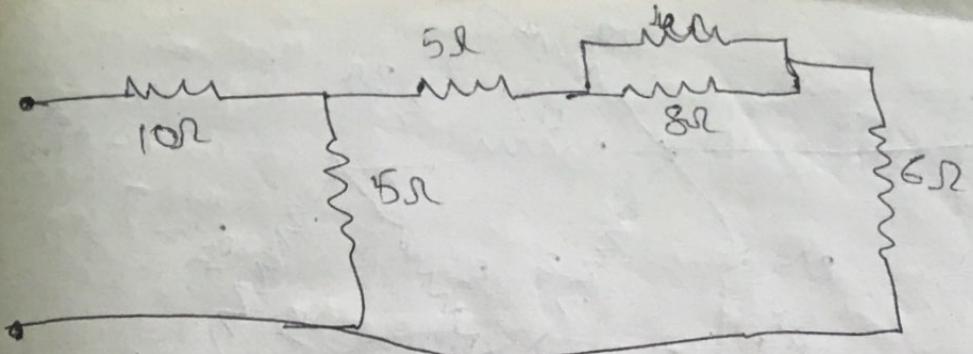

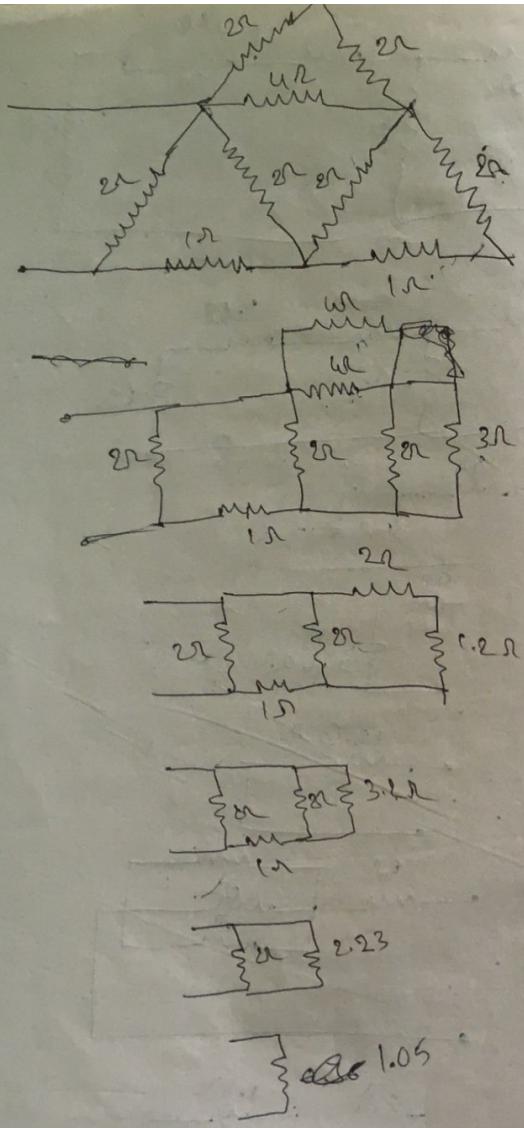

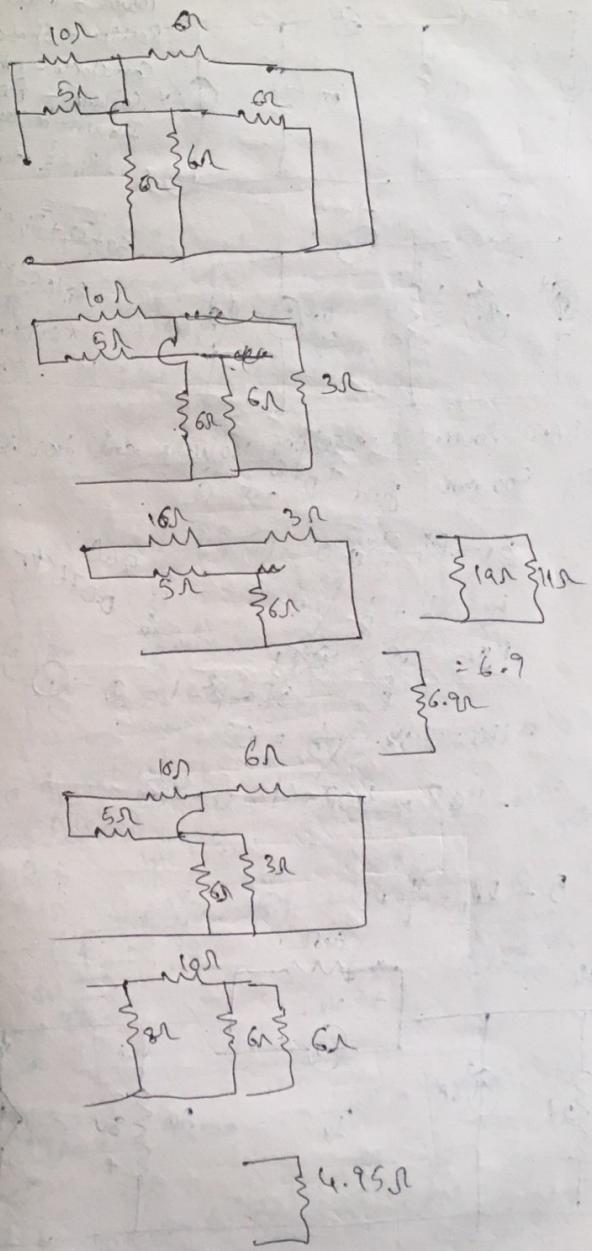
$$\frac{3\Omega}{7\Omega} = \frac{1}{7}$$





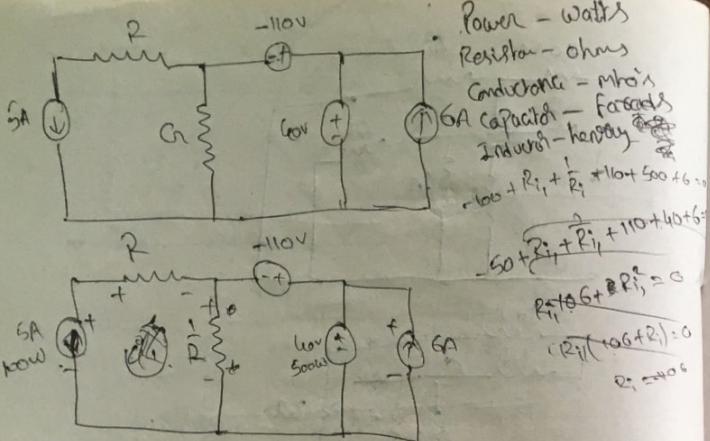


The 5Amp. source is supplying 100Watts and 110V battey supplying 500Watts find 'R' and 'G'
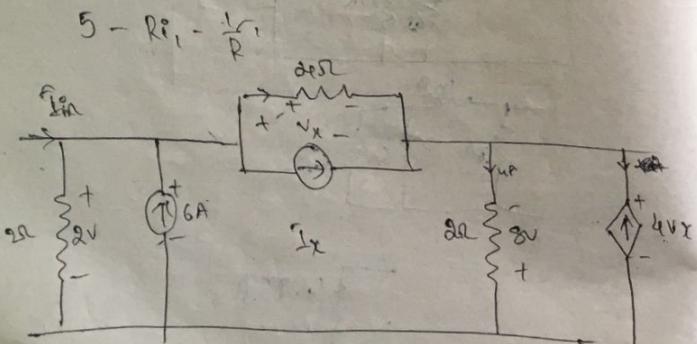
$$\begin{aligned}
 5 - R_i - \frac{1}{R} &= 0 \rightarrow ① \\
 5 &= R + \frac{1}{R} \\
 R_i &= \frac{1}{R} \\
 5R - R^2 - 1 &= 0 \rightarrow ① \\
 -110 - 40R - \frac{1}{R} &= 0 \\
 -110R - 40R - 1 &= 0 \rightarrow ②
 \end{aligned}$$


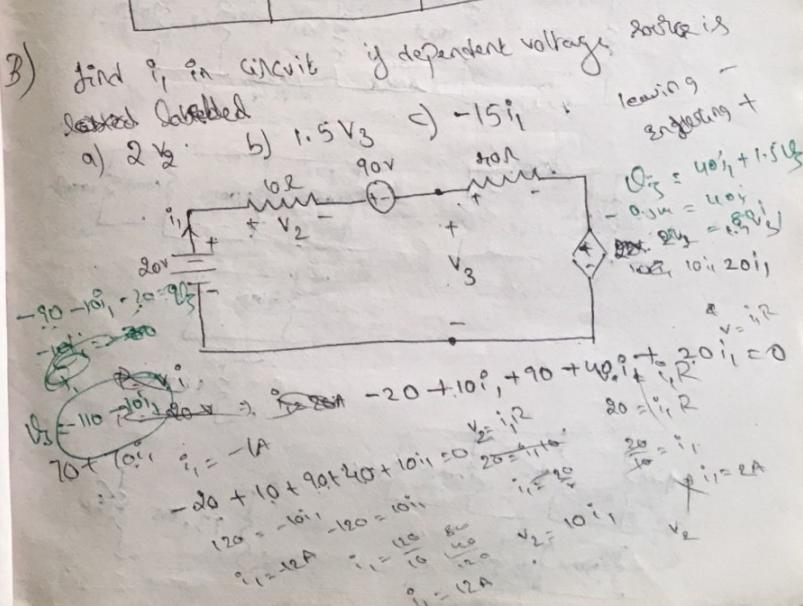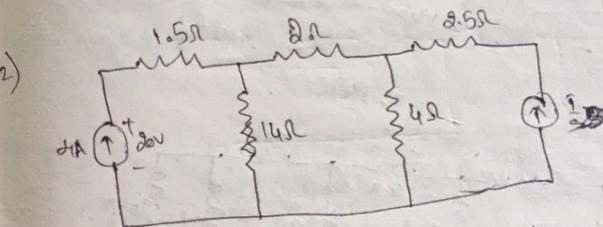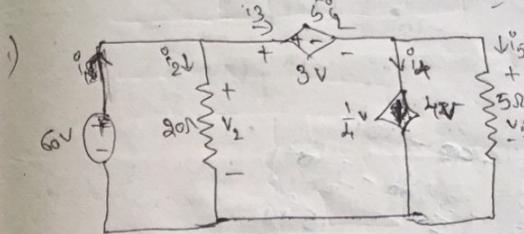
$$\begin{aligned}
 P &= V^2 \\
 P &= V \cdot I \\
 P &= V^2 / R \\
 P &= V^2 / R
 \end{aligned}$$





$i_1 = -12A$


$v_2 = 11^{\circ} R$ 
 $\Rightarrow v_2 = -12V$

$i_1 = -12A$ 
 $-90^\circ - 10^\circ + 20^\circ = 60^\circ$ 
 $-70^\circ = 10^\circ$ 
 $i_1 = -7A$


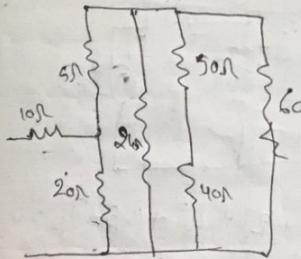
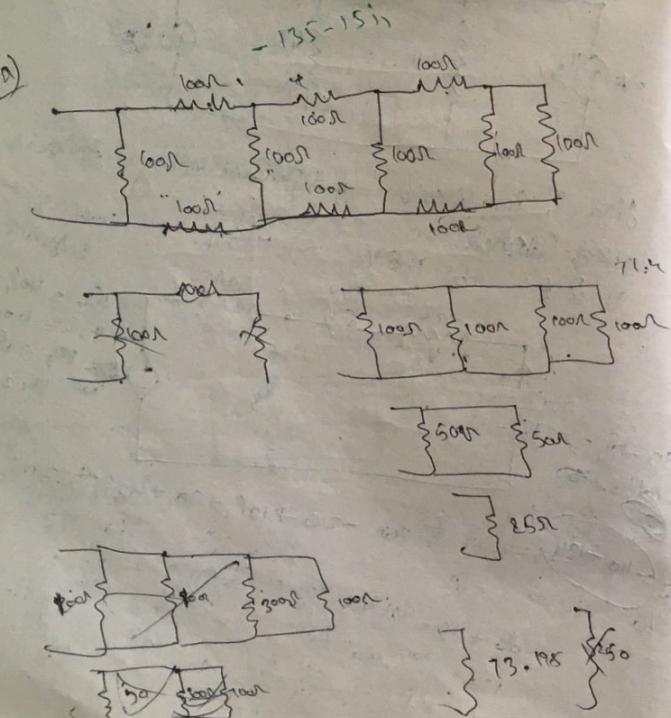
$v_3 = -90^\circ - 10^\circ$ 
 $1.5 v_3 = -\frac{3}{2} \times 20^\circ - 3 \times 10^\circ$ 
 $= -135^\circ - 15^\circ$




3) 18.28

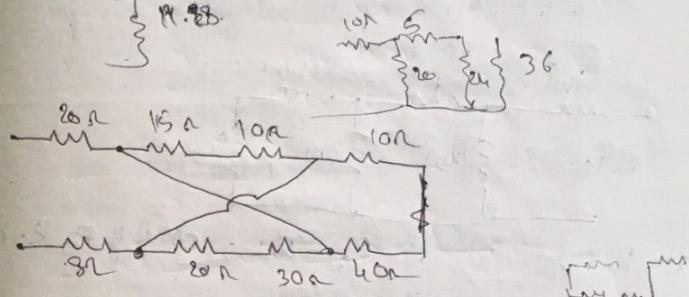


10Ω 5Ω 10Ω 2Ω 3Ω

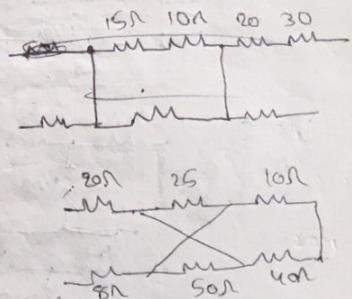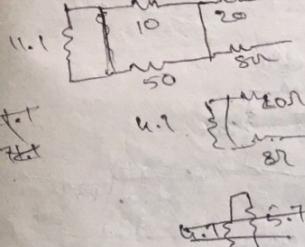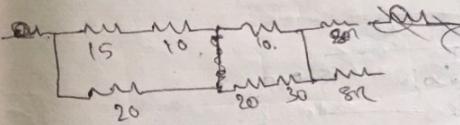

6.9

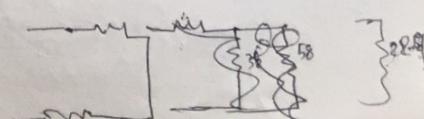


35 18.6  
55 40

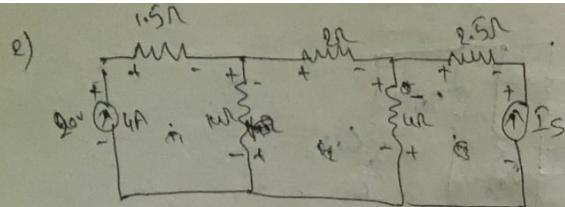


$$-4 + 1.5i_2 + 14i_1 + 2i_0 + 4i_3 + 2.5 + i_s = 0$$

$$-6 + 2^4 + 5 = 0$$

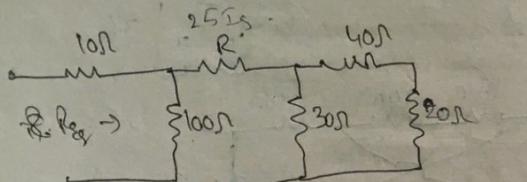

$$a) R = 8 \Omega \quad ; \quad b) R_{\text{eq}} = 8 \Omega \quad ; \quad c) f \neq f_{\text{eq}}, R \neq R_{\text{eq}}$$

(a)  $R = 80\Omega$

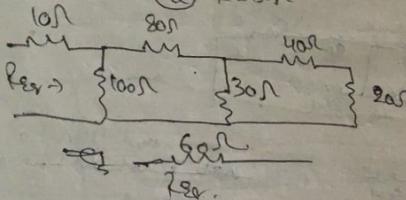


b) 8.

$$\frac{110R + 3200}{R+120} = 80$$

$$140R + 3200 = 80R + 9600$$

$$30R = 6400$$

R = ~~Scor~~, 213.33

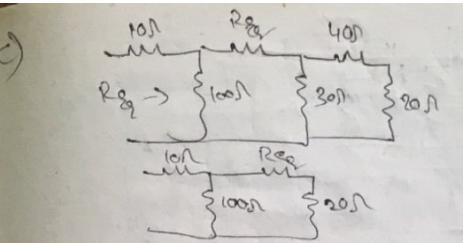

$$\frac{(R_{eq} + 20) \times 100}{(R_{eq} + 20) + 100} + 10 = R_{eq}$$

$$\frac{R_{eq} 100 + 2000}{R_s + 100} + 10 = R_a$$


$$R_{eq} + 100 = \frac{P_2^2}{R_{eq}} + 1200$$


$$110 R_{eq} + 3200 = R_{eq}^2 + 120$$

$$-400 \log + 3080 = P_{eq}^2$$

*[Signature]* Re *[Signature]*

51.1895

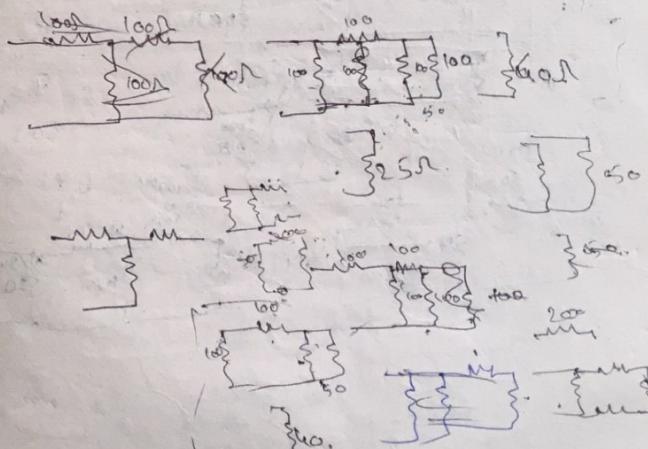


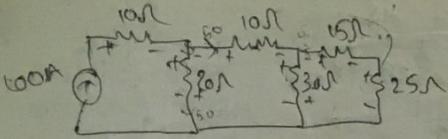

$$100V - 10 - 10.$$



$N = R$

$$25A$$

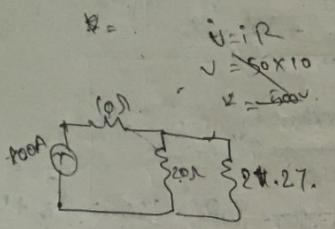

$$I = \frac{100}{20+27} \times 10 = 4.96.$$



$$V = iR$$

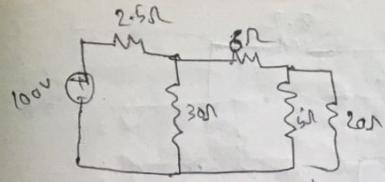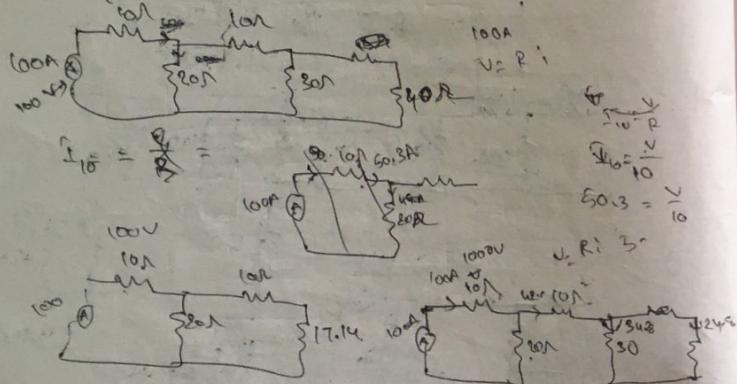



Find the Power absorbed by each resistor.


$$P_{2.5\Omega} =$$

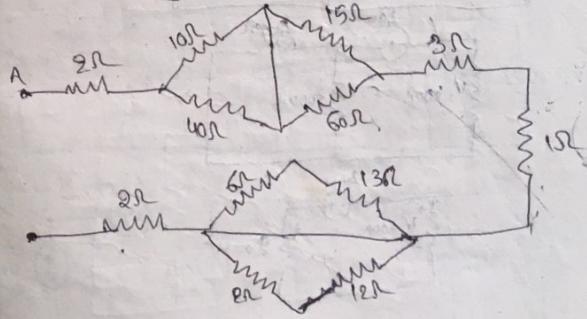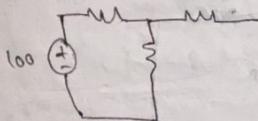- 1)  $P_{\text{out}}$  If a current enters into the terminal of element the power is said to be absorbed.
- 2) +ve terminal element to power it is said to be delivered.
- 3)  $R, L, C \rightarrow$  absorbed powers
- 4)  $V, i \rightarrow$  may absorb (or) deliver.




p)

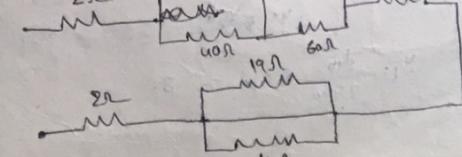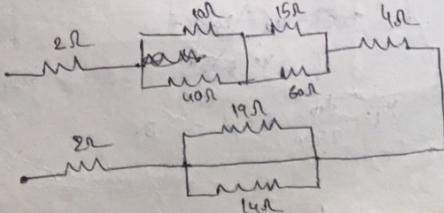



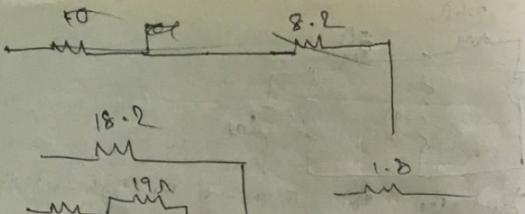


38.

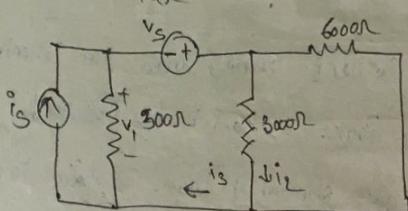

Ans. let  $V_x = 10V$  and find  $i_s$ ; b) let  $i_s = 5A$  and find

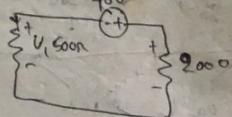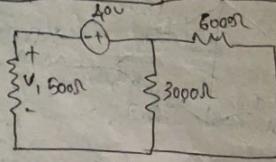
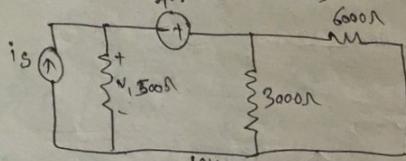
\* calculate ratio of  $V_x/i_s$  when  $i_s = 0$  open circuit  $V_x = 0$  short it



$$300 \times 40 - 40 \times 2000 = -40 = 1600$$


$$V_x = \frac{40}{2500} \times 500 = 8.$$

0.08

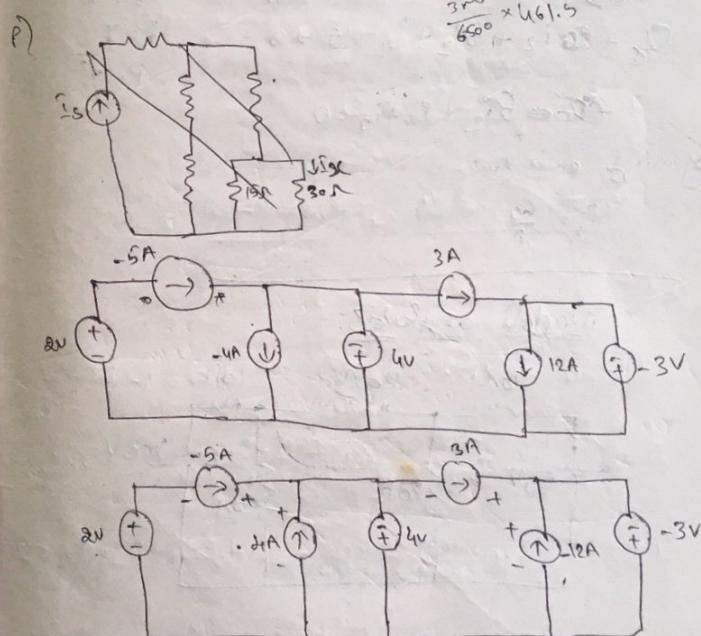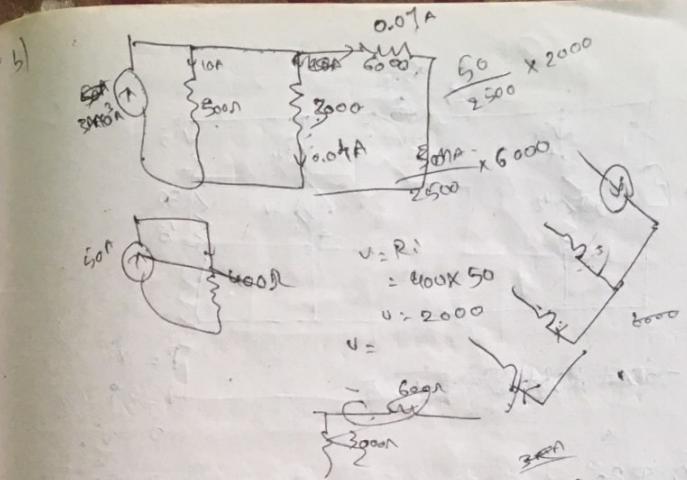

$$P_{xy} = V_x^0 \approx 2 \times -5 = -10 \text{ Watts}$$

1)

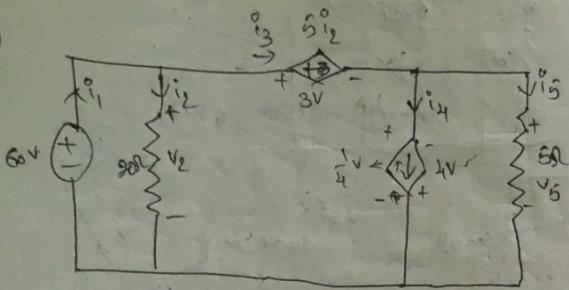

$$-60 + 20i_2 + 3i_3 + 5i_2 + i_4 + i_5 = 0$$


~~60 + 20i<sub>2</sub> + 3i<sub>3</sub> + 5i<sub>2</sub> + i<sub>4</sub> + i<sub>5</sub> = 0~~

$$60 + 10i_2 + 5i_2 + i_4 + i_5 = 0$$



By using ohm's law:-

$$i_1 = \frac{60}{R}$$


Nodal analysis:-

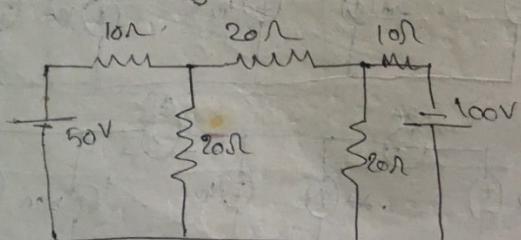
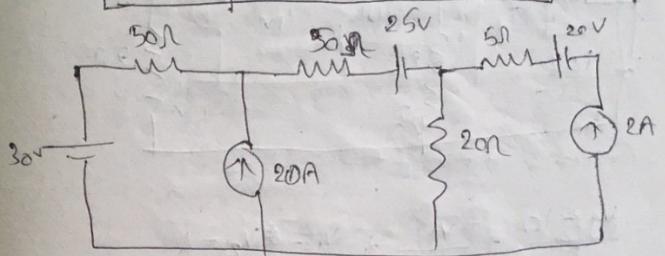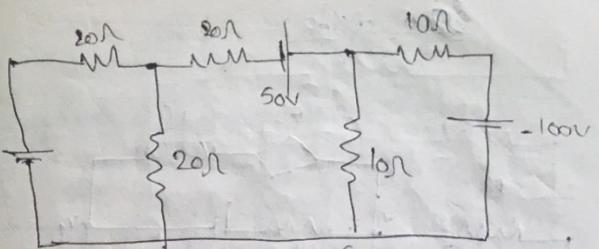
$$\begin{aligned} P &= V^2 \\ V &= R^2 \\ \Rightarrow P &= \frac{V^2}{R} \\ P &= i^2 R \\ R &= \frac{V}{i} \\ R &= V^2 \end{aligned}$$



4)

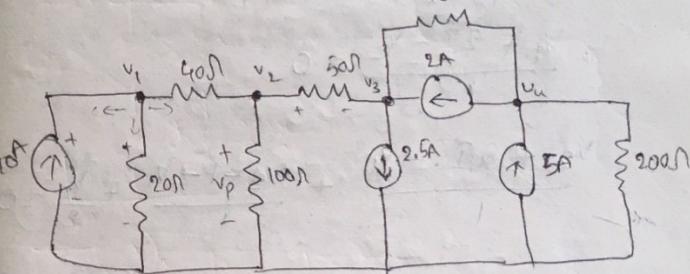


$$10 + \frac{V_1 - V_2}{20} + \frac{V_1 - V_4}{40} = 0$$

$$\frac{V_2 - V_1}{40} + \frac{V_2 - V_3}{100} + \frac{V_2 - V_4}{50} = 0$$

$$\frac{V_3 - V_4}{10} + \frac{V_3 - V_2}{50} + 2.5 - 2 + \frac{V_3 - V_4}{200} = 0$$

$$\frac{V_4 - V_3}{10} + 2 - 5 + \frac{V_4 - V_1}{200} = 0$$

~~Top node :-~~

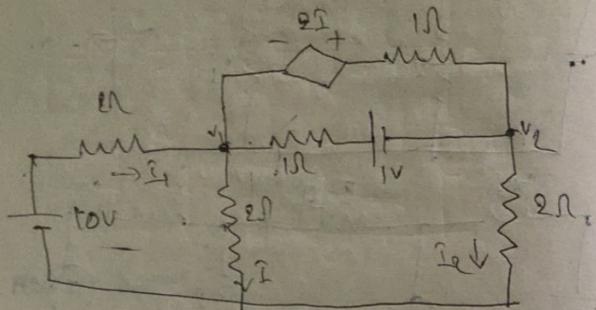

$$\frac{V_1 - 10}{2} + \frac{V_1}{2} + \frac{V_1 - V_2 - 1}{1} = 0$$


$$+ \frac{V_1 + 2i - V_2}{1} = 0$$

$$\frac{V_2 + 2i - V_1}{1} + \frac{V_2 - 1 - V_1}{1} + \frac{V_2}{2} = 0$$

$$V_1 - 10 + V_1 + 2V_1 - 2V_2 + 2 + 2V_1 + 4i - 2V_2 = 0 \quad \text{L1}$$

$$2V_2 + 4i - 2V_1 + 2V_2 - 2 - 2V_1 + V_2 = 0 \quad \text{L2}$$
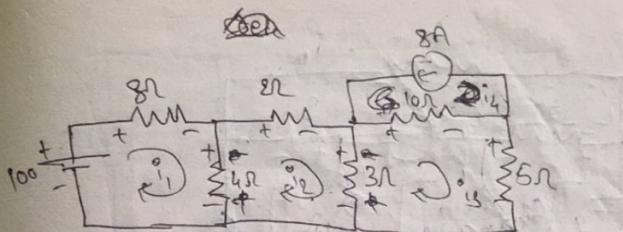
$$2V_1 - 10 + 2V_1 - 2V_1 = 2V_2 - 2 + 2V_1 + 4i - 2V_2 = 0$$



$$100 - 8i_1 - 4i_1 + 4i_2 = 0 \quad \text{①}$$

$$-4i_2 + 4i_1 - 2i_2 + 3i_2 + 3i_3 = 0 \quad \text{②}$$

$$-3i_3 - 10i_4 + 10i_4 - 5i_3 + 5i_2 = 0 \quad \text{③}$$

$$10i_4 = -8 \quad \cancel{\text{L3}}$$

$$-100 + 8i_1 + 4i_1 - 4i_2 = 0 \quad \text{①}$$

$$4i_2 - 4i_1 + 2i_2 + 3i_2 - 3i_3 = 0 \quad \text{②}$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0 \quad \text{③}$$

$$i_4 = 8$$

for ① :-

$$-100 + 12i_1 - 4i_2 = 0$$


② :-

$$9i_2 - 4i_1 - 3i_3 = 0$$

③ :-

$$18i_3 - 3i_2 - 10i_4 = 0$$

$$18i_3 - 3i_2 = 0$$

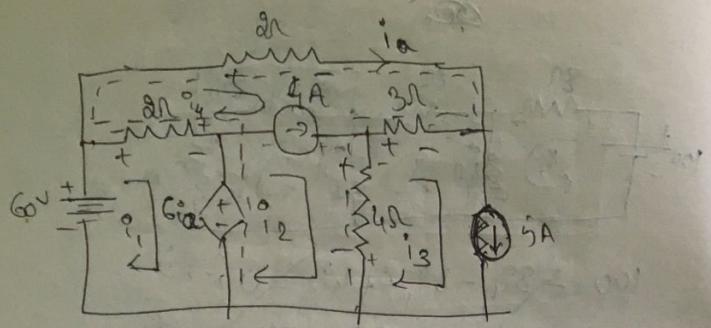

$$-2i_2 - 60 + 2i_1 + 6i_a = 0 \rightarrow \textcircled{1}$$

$$-6i_a - i_2 - i_4 = 4 \rightarrow \textcircled{2}$$

$$i_1 - i_2 + i_3 - i_4 = 0 \rightarrow \textcircled{3}$$

$$+i_3 = 5 \quad i_2 = 4 + i_a$$

$$i_3 = +5 \rightarrow \textcircled{4}$$

$$-6i_a + 2i_4 + 8i_4 - 2i_1 + 3i_4 - 3i_3 + 4i_2 + 4i_3 = 0$$

L(4)

$$-60 + 2i_1 + 6i_a = 0$$

$$i_2 - i_4 = 4 \quad i_3 = +5$$


$$-6i_a + 8i_4 - 2i_1 - 7i_3 + 4i_2 = 0$$

$$-6i_a + 11i_4 - 2i_1 + 35 + 4i_2 = 0$$

$$-6i_a + 11i_4 - 2i_1 + 35 + 16 + 4i_2 = 0$$

$$-6i_a + 17i_4 - 2i_1 + 51 = 0$$

$$-6i_a$$

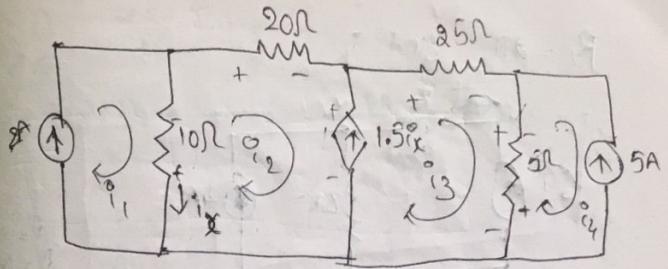

$$i_1 = i_2$$

~~$$-10i_2 + 10i_2 + 20i_2 + 1.5i_x = 0$$~~

~~$$-1.5i_x + 25i_3 + 5i_3 - 5i_u = 0$$~~

~~$$i_1 = i_2$$~~

$$i_{11} = 2$$


$$i_1 - i_2 = i_x$$

$$-1.5i_x + 25i_3 + 5i_3 - 5i_u = 0$$

$$i_u = 5$$



$$R_L = 2\Omega \text{ find } i_L$$

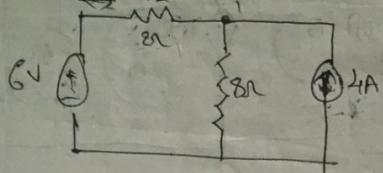

$$i_L = \frac{V_1}{R_L} = \frac{6}{2} = 3A.$$

$$\begin{aligned} P &= V_i^2 \\ P &= V_i R \\ P &= i^2 R \\ P &= 16 \times 3 \\ P &= 48 \text{ Watts} \end{aligned}$$

$$\frac{V_1 - 6}{2} + \frac{V_1}{8} - 4 = 0$$

$$2V_1 - 12 + V_1 - 32 = 0$$

$$3V_1 - 56 = 0$$





$$V_1 = \frac{56}{3} = 11.2V$$

$$i_L = \frac{V_1}{R_L} = \frac{11.2 - 6}{2} = \frac{5.2}{2} = 2.6A.$$

$$P = V_i \times i_L$$

$$= 11.2 \times 2.6 = 29.12 \text{ Watts}$$

$$= 44.8 \text{ Watts}$$

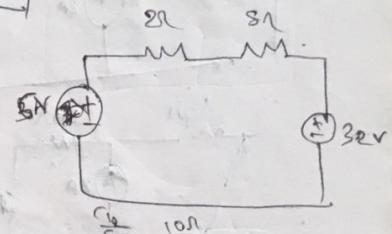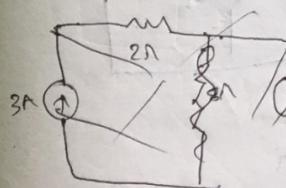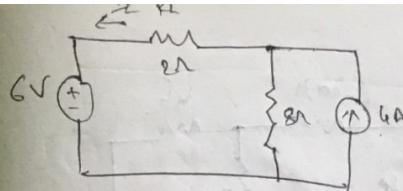
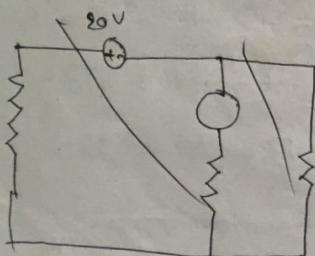


$$32 + 10i_L + 6 = 0$$

$$32 + 10i_L = 0$$

$$32 - 6 = 12$$

Superposition Th:-

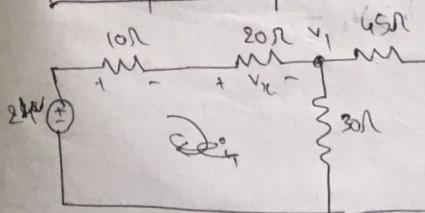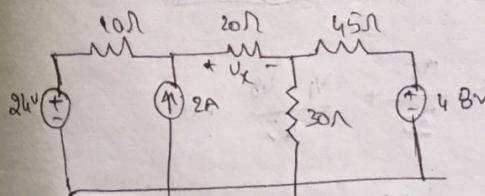



$$\begin{aligned} i_1 &= \frac{V_1 - 24}{30} = \frac{24 - 24}{30} = 0 \\ i_2 &= -\frac{15}{30} = -\frac{1}{2} \\ i &= 0.5 \end{aligned}$$

$$\frac{V_1 - 24}{30} + \frac{V_1}{30} + \frac{V_1}{45} = 0 \quad i = 0.5$$


$$45V - 1080 + 45V_1 + 30V_1 = 0$$

$$19V_1 = 1080 \quad V_1 = 56.3$$

$$V_1 = 9V$$

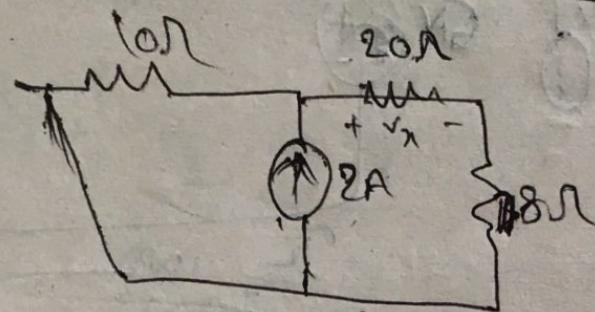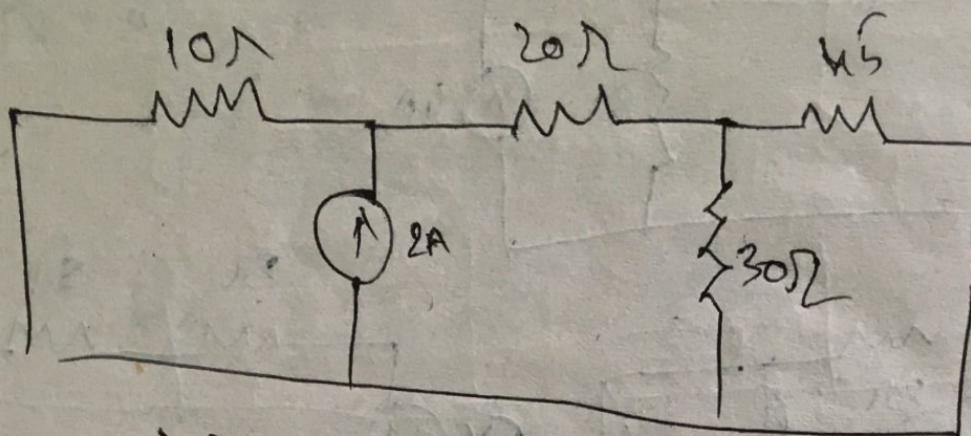

$$V_x = \frac{2}{38} \times 18 = 0.9V$$

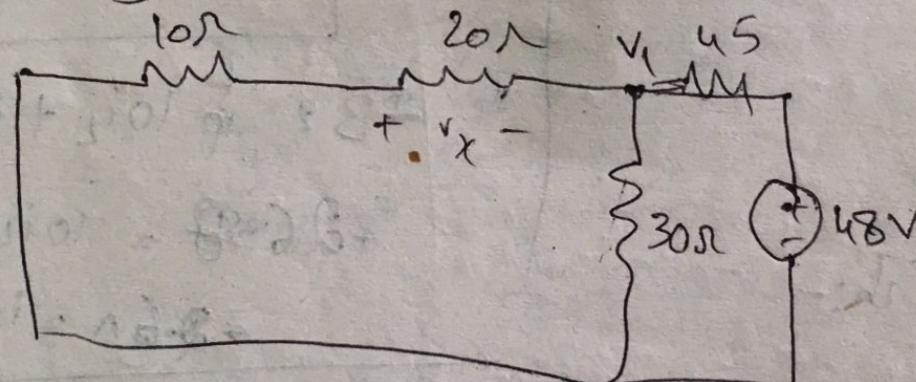

$$\frac{V_1}{38} + \frac{V_1}{30} + \frac{V_1 - 48}{45} = 0$$

$$45V_1 + 45V_1 +$$